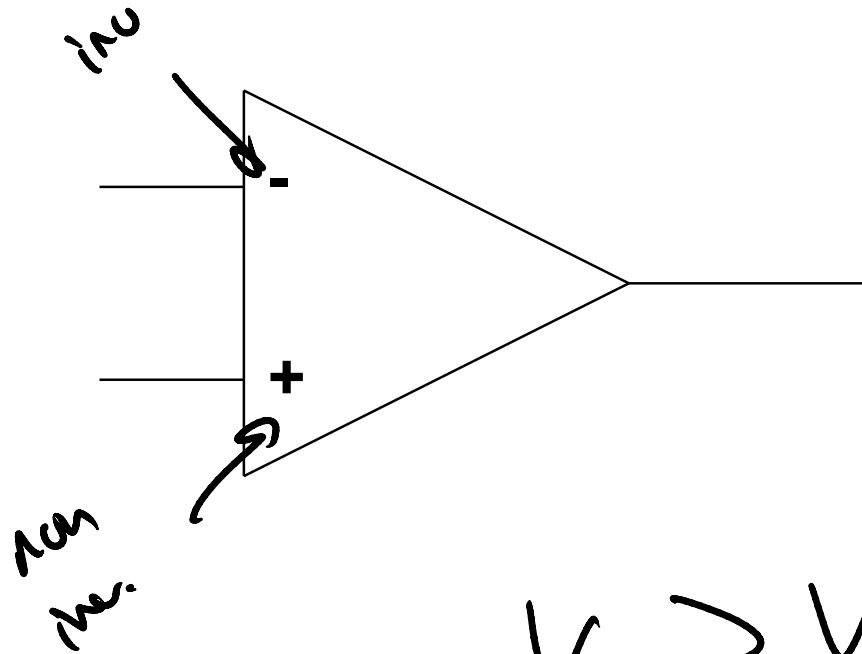


Operational Amplifiers (OpAmps) and Comparators

Cyrus Bazeghi
Winter 2010



Operational Amplifier



$$V_{out} = G (V_+ - V_-)$$

* where $G \rightarrow \infty$
100k


⊙ inputs draw no current

$$V_+ > V_- \quad \uparrow \quad V_{out}$$

$$V_+ < V_- \quad \downarrow \quad V_{out}$$



How do we use OpAmps?

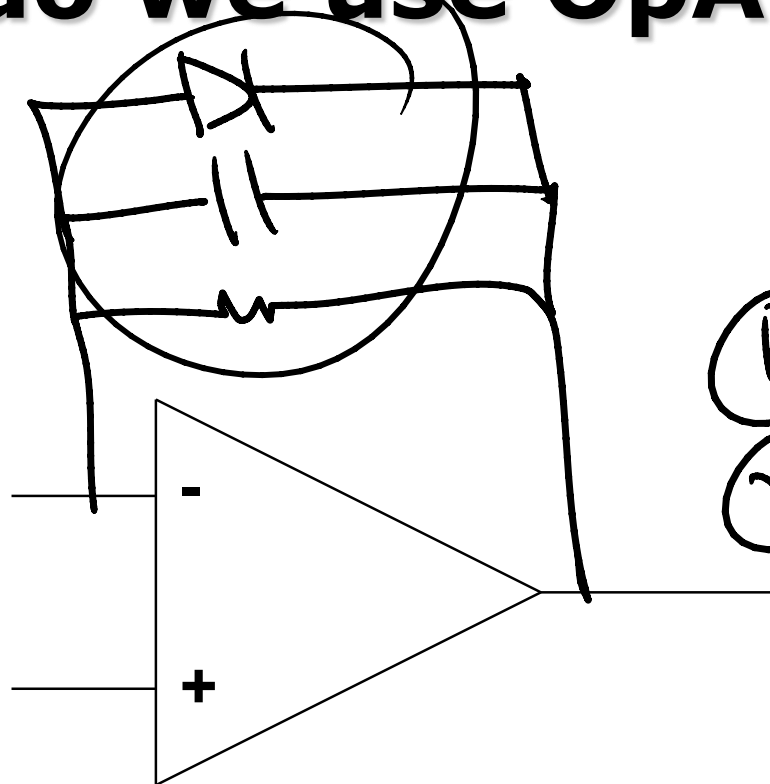

Not working

- ① Pull Up
- ② Feedback

Always use on negative
Feedback



The Golden Rules

ideal


- (1) inputs draw no current
- (2) $v_- = v_+$ are the same voltage

applies only when


- + negative feedback
- + within op. specs



Inverting Amplifier

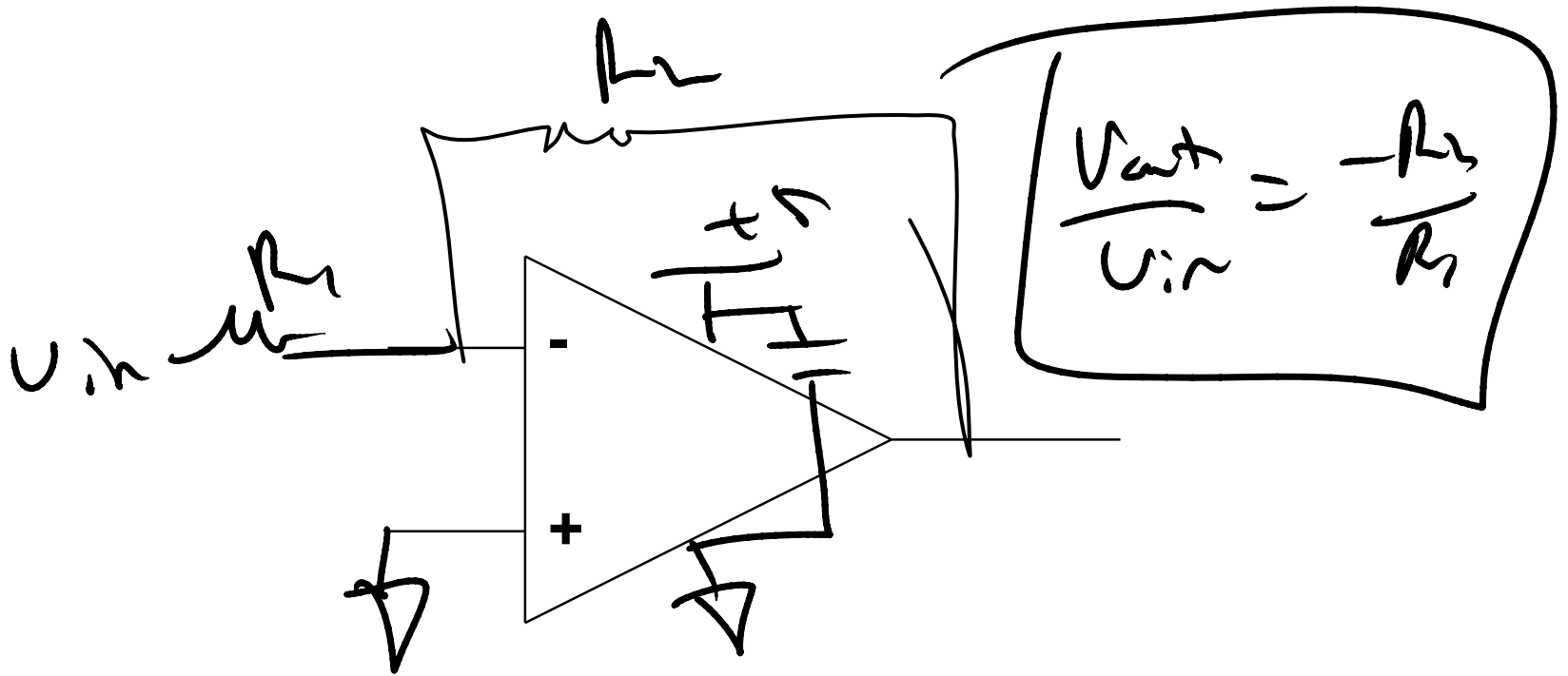


Non-Inverting Amplifier

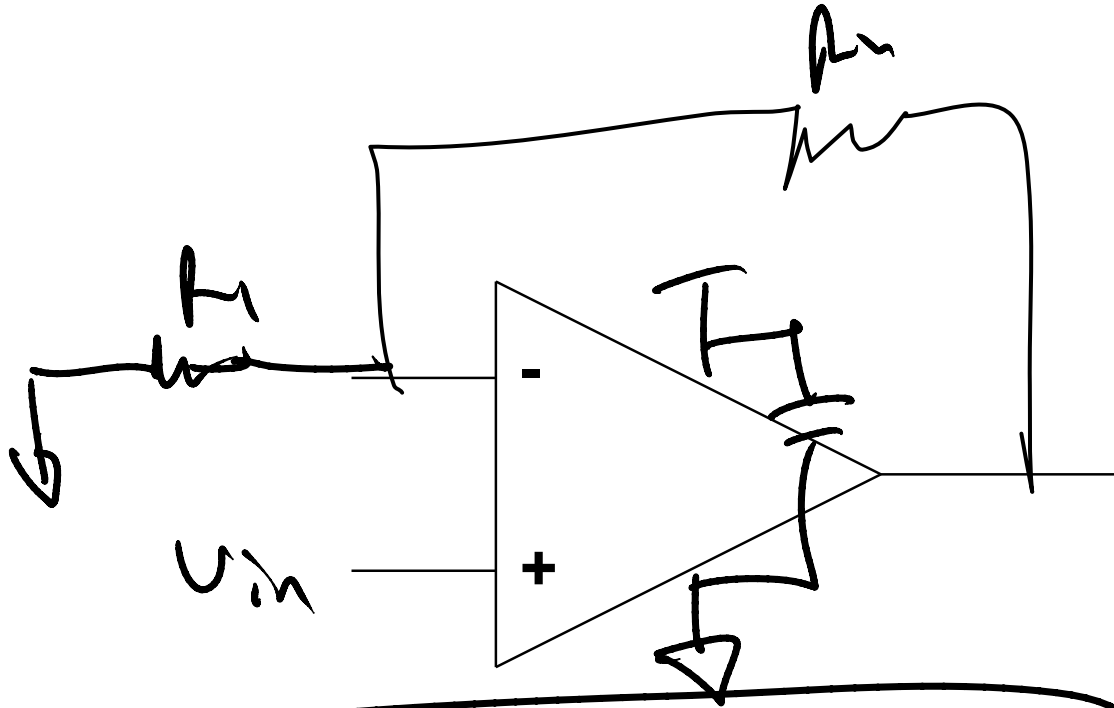


$$\frac{v_{out}}{v_{in}} = 1 + \frac{R_2}{R_1}$$



Non-Inverting Buffer

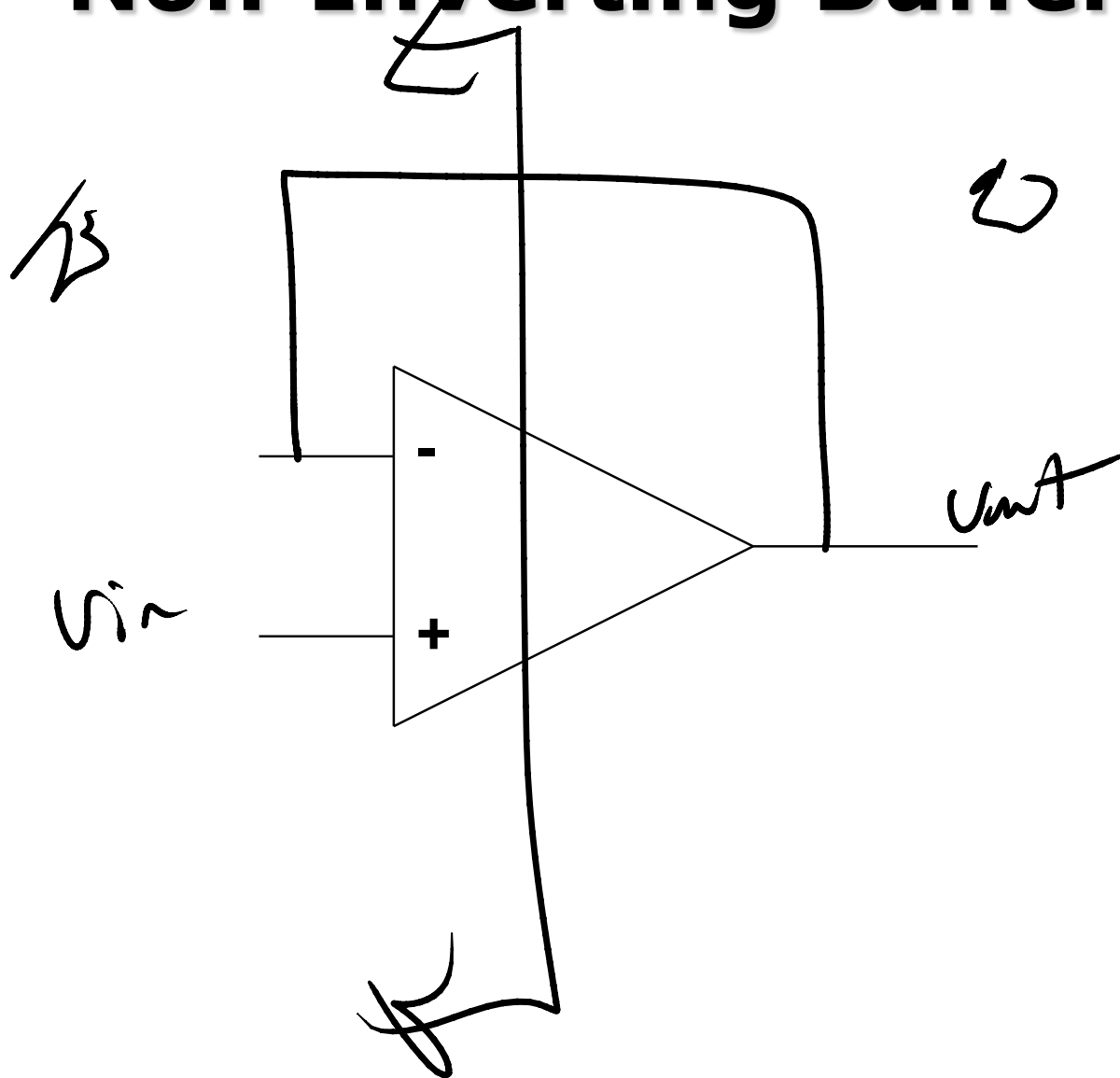

What about a real source?

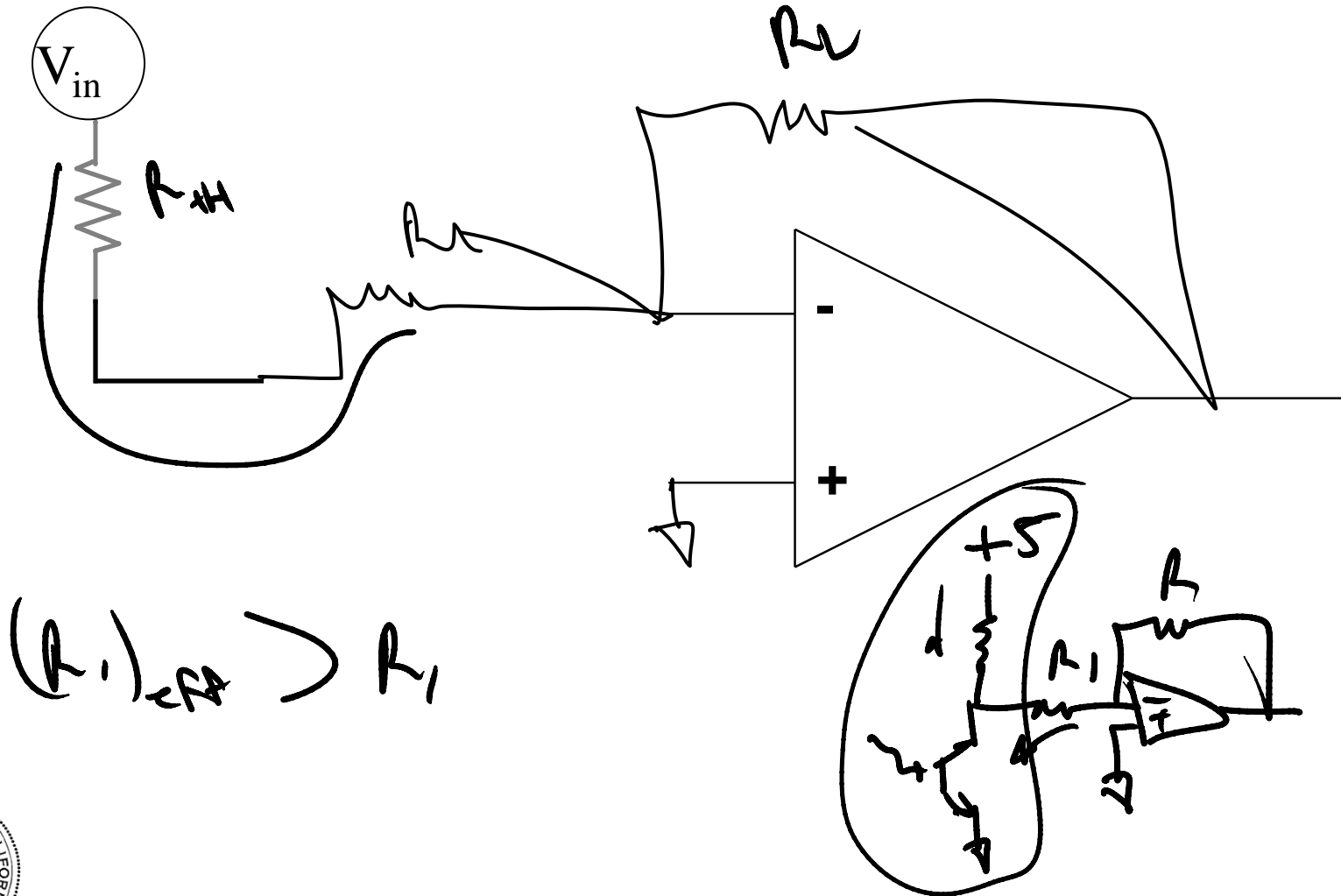


$$(R_i)_{opA} \gg R_i$$




What if I connect the two inputs?

ideal op amp : $V_{out} = 0$

real. Life : rail one way or the other

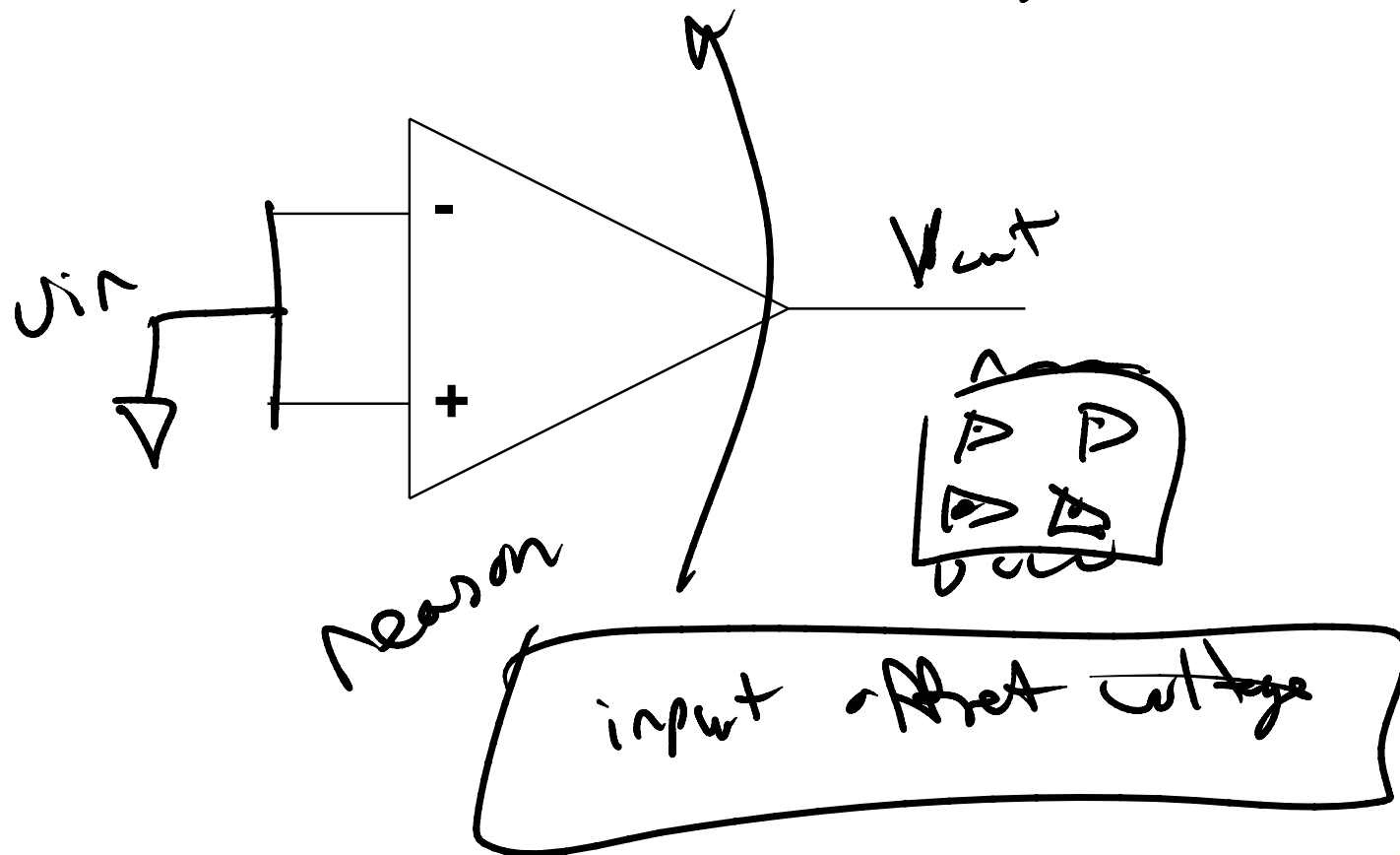


Input Offset Voltage?

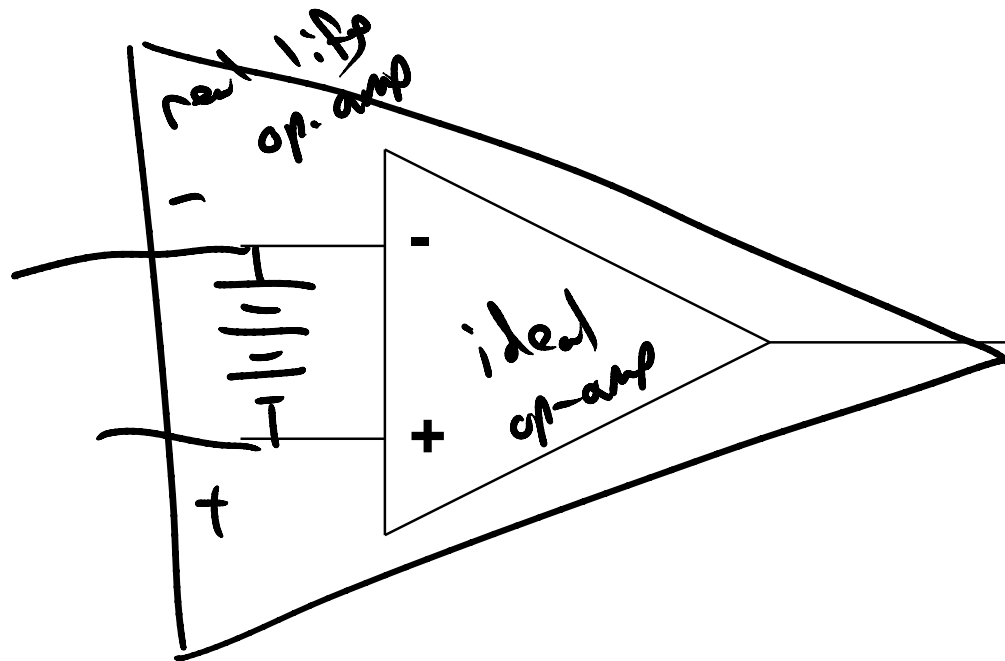


Input Offset Voltage Specifications

ELECTRICAL CHARACTERISTICS ($V_{CC} = 5.0\text{ V}$, $V_{EE} = \text{Gnd}$, $T_A = 25^\circ\text{C}$, unless otherwise noted.)


Characteristics	Symbol	LM224			LM324A			LM324			LM2902			LM2902V/NCV2902			Unit
		Min	Typ	Max	Min	Typ	Max	Min	Typ	Max	Min	Typ	Max	Min	Typ	Max	
Input Offset Voltage $V_{CC} = 5.0\text{ V to }30\text{ V}$ (26 V for LM2902, V), $V_{ICR} = 0\text{ V to }V_{CC} - 1.7\text{ V}$, $V_O = 1.4\text{ V}$, $R_S = 0\ \Omega$ $T_A = 25^\circ\text{C}$	V_{IO}																mV
$T_A = T_{\text{high}}$ (Note 2)		-	2.0	5.0	-	2.0	3.0	-	2.0	7.0	-	2.0	7.0	-	2.0	7.0	
$T_A = T_{\text{low}}$ (Note 2)		-	-	7.0	-	-	5.0	-	-	9.0	-	-	10	-	-	13	
		-	-	7.0	-	-	5.0	-	-	9.0	-	-	10	-	-	10	
Average Temperature Coefficient of Input Offset Voltage $T_A = T_{\text{high}} \text{ to } T_{\text{low}}$ (Notes 2 and 4)	$\Delta V_{IO}/\Delta T$	-	7.0	-	-	7.0	30	-	7.0	-	-	7.0	-	-	7.0	-	$\mu\text{V}/^\circ\text{C}$

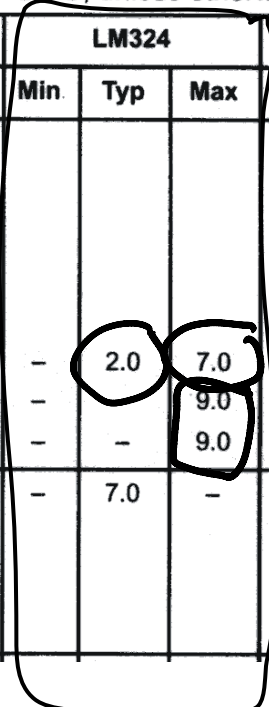

Effects of Input Offset Voltage

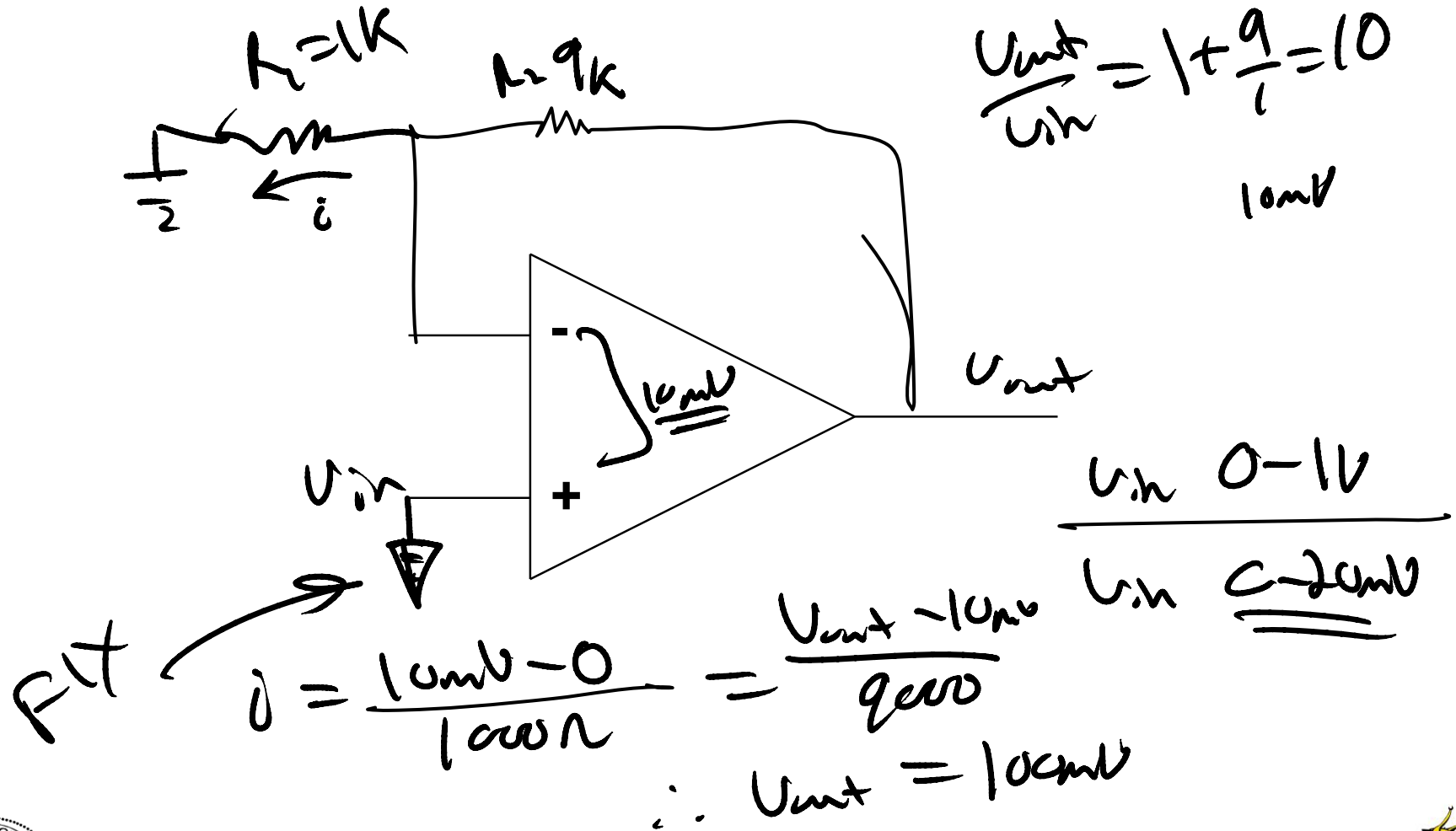


How to fix

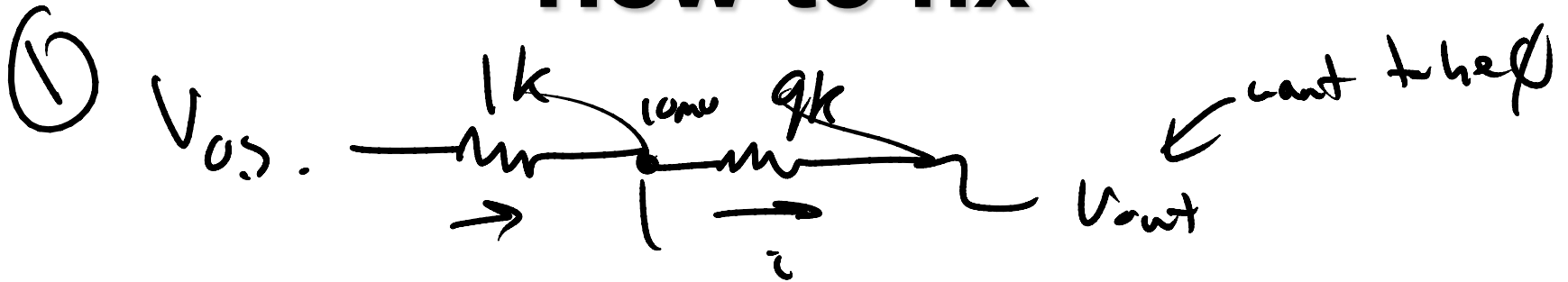


$$i = \frac{10\mu\text{V} - 0}{9k} = 11.1\mu\text{A}$$

$$11.1\mu\text{A} = \frac{V_{os} - 10\text{mV}}{1k}$$

$$V_{os} = 21.1\text{mV}$$

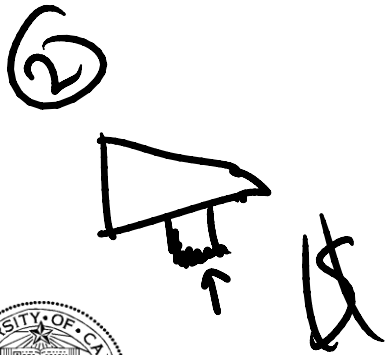

Input Bias Current

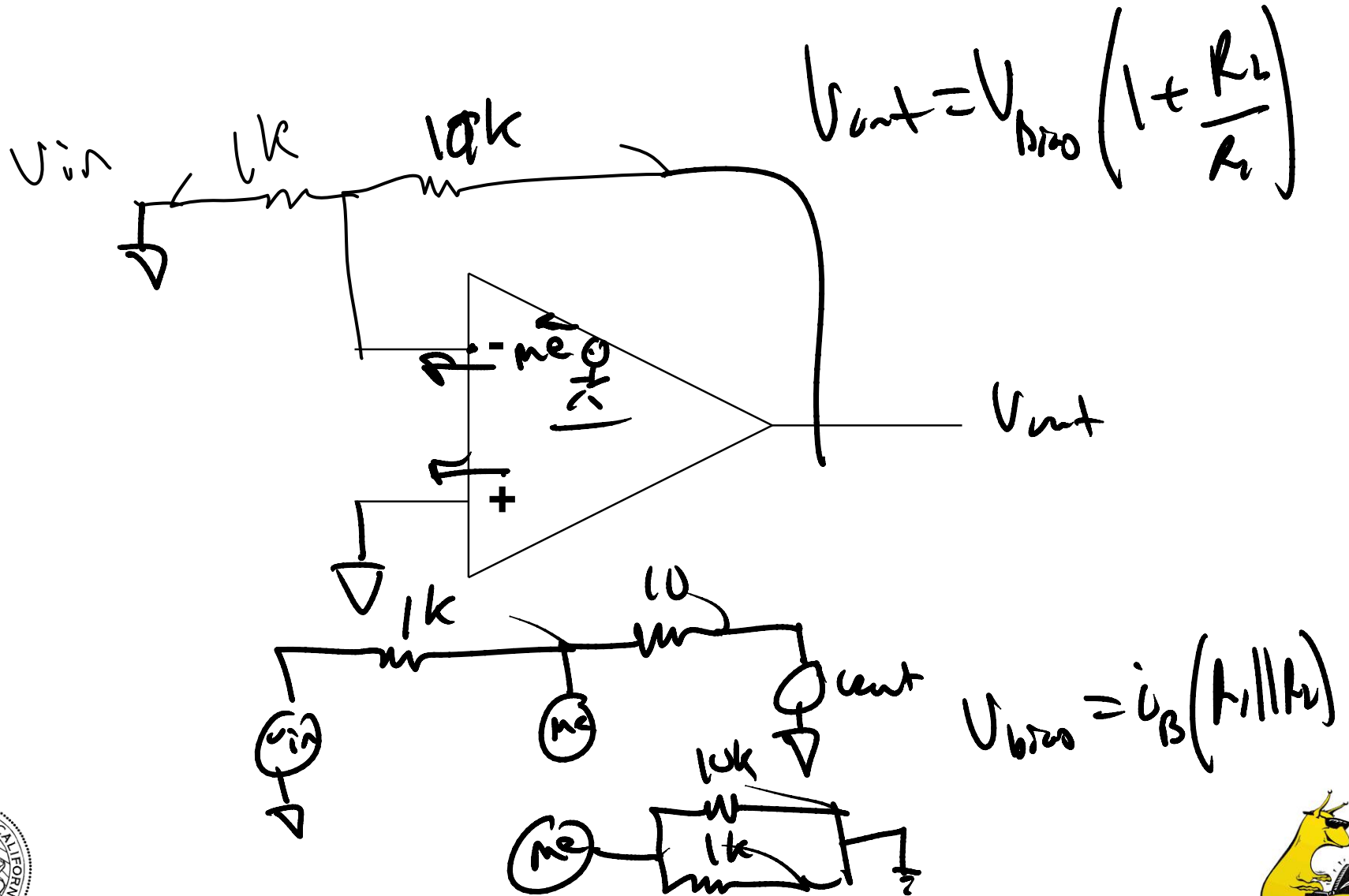

Input Bias Current Specifications


Input Offset Current $T_A = T_{high} \text{ to } T_{low}$ (Note 2)	I_{IO}	-	3.0	30	-	5.0	30	-	5.0	50	-	5.0	50	-	5.0	50	nA
Average Temperature Coefficient of Input Offset Current $T_A = T_{high} \text{ to } T_{low}$ (Notes 2 and 4)	$\Delta I_{IO}/\Delta T$	-	10	-	-	10	300	-	10	-	-	10	-	-	10	-	pA/°C
Input Bias Current $T_A = T_{high} \text{ to } T_{low}$ (Note 2)	I_{IB}	-	-90	-150	-	-45	-100	-	-90	-250	-	-90	-250	-	-90	-250	nA
Input Common Mode	V_{ICM}	-	-	-300	-	-	-200	-	-	-500	-	-	-500	-	-	-500	V

min 324 max

-90nA → 250nA
250nA @ H.T.



Can We Correct for Input Bias Current

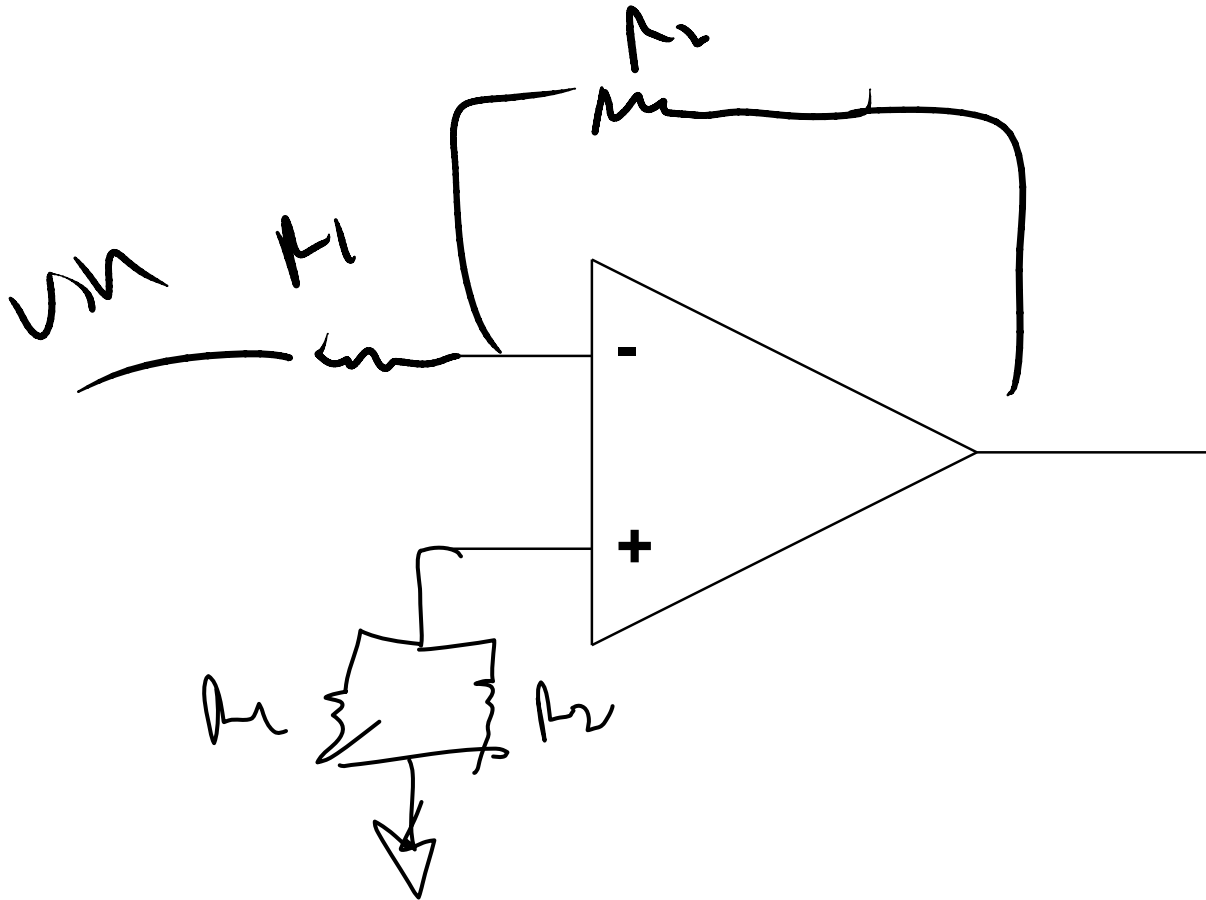

Does this fix the bias current problem?

<p>Input Offset Current $T_A = T_{high} \text{ to } T_{low}$ (Note 2)</p>	I_{IO}	-	3.0	30	-	5.0	30	-	5.0	50	-	5.0	50	-	5.0	50	nA
<p>Average Temperature Coefficient of Input Offset Current $T_A = T_{high} \text{ to } T_{low}$ (Notes 2 and 4)</p>	$\Delta I_{IO}/\Delta T$	-	10	-	-	10	300	-	10	-	-	10	-	-	10	-	pA/°C
<p>Input Bias Current $T_A = T_{high} \text{ to } T_{low}$ (Note 2)</p>	I_{IB}	-	-90	-150	-	-45	-100	-	-90	-250	-	-90	-250	-	-90	-250	nA
<p>Input Common Mode</p>	V_{ICM}																V


324

9

-250



Output Voltage Limitations

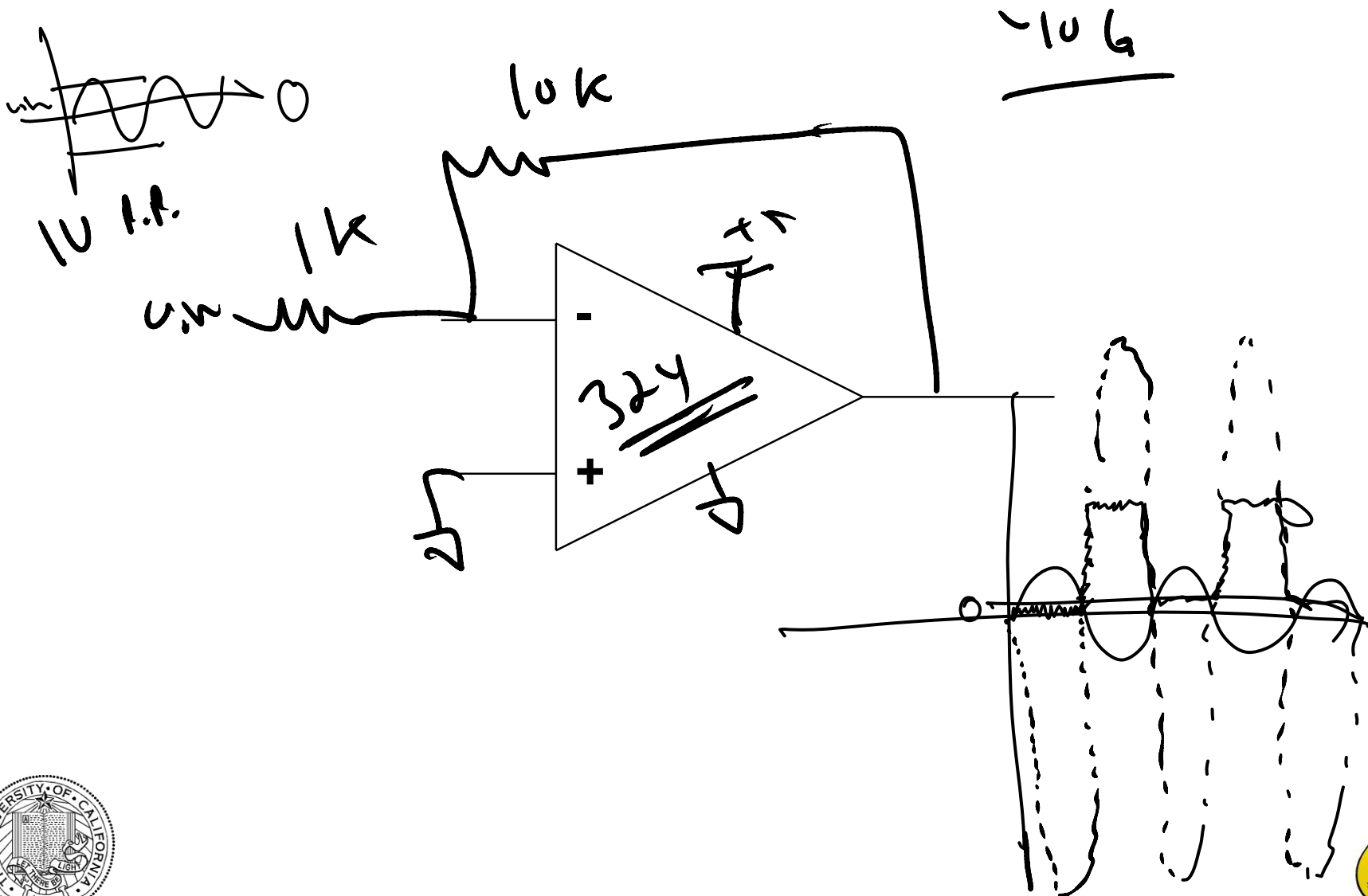

Does that fix the bias current problem?



Output Voltage Specifications

ELECTRICAL CHARACTERISTICS ($V_{CC} = 5.0\text{ V}$, $V_{EE} = \text{Gnd}$, $T_A = 25^\circ\text{C}$, unless otherwise noted.)


Characteristics	Symbol	LM224			LM324A			LM324			LM2902			LM2902V/NCV2902			Unit
		Min	Typ	Max	Min	Typ	Max	Min	Typ	Max	Min	Typ	Max	Min	Typ	Max	
Output Voltage— High Limit ($T_A = T_{\text{high}}$ to T_{low}) (Note 5)	V_{OH}																V
$V_{CC} = 5.0\text{ V}$, $R_L = 2.0\text{ k}\Omega$, $T_A = 25^\circ\text{C}$		3.3	3.5	—	3.3	3.5	—	3.3	3.5	—	3.3	3.5	—	3.3	3.5	—	
$V_{CC} = 30\text{ V}$ (26 V for LM2902, V), $R_L = 2.0\text{ k}\Omega$		26	—	—	26	—	—	26	—	—	22	—	—	22	—	—	
$V_{CC} = 30\text{ V}$ (26 V for LM2902, V), $R_L = 10\text{ k}\Omega$		27	28	—	27	28	—	27	28	—	23	24	—	23	24	—	
Output Voltage— Low Limit, $V_{CC} = 5.0\text{ V}$, $R_L = 10\text{ k}\Omega$, $T_A = T_{\text{high}}$ to T_{low} (Note 5)	V_{OL}	—	5.0	20	—	5.0	20	—	5.0	20	—	5.0	100	—	5.0	100	mV
Output Source Current	I_{OS}																mA

$R_L = 2.0\text{ k}\Omega$

not very close to rails at all




The Importance of Test Conditions

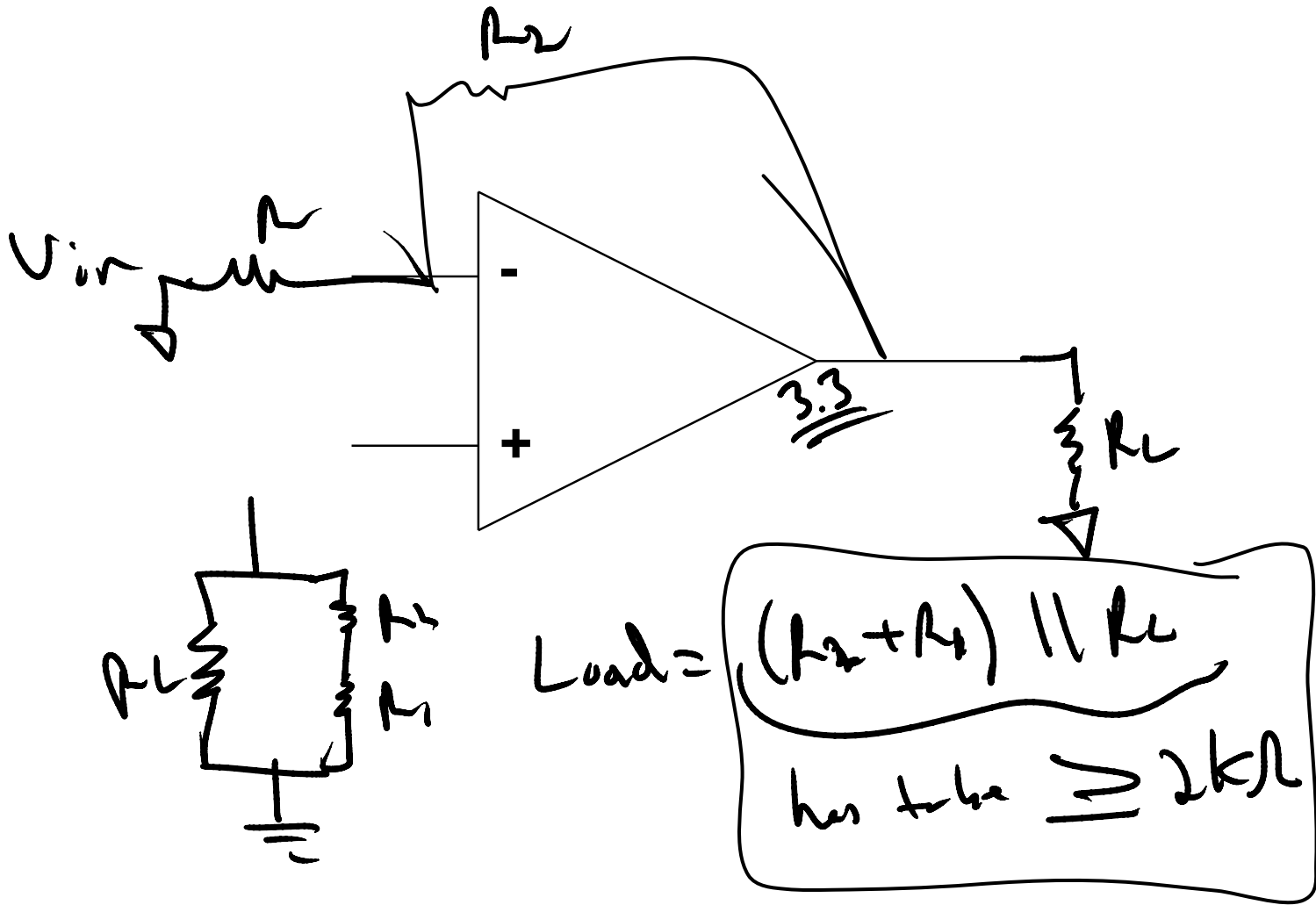

A Comparison of Some Op-Amps


Parameter	LM324	LM6144	LMC6484	LMC6494
Input Offset Voltage	7mV	3.3mV	3.7mV	6.8mV
Input Bias Current	250nA	526nA	4pA	200pA
Input Offset Current	50nA	80nA	2pA	100pA
Output Voltage Hi @ 10K Ω	3.5V	4.87V		
Output Voltage Lo @ 10K Ω	0.02V	0.05V		
Output Voltage Hi @ 2K Ω	3V	4.8V	4.7V	4.7V
Output Voltage Lo @ 2K Ω		0.13	0.24V	0.24V
Output Voltage Hi @ 600 Ω			4.24V	4.24V
Output Voltage Lo @ 600 Ω			0.65V	0.65V
Unity Gain Bandwidth	1MHz	6MHz	1.5MHz	1.5MHz
Slew Rate	0.42V/ μ S	11V/ μ S	0.63V/ μ S	0.5V/ μ S
Input Common Mode Range	0-3.5V	0-5V	0-5V	0-5V
Cost @ 1k	\$0.088	\$2.80	\$1.39	\$1.59
Temperature Range	0° – 70° C	-40° – 85° C	-40° – 85° C	-40° – 125° C

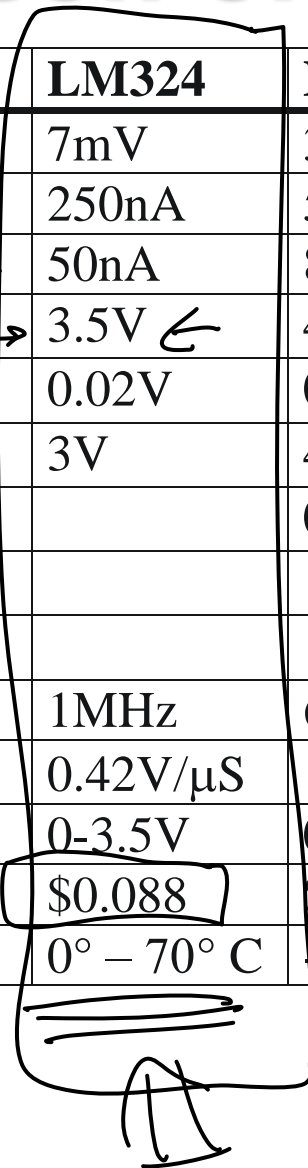


What is this?

Comparator

Very fast, not linear

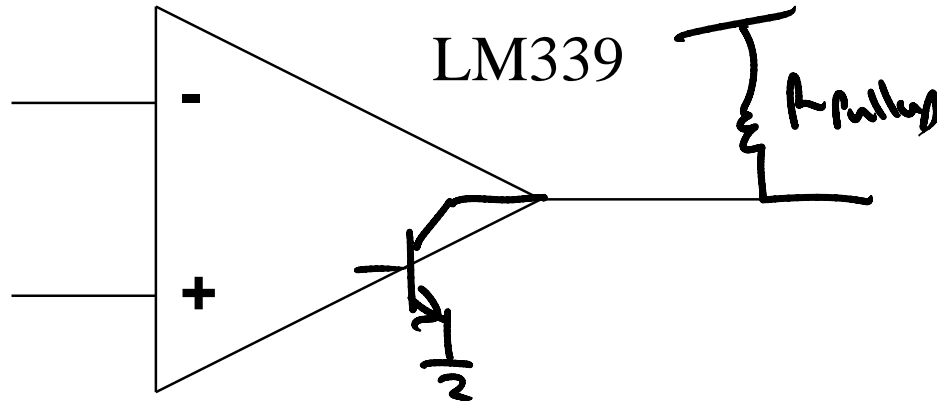

The Comparator

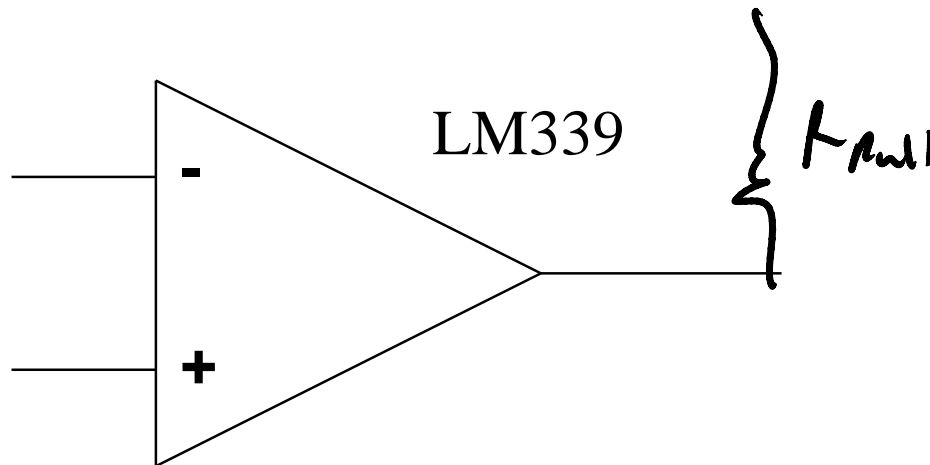


outputs!




Comparator : open collector
op amp : push-pull (to terminate)






How might you use it?

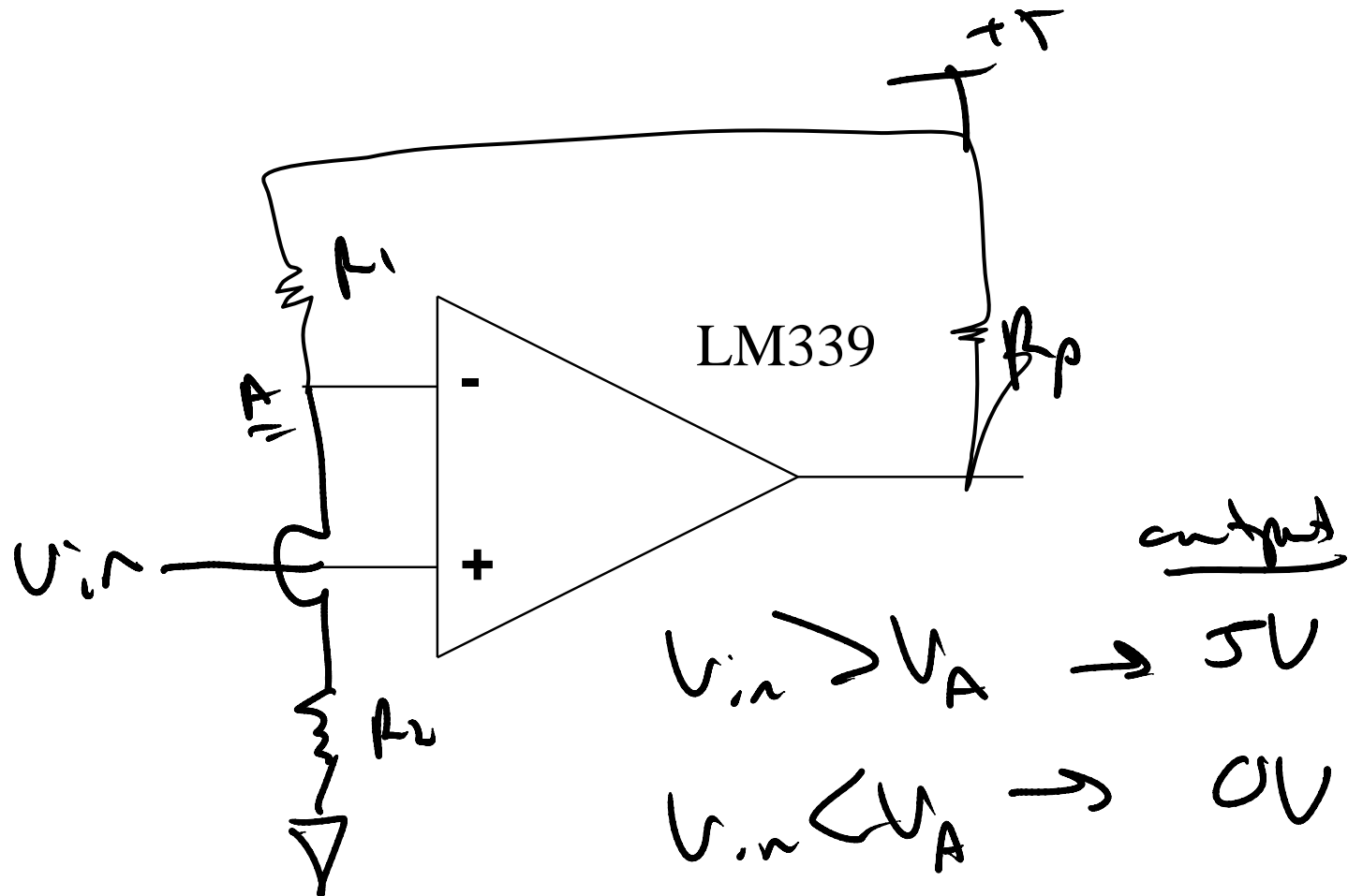


Implementing Hysteresis

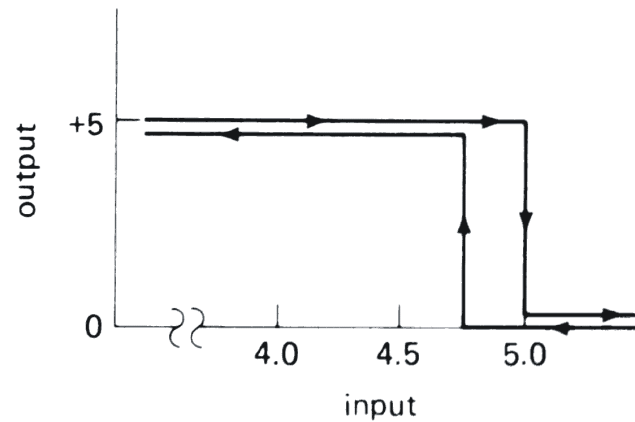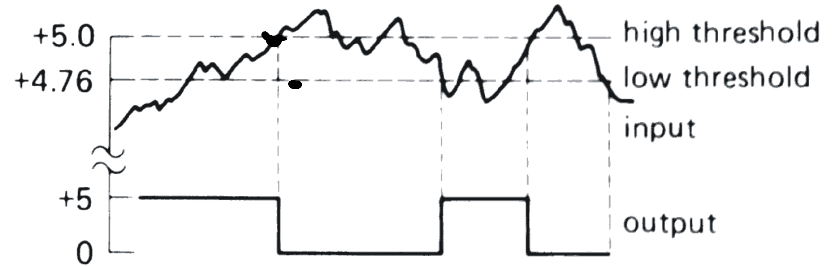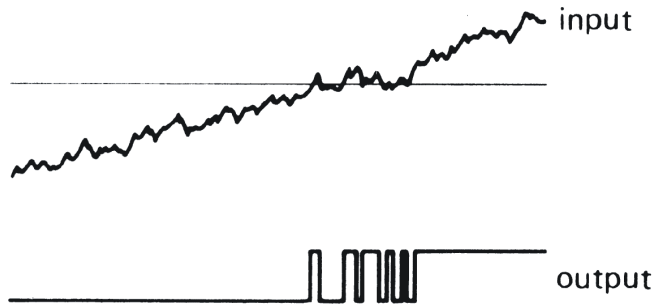


How does this work?

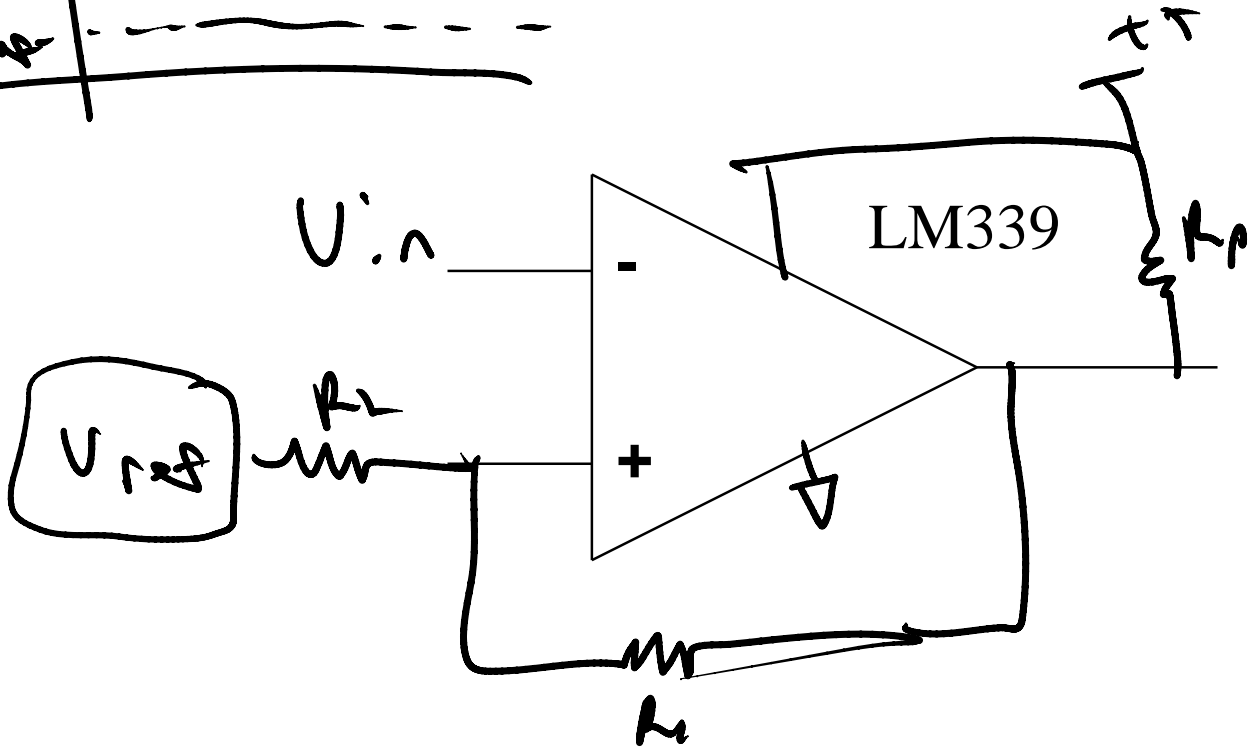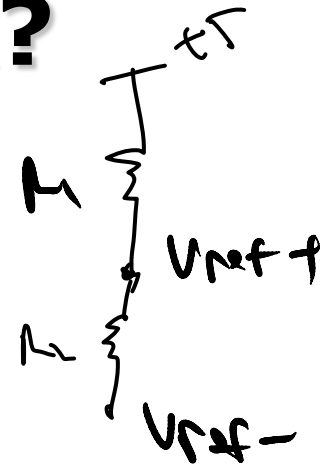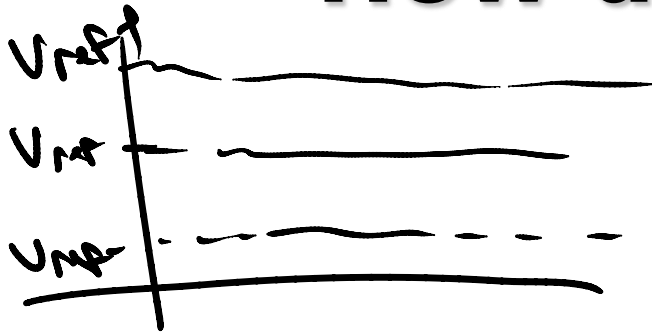

Same schmitt trigger

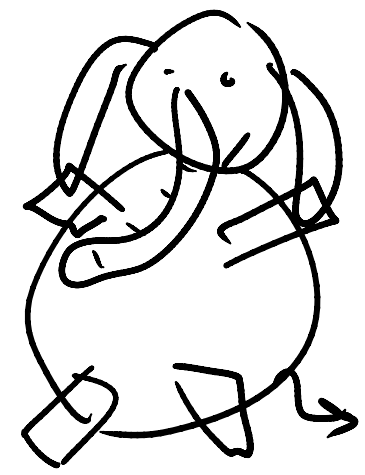


Eliminating the separate Vref?

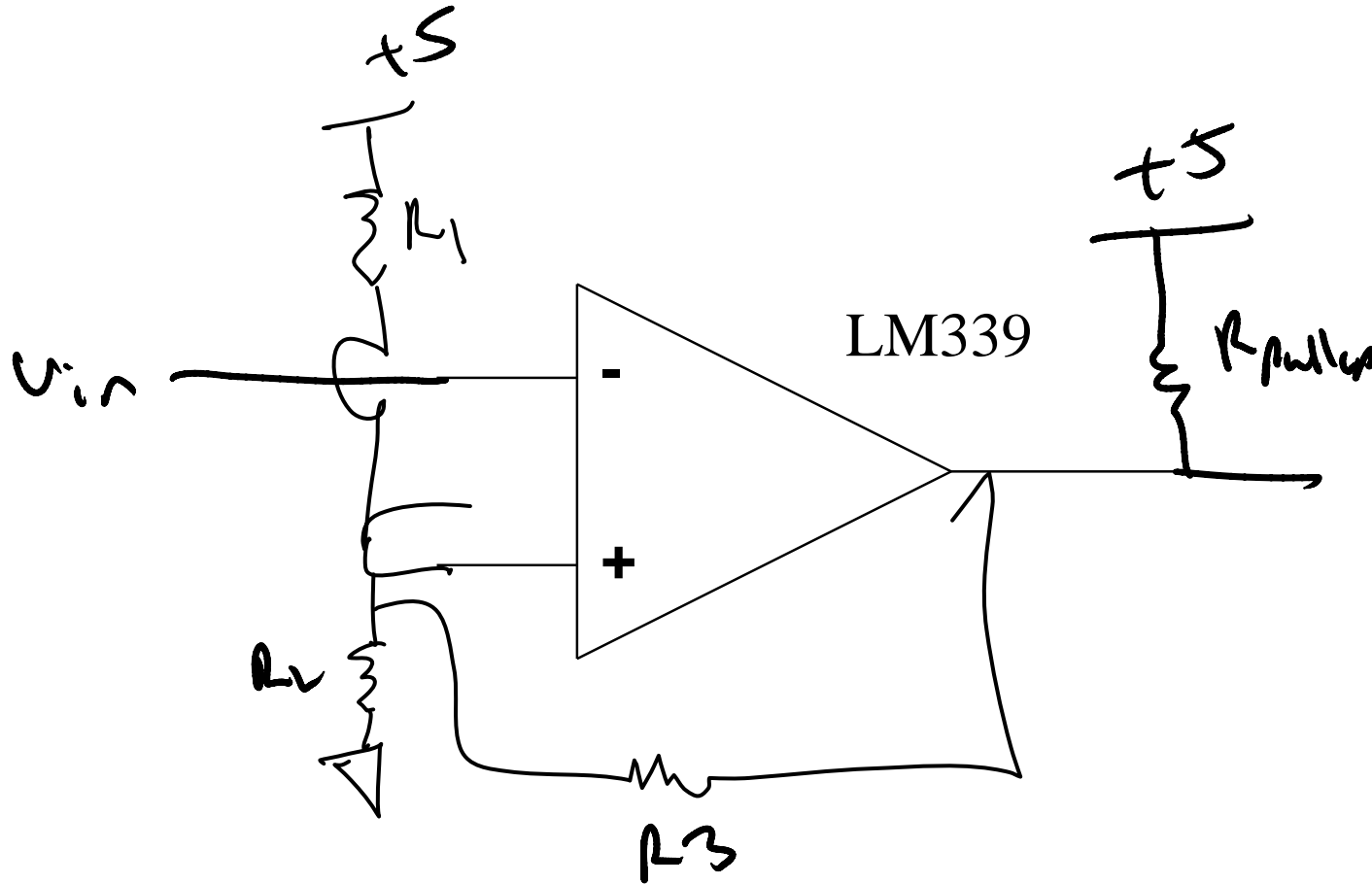


What is going on?

iA output high

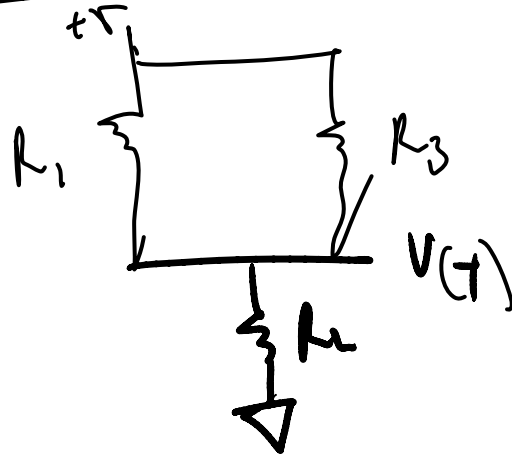

$$R_3 \gg R_2$$

iA output low

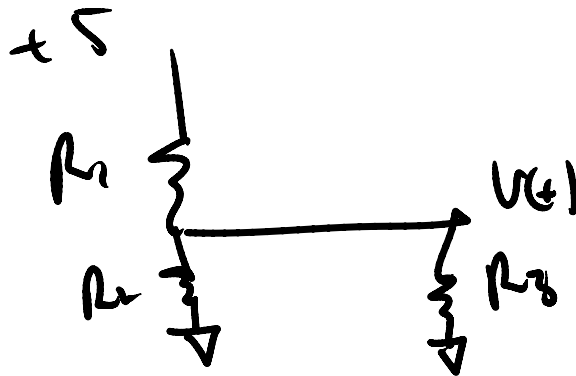

Inverting Comparator Design

Procedure (1.3) *Cookbook on Comp.*

V_{A1} = high threshold

V_{A2} = low threshold

$$\Delta V = V_{A1} - V_{A2}$$

$$N = \frac{\Delta V}{V_{A2}}$$


$$R_1 = N R_3$$

$$R_2 = \frac{R_1 \parallel R_3}{\left(\frac{V_{CC}}{V_{A1}} - 1\right)}$$

pick:

$$R_3 = 1 \text{ M}\Omega$$

$$R_1 = 3.9 \text{ k}\Omega$$

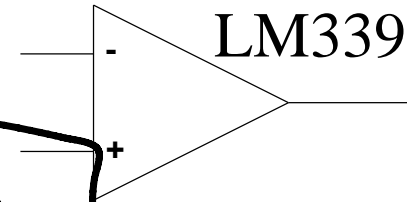

if R_1 too big ($> 1 \text{ M}\Omega$)
then reduce R_3
& try again



Inverting Comparator Design Procedure (2.3)

$$V_{AI} = 1.625$$

$$V_{AL} = 1.375$$

$$\Delta V = 0.25$$


$$N = \frac{0.25}{1.375} = 0.182$$

$$R_3 = 1\text{M}\Omega$$

$$R_1 = NR_3 = 182\text{k}\Omega$$

$$R_2 = \frac{182\text{k}\Omega \parallel 1\text{M}\Omega}{\frac{5}{1.625} - 1} \approx \frac{154\text{k}\Omega}{2} \approx 77\text{k}\Omega$$

trip point \odot 1.5V
 ΔV 0.25V
 hyst.

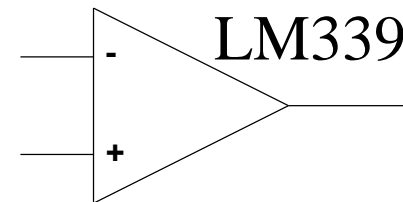

The Non-Inverting Configuration

