

Stepper Motors

Cyrus Bazeghi
Winter 2010

;) :



Stepper Motors

- Different types of stepper motors
- Differences in Characteristics
- Stepper Drive Techniques
- Stepper Dynamics
- Snubbing for Stepper Motors

P.M.
V.R.
Hybrid


lab

Detent Torque




Permanent Magnet (PM) Stepper Motor

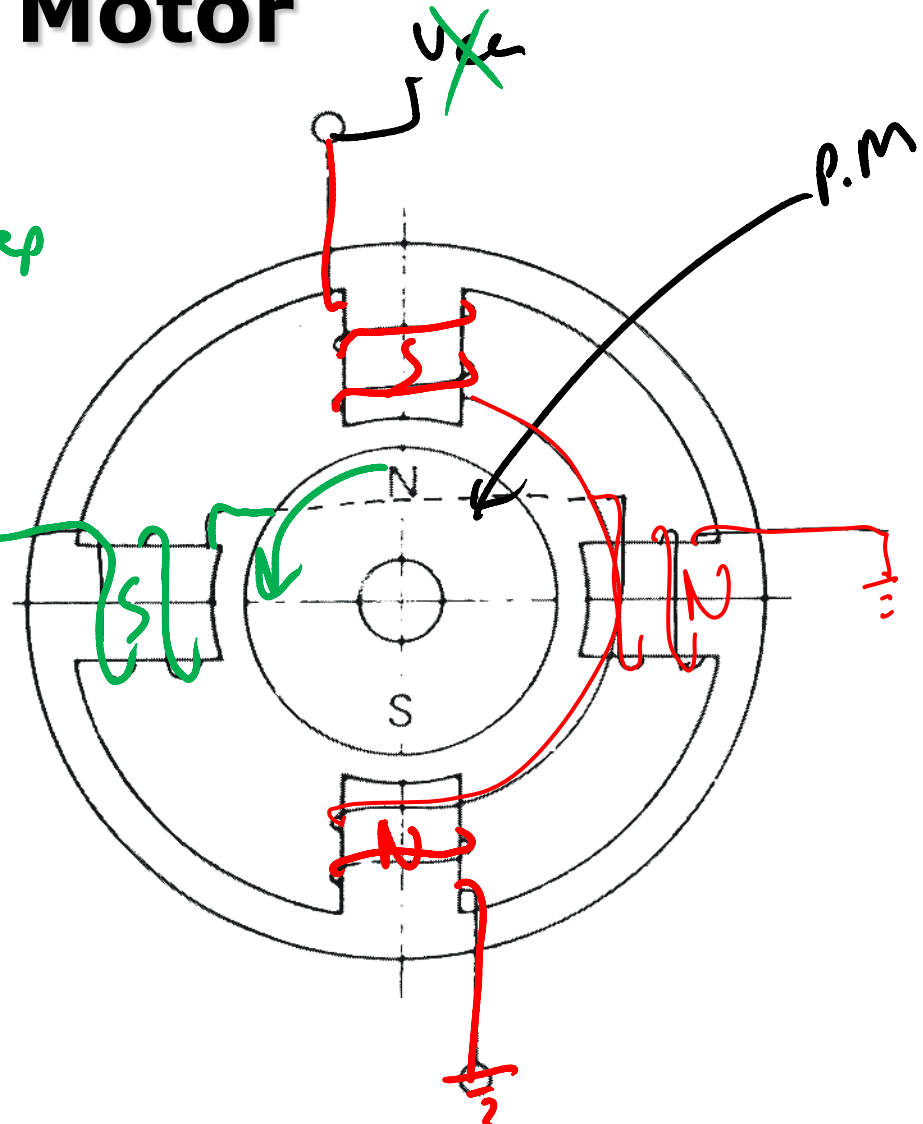- 2 varieties
- 24 steps $15^\circ/\text{step}$
 - 48 steps $2.5^\circ/\text{step}$




PM Stepper Motor Operation

1 → 3
2 → 4
3 → 1
4 → 2

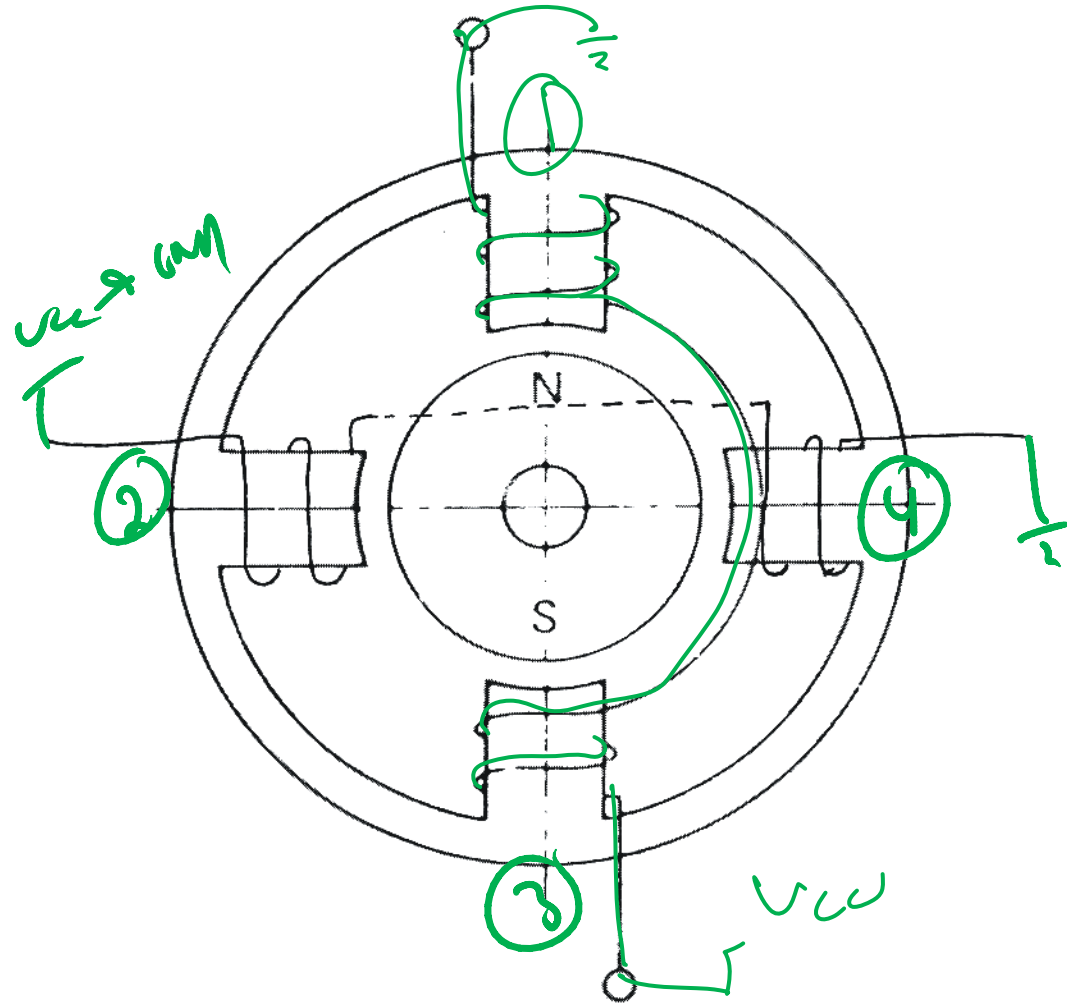


Torque vs. Angular Displacement

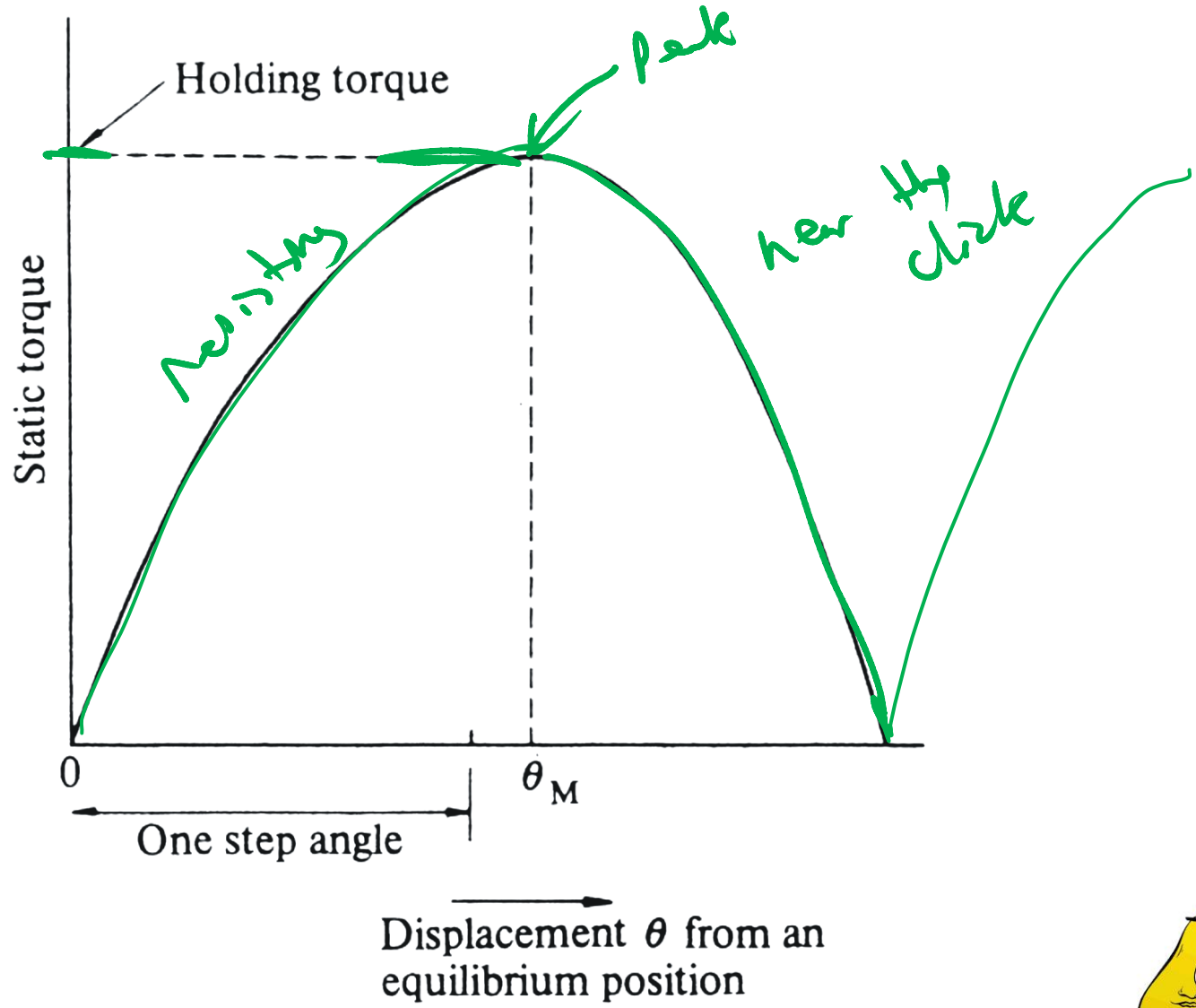

Variable Reluctance (VR) Stepper Motor

PM ADV
 Higher T
 Detent torque

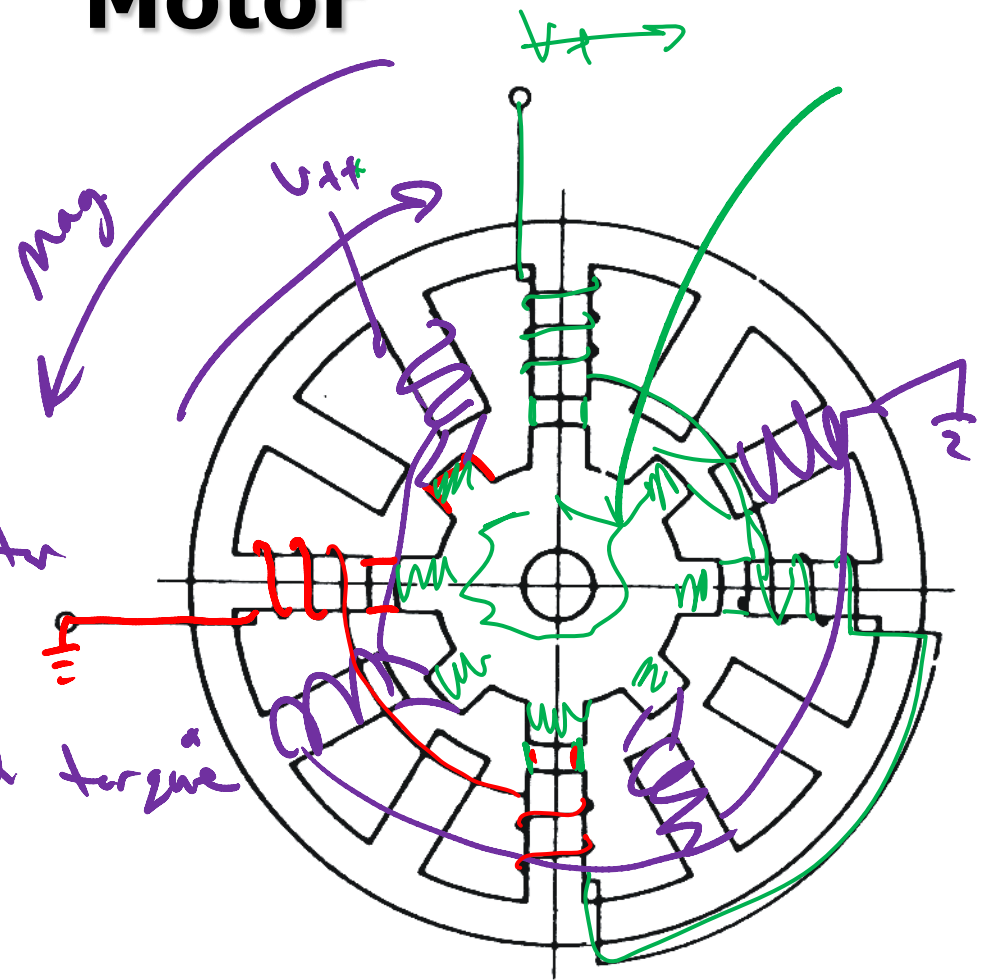VR ADV
 lower inertial motor
 - weight less
 higher top speed
 higher top end torque



Hybrid Stepper Motor


VR

Teeth structure

— Fine resolution

PM

Detent torque

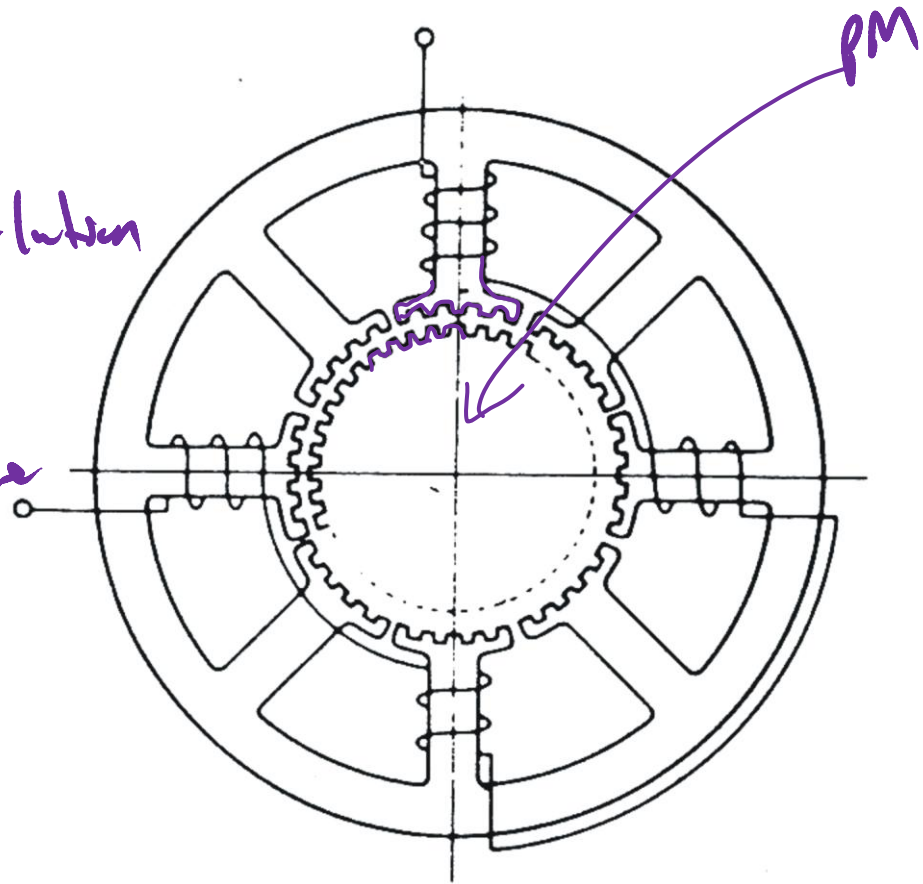

Hybrid Rotor Offset Teeth


Stand Config

2ev steps / rev.

1.8° / step

400 steps / rev

0.9° / step

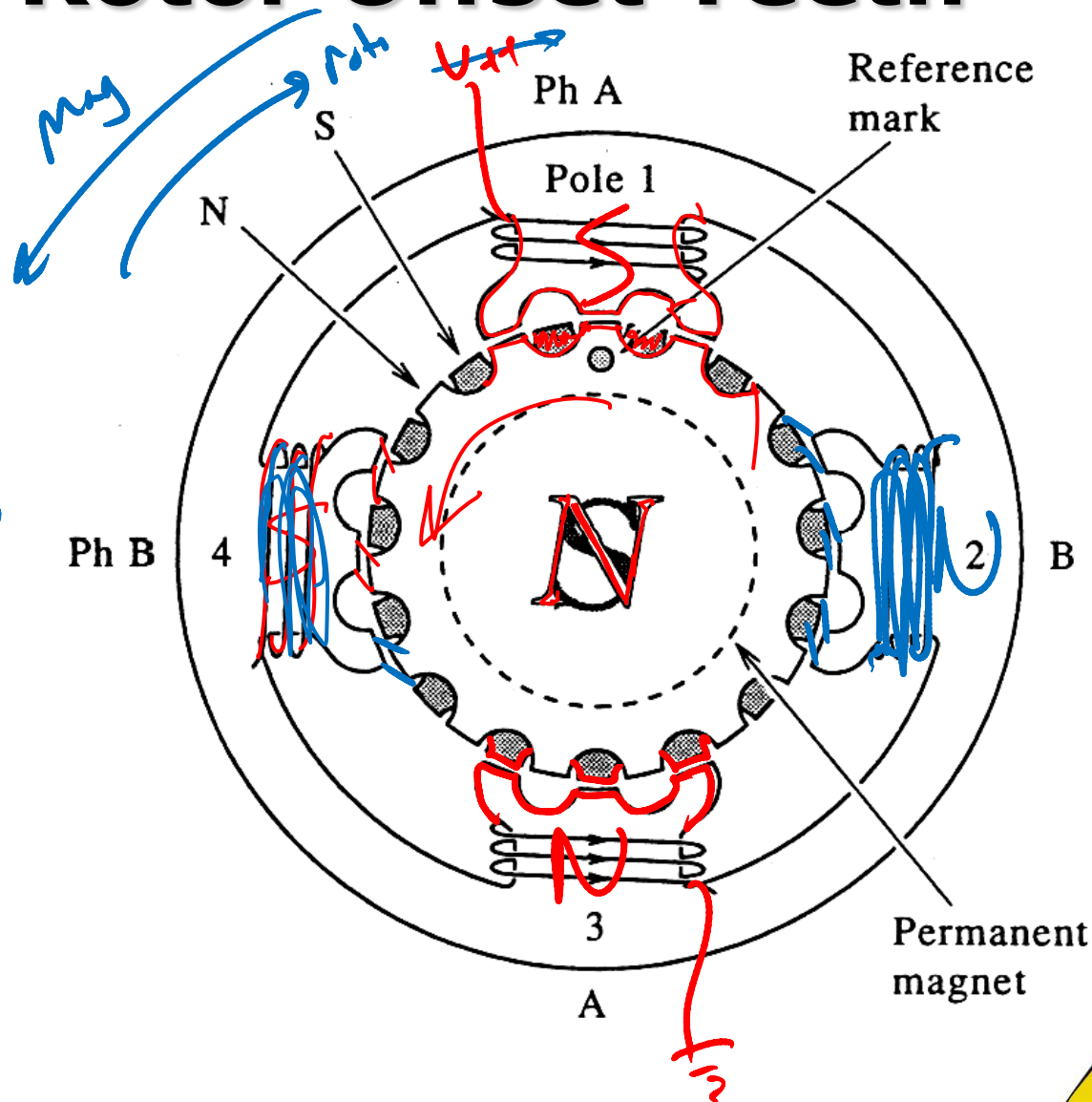

Variations in Output Torque


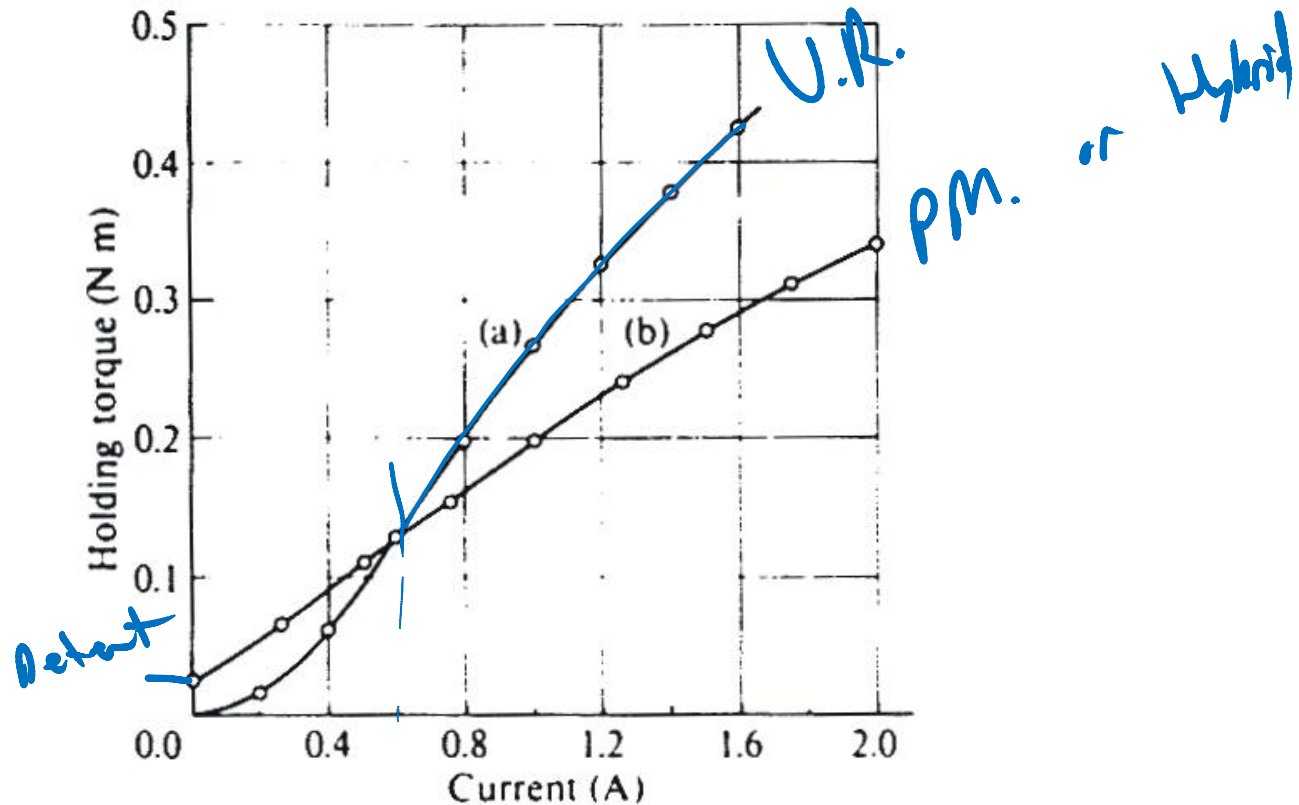


Fig. 2.74. Examples of T/I characteristics: (a) a 1.8° four-phase VR motor; and (b) a 1.8° four-phase hybrid motor. (After Ref. [17].)

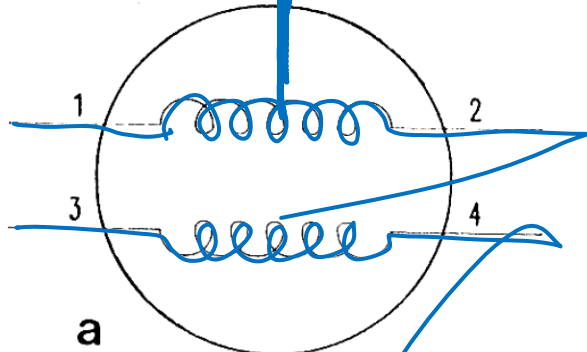


Stepper Motor Wiring

Handwritten diagram showing four vertical lines with horizontal crossbars, labeled 1, 2, 3, 4 below.




a

2-phase

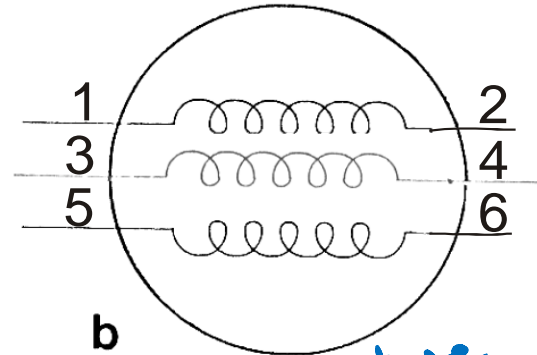


b

3-phase

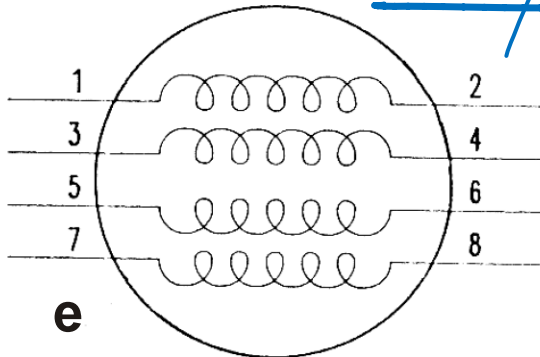


e

4-phase
2 or 8

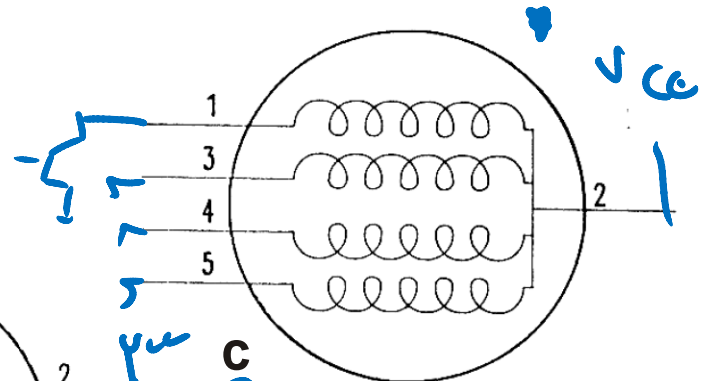

c

2-phase



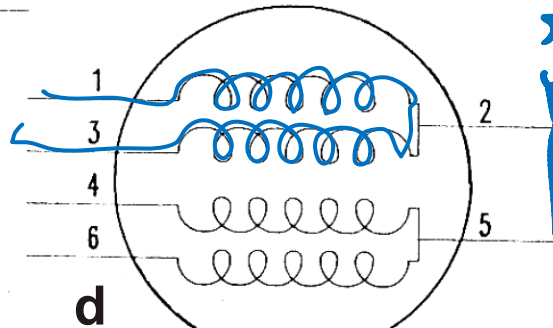


d

2 phase universal winding




Wiring Direction is Important

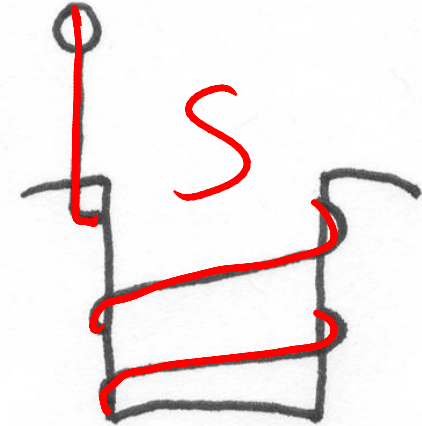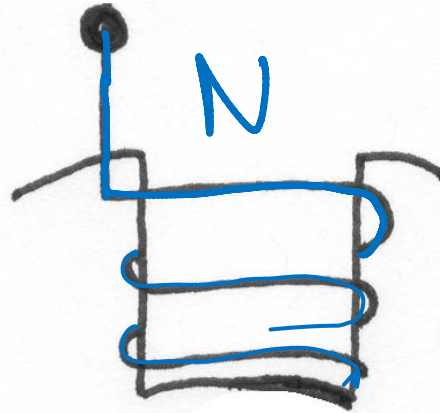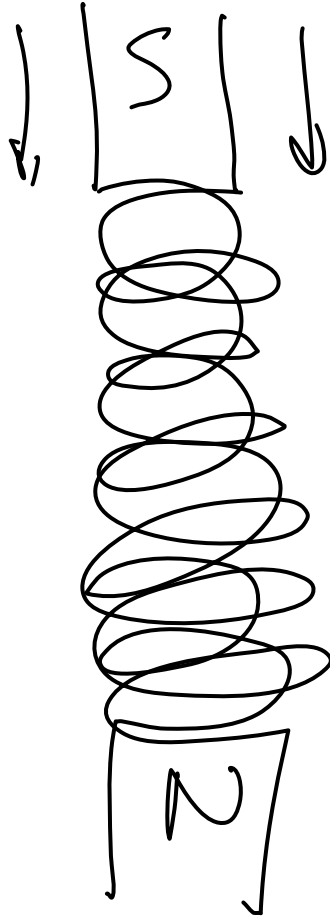


Bifilar wound



2-Phase Universal Wound vs. 4-Phase

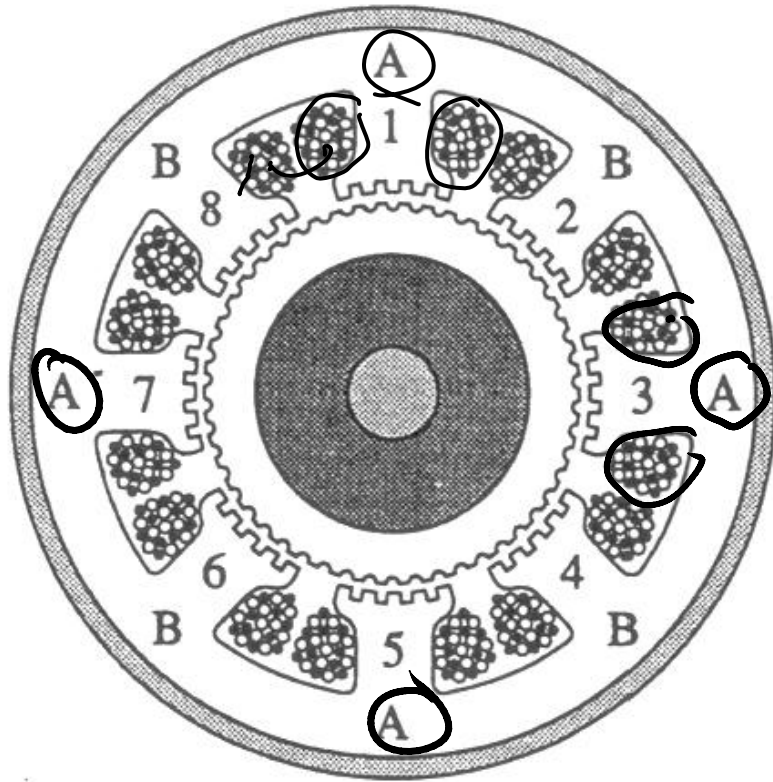



a

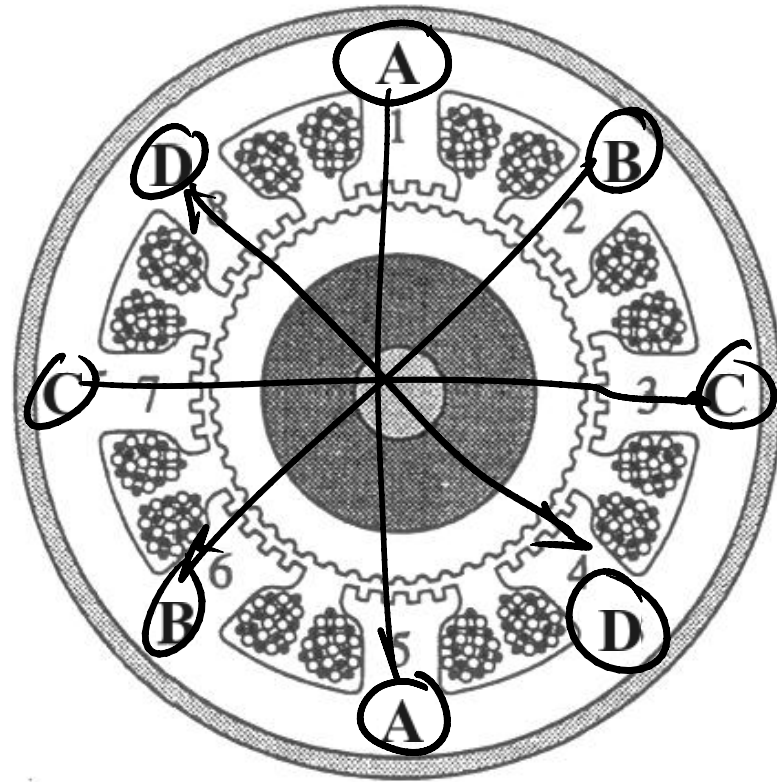


b



Driving Stepper Motors

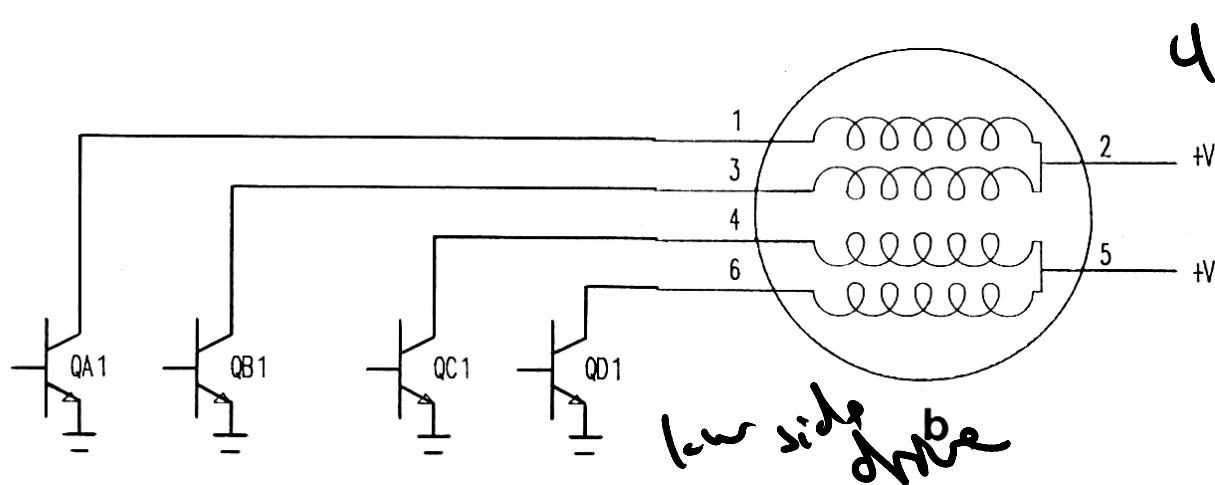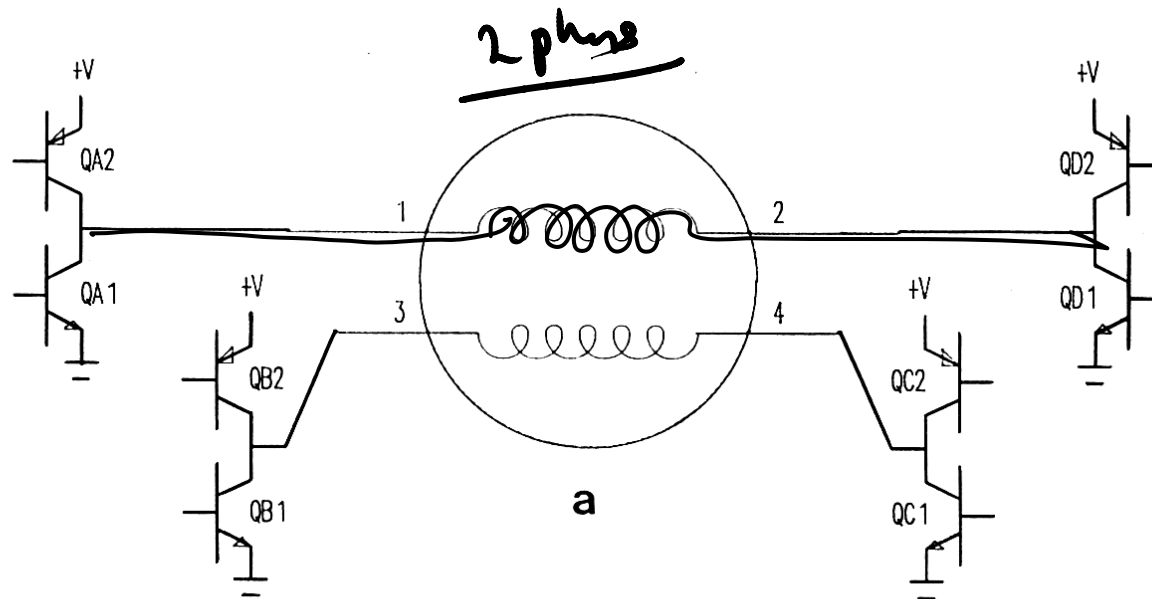

Stepper Sequences: Full Step

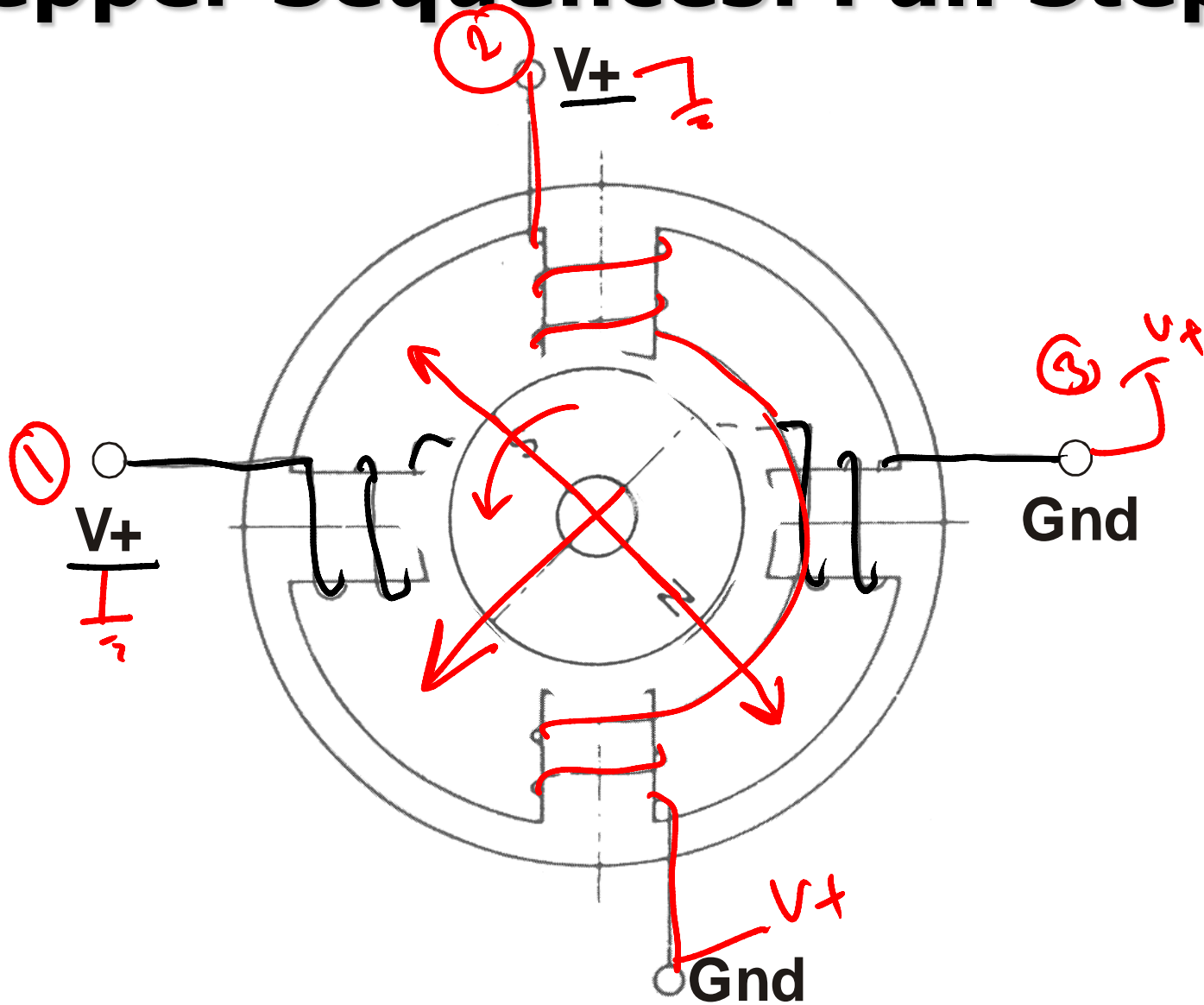


Stepper Sequences: Full Step

BIPOLAR


Step	Q ₁ -Q ₄	Q ₂ -Q ₃	Q ₅ -Q ₈	Q ₆ -Q ₇
1	ON	OFF	ON	OFF
2	ON	OFF	OFF	ON
3	OFF	ON	OFF	ON
4	OFF	ON	ON	OFF
1	ON	OFF	ON	OFF

CW ROTATION (indicated by a downward arrow on the left)

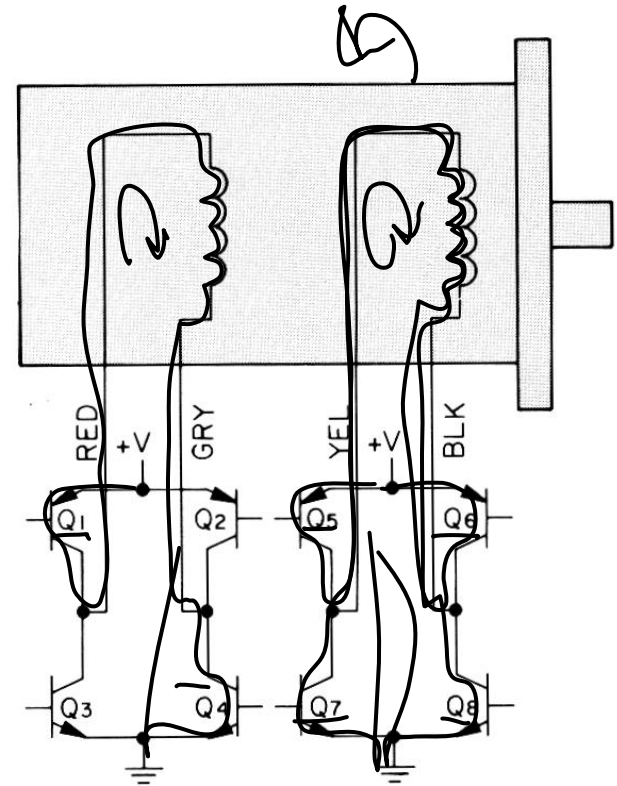
CCW ROTATION (indicated by an upward arrow on the right)



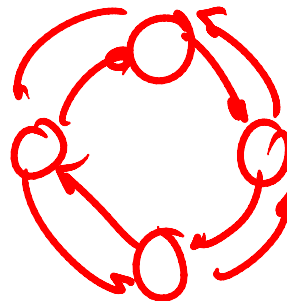- Summary
- Best T
 - Most Power used
 - ~~Best~~ Least Fine resolution




Stepper Sequences: Wave Drive

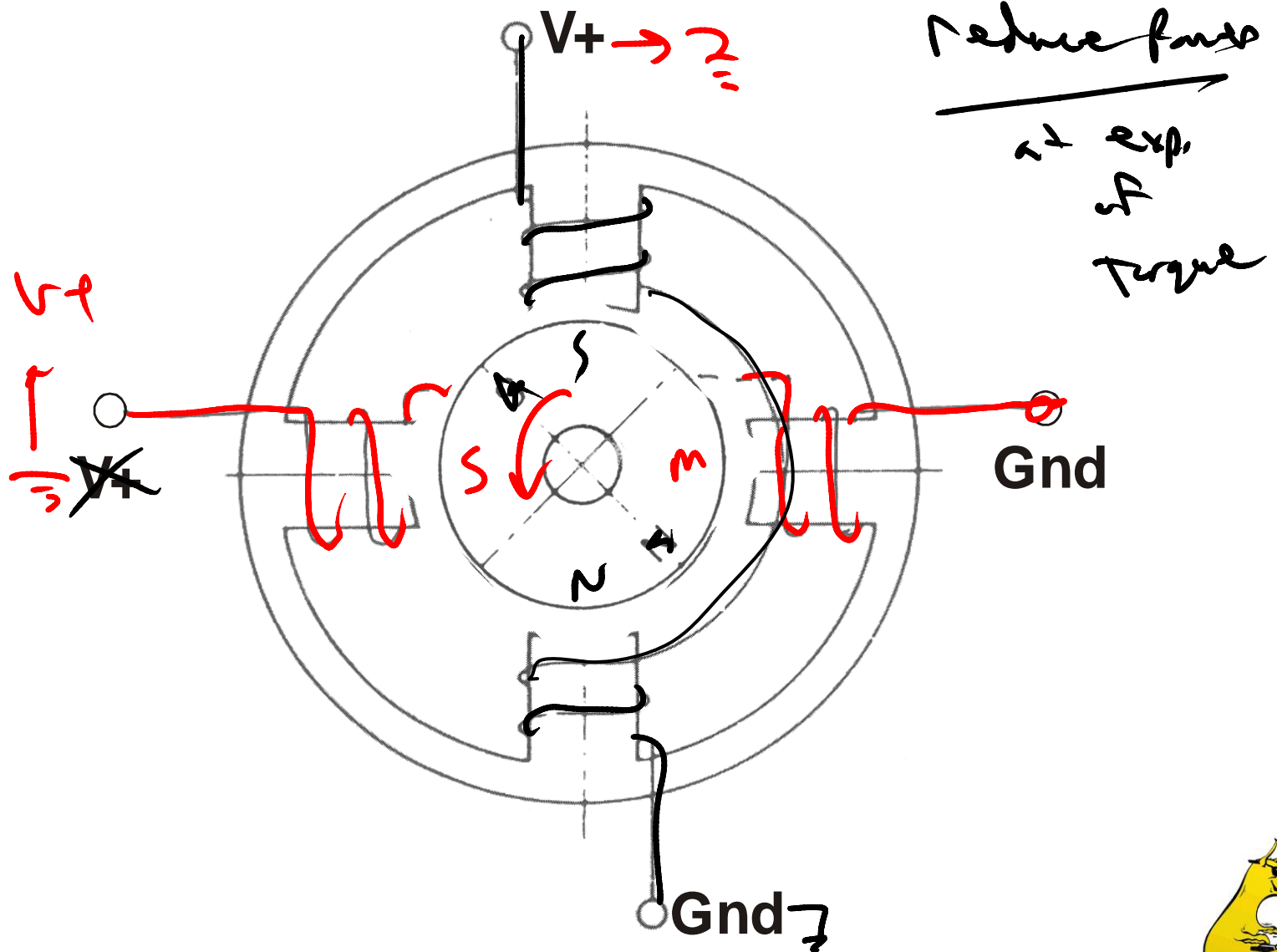

Stepper Sequences: Wave Drive


	Step	Q ₁ -Q ₄	Q ₂ -Q ₃	Q ₅ -Q ₈	Q ₆ -Q ₇
CW ROTATION	1	ON	OFF	OFF	OFF
	2	OFF	OFF	OFF	ON
	3	OFF	ON	OFF	OFF
	4	OFF	OFF	ON	OFF
	1	ON	OFF	OFF	OFF

CCW ROTATION

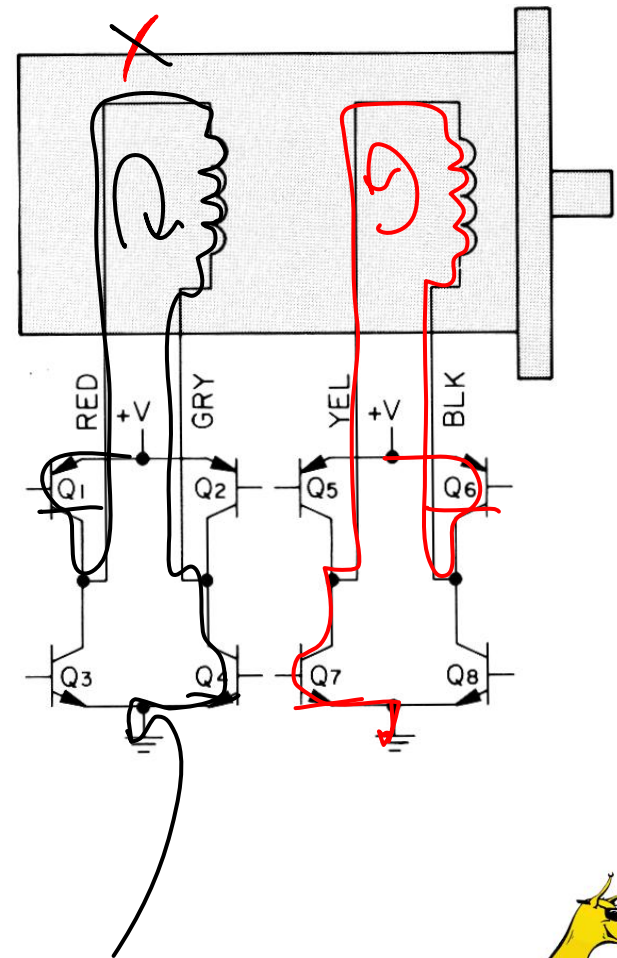



Stepper Sequences: Half-Step

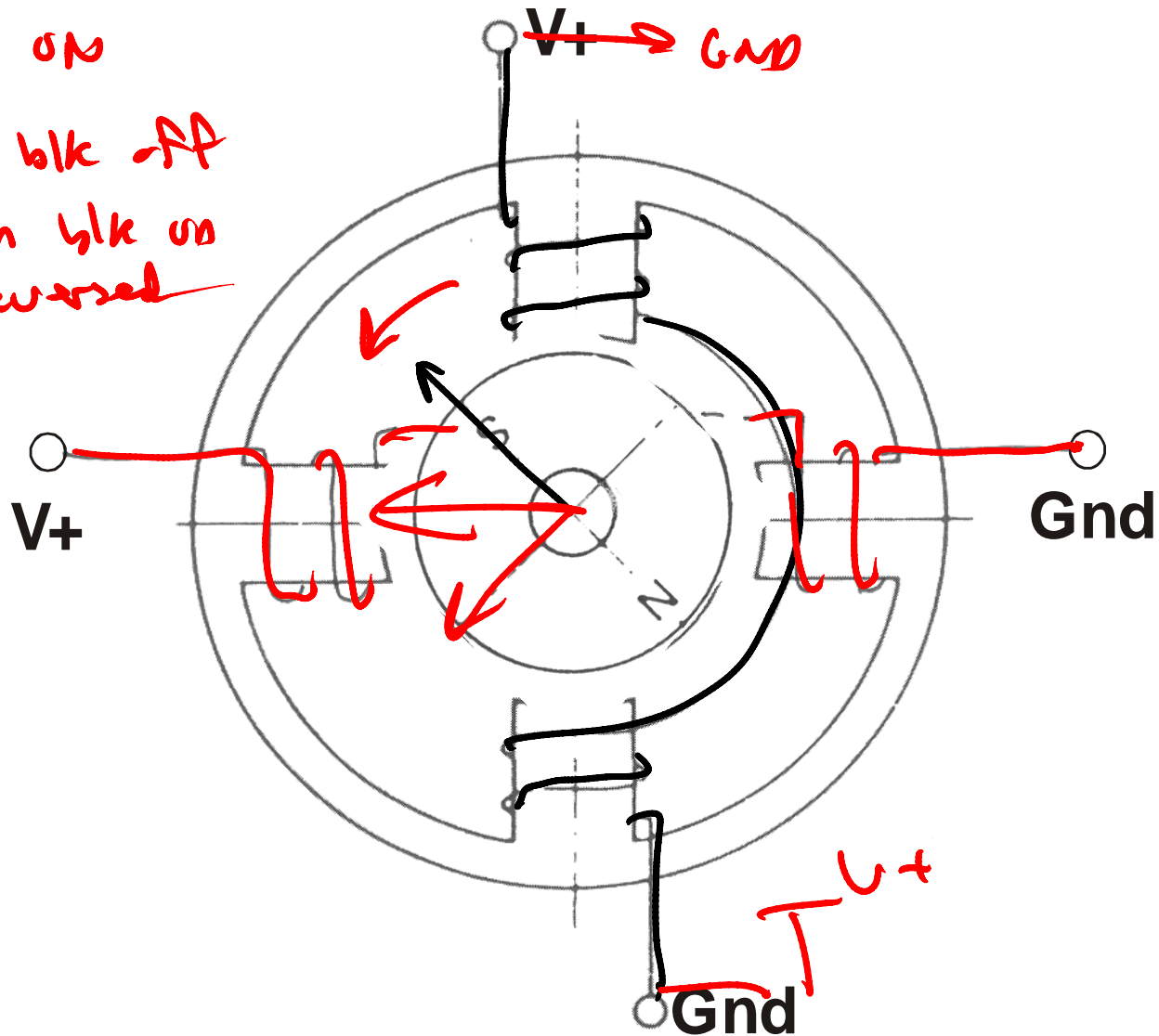
- ① Both on
- ② turn blk off
- ③ turn blk on reversed




Stepper Sequences: Half-Step Drive

Step	Q ₁ -Q ₄	Q ₂ -Q ₃	Q ₅ -Q ₈	Q ₆ -Q ₇
1	ON	OFF	ON	OFF
2	ON	OFF	OFF	OFF
3	ON	OFF	OFF	ON
4	OFF	OFF	OFF	ON
5	OFF	ON	OFF	ON
6	OFF	ON	OFF	OFF
7	OFF	ON	ON	OFF
8	OFF	OFF	ON	OFF
	ON	OFF	ON	OFF


CW ROTATION
CCW ROTATION

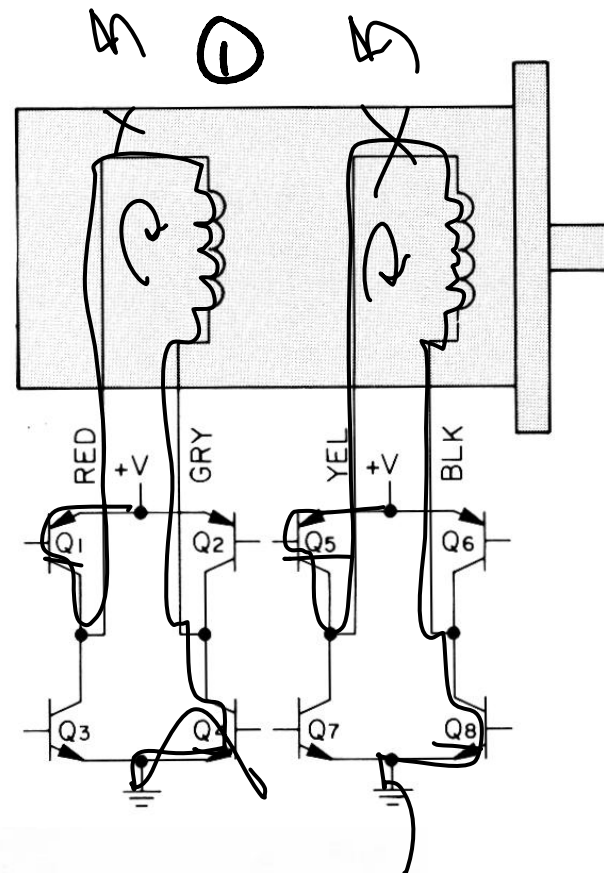


Generating the Drive

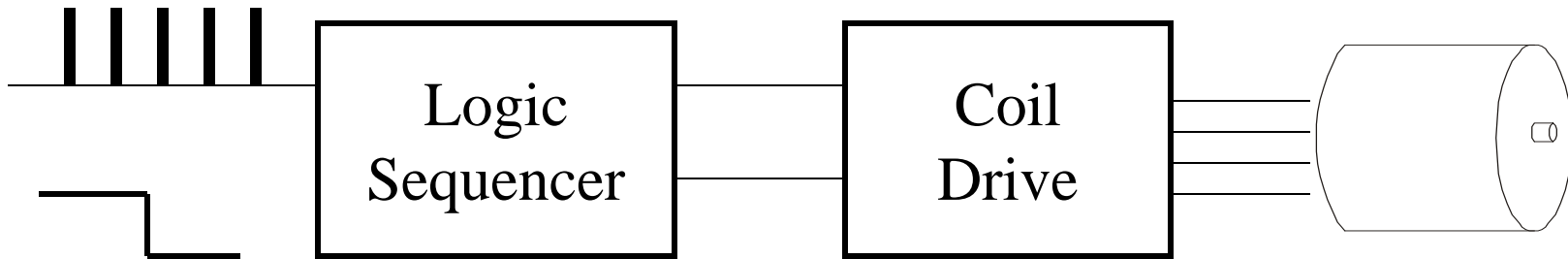

in lab → *MC*
HC12


H-bridge
A3949 ①

② *Combining Control & Drive*
A3922 - stepper driver




③ *L297 stepper motor ctrl.* & *L298 Anal. H-bridge driver*



Stepping Dynamics

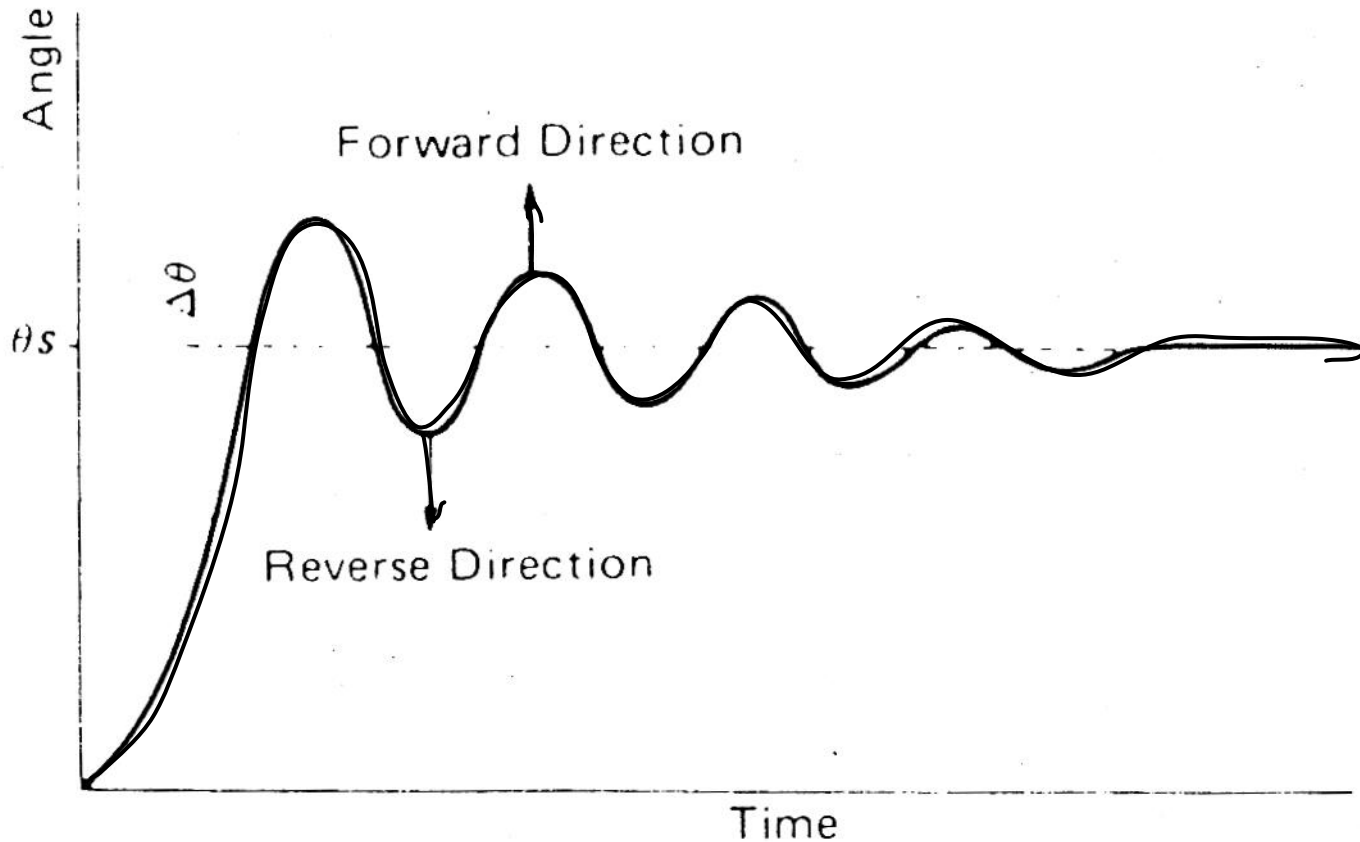

Load Effects on Step Dynamics

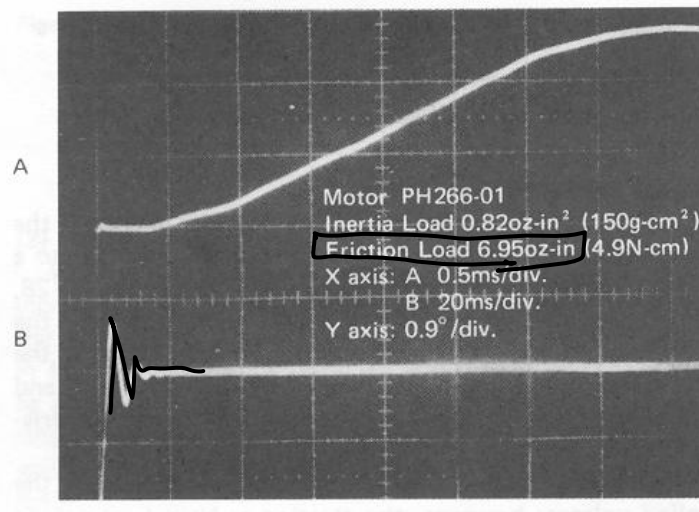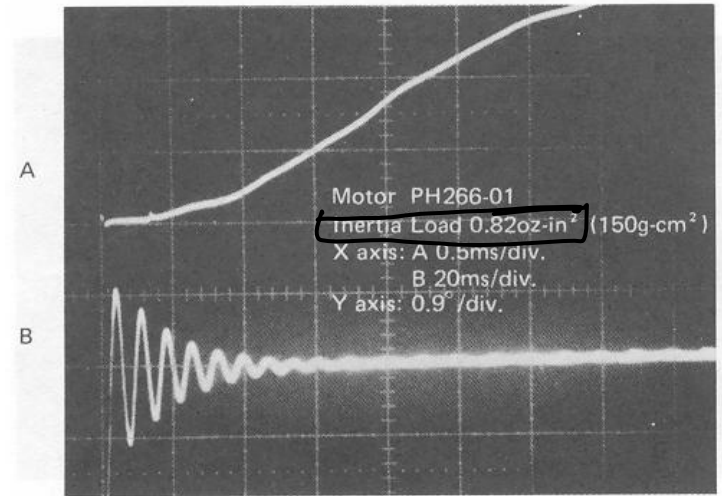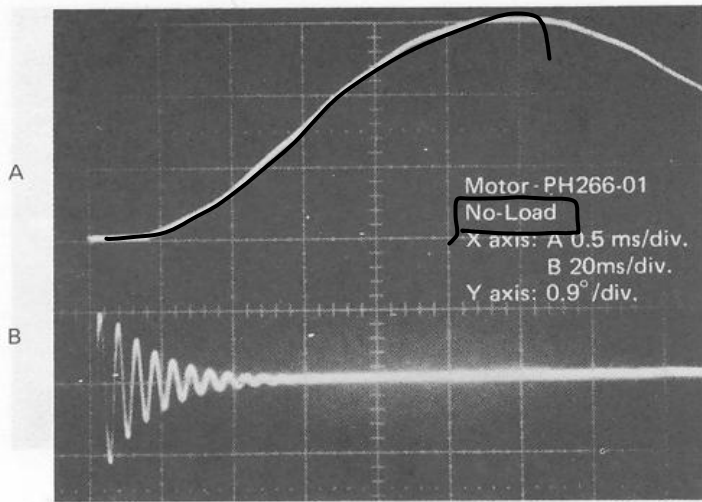

Drive Effects on Step Dynamics



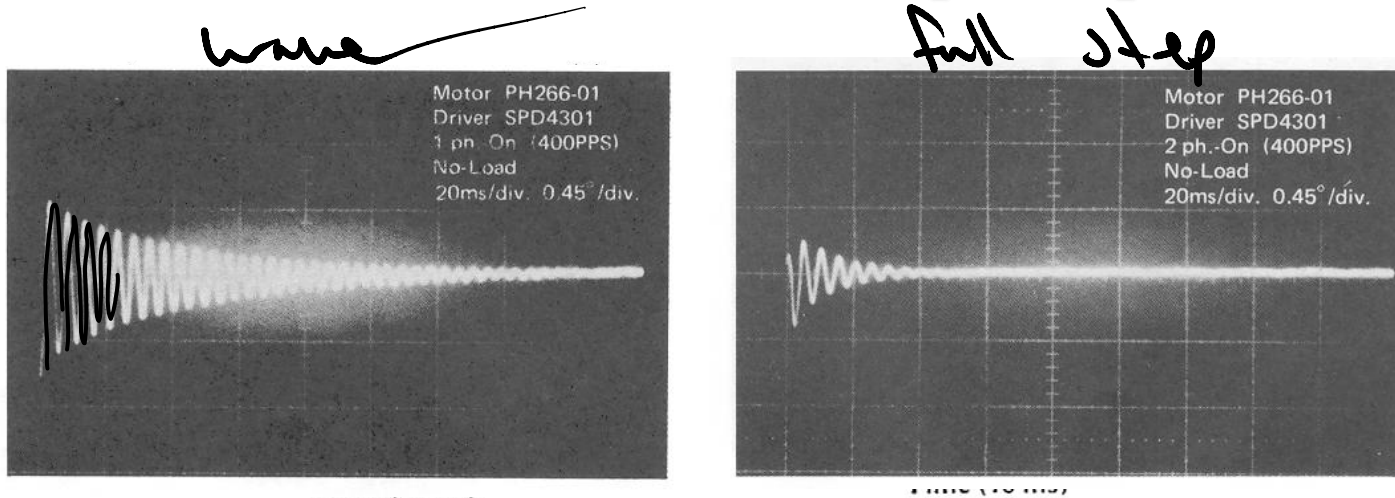



Fig. 2.55. Difference in single-step response between the single-phase (a) and two-phase (b) excitation.

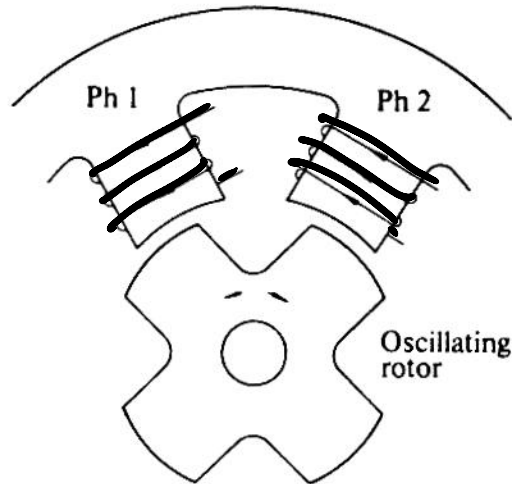


Stepper Motor Performance Curves

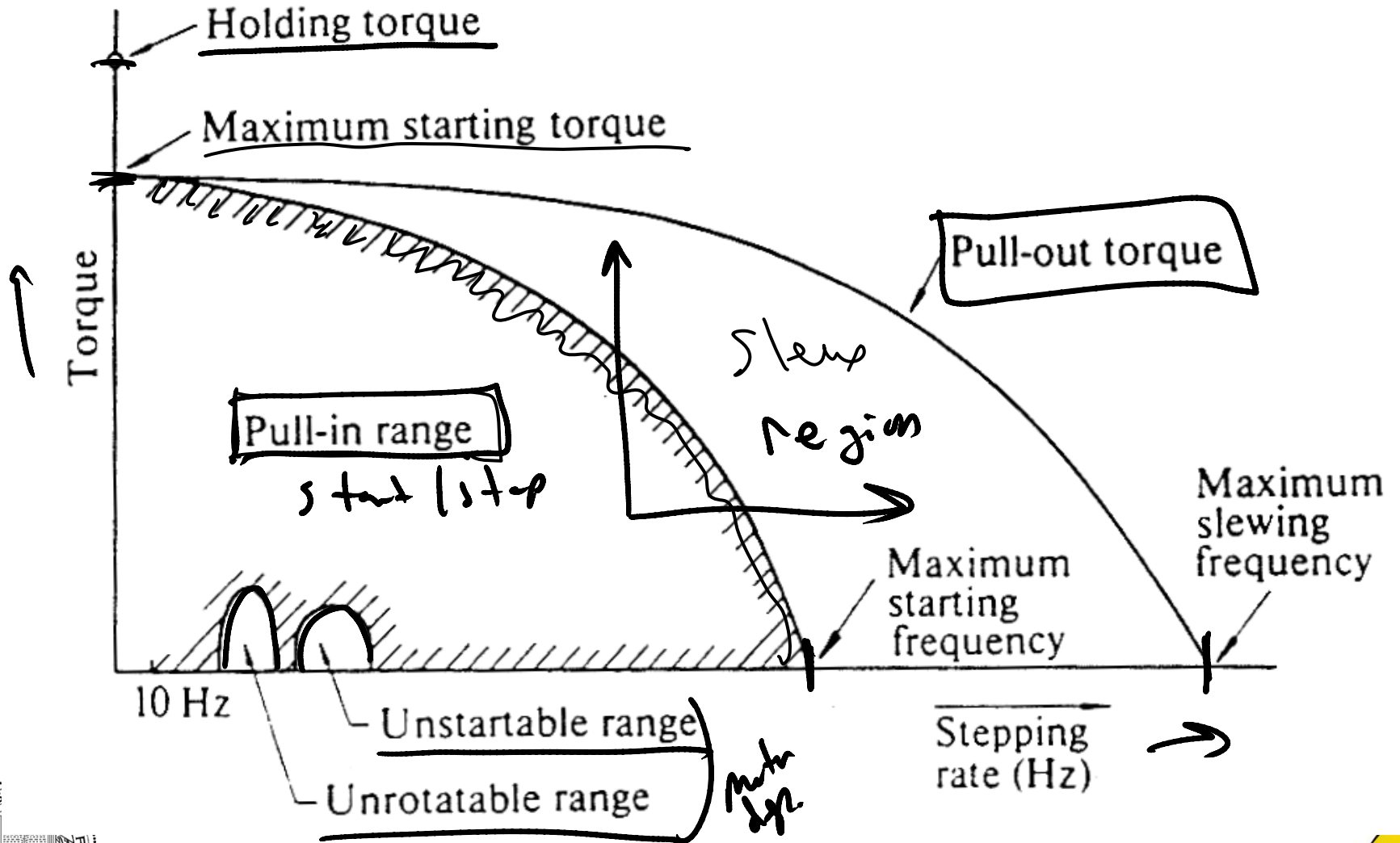


Stepper Motor Current Dynamics

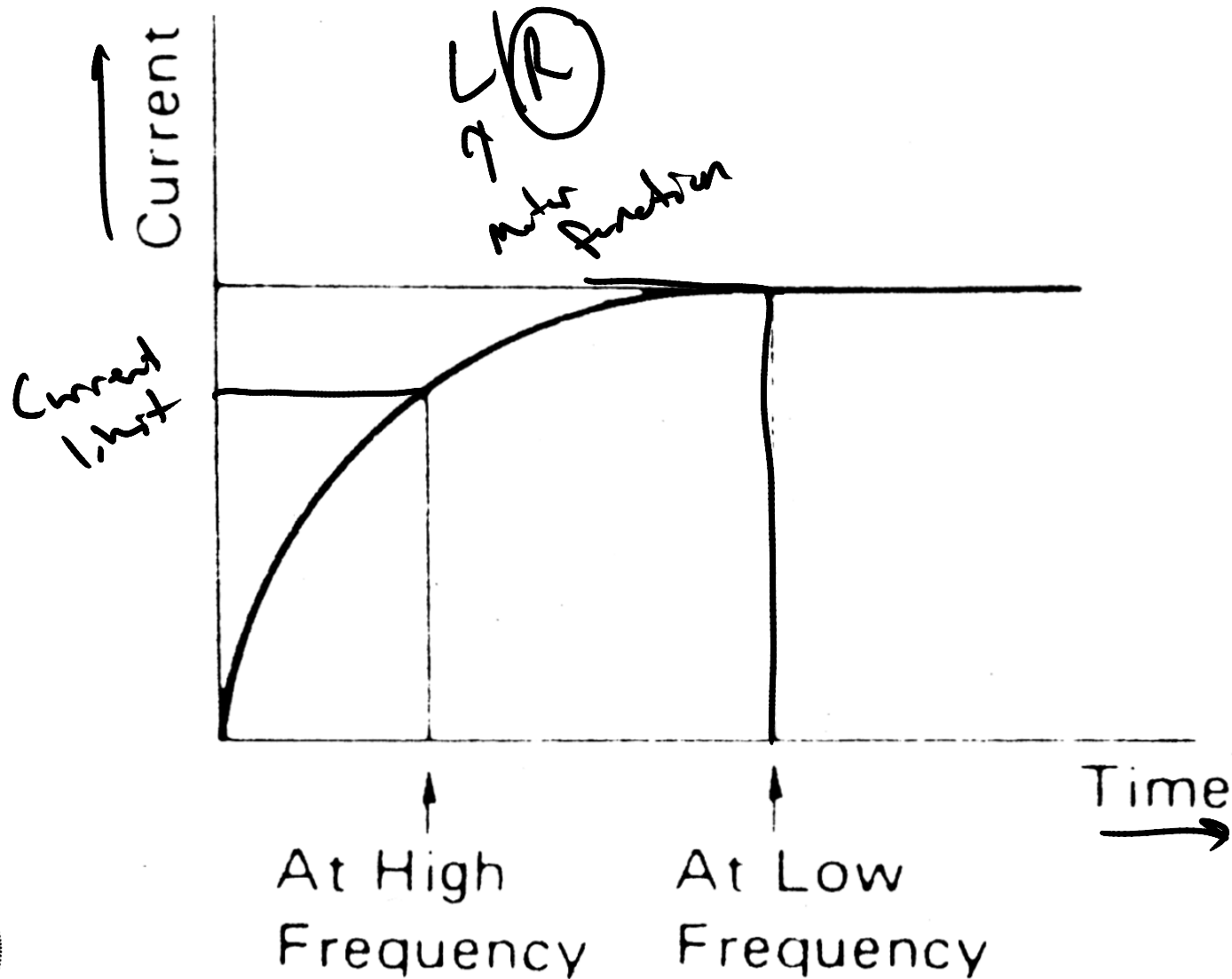


L/nR Drive (1.3)

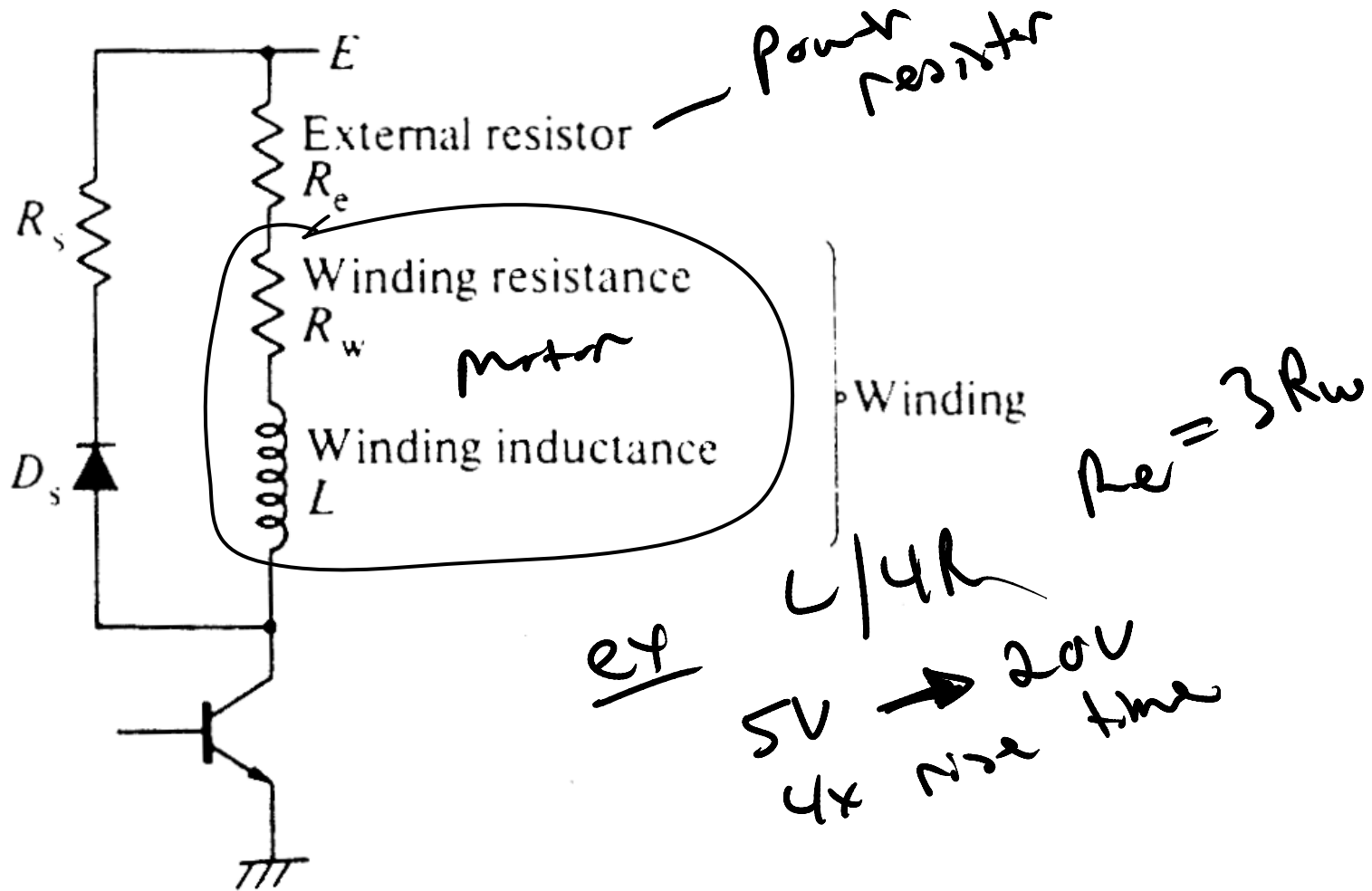


L/nR Drive (2.3)

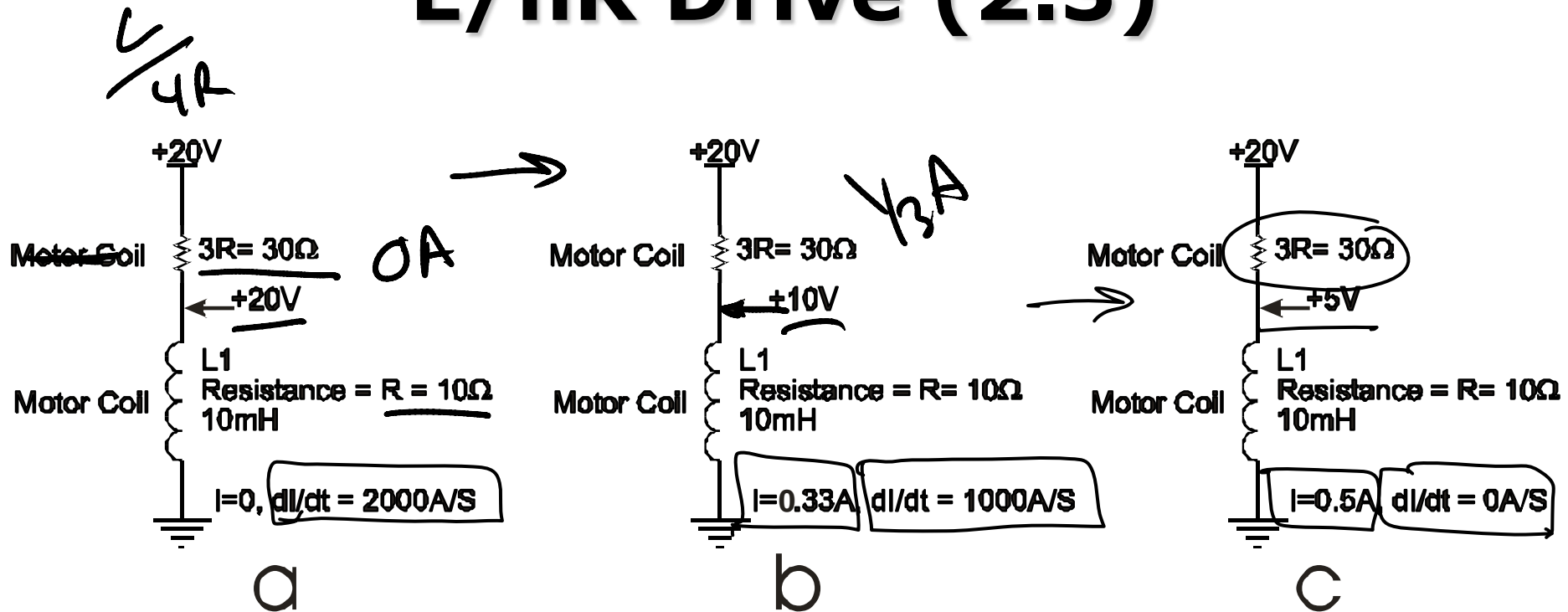

$5V \rightarrow 20V$

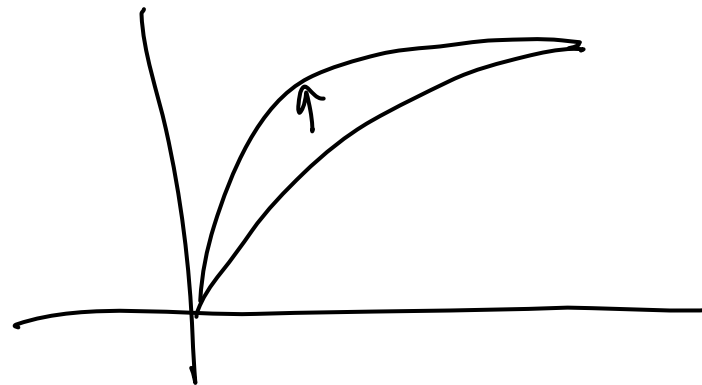



L/nR Drive (3.3)

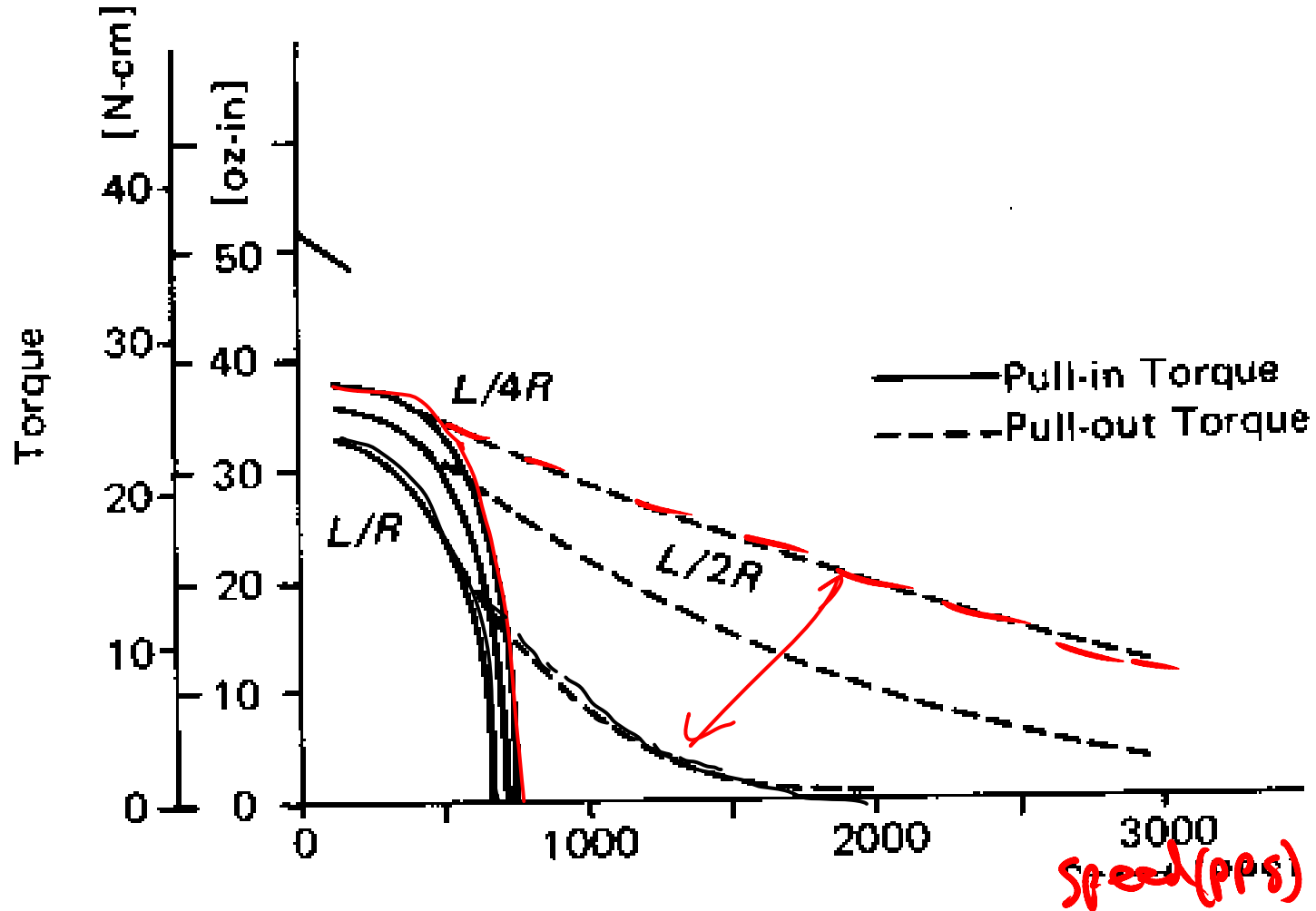

2-Level Drive

PTB
works well



Cons
2 volages

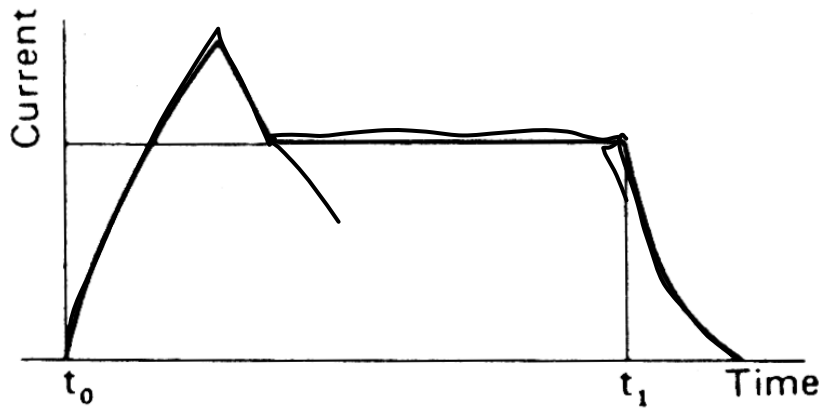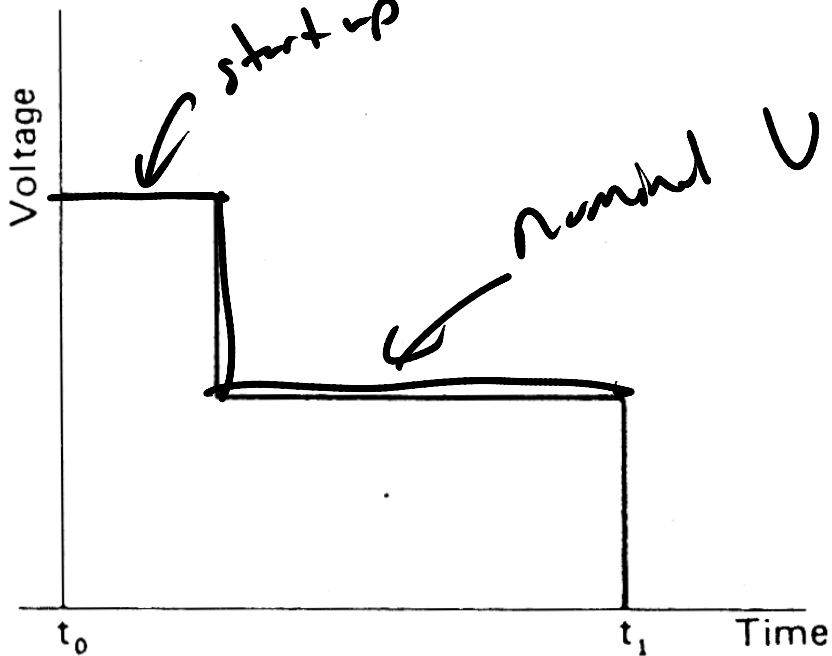

Chopper Drive


Peak & Hold

Con
Notoriously high
EMI

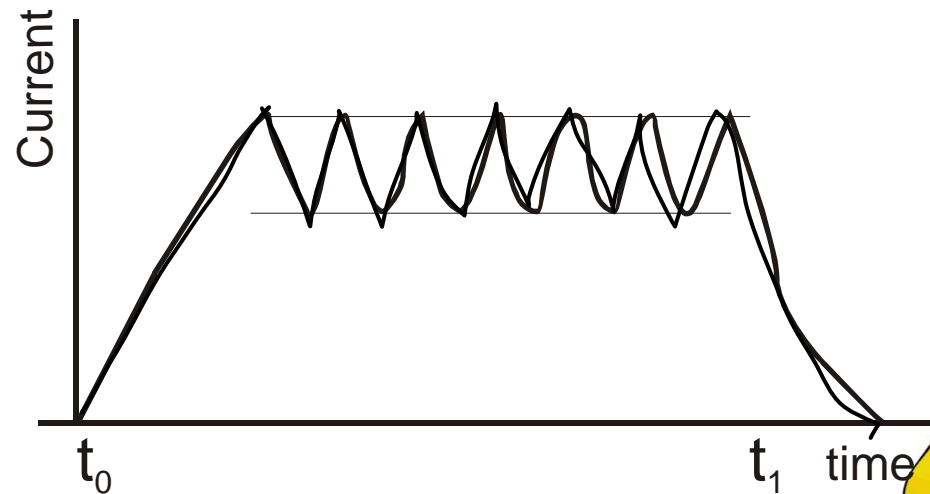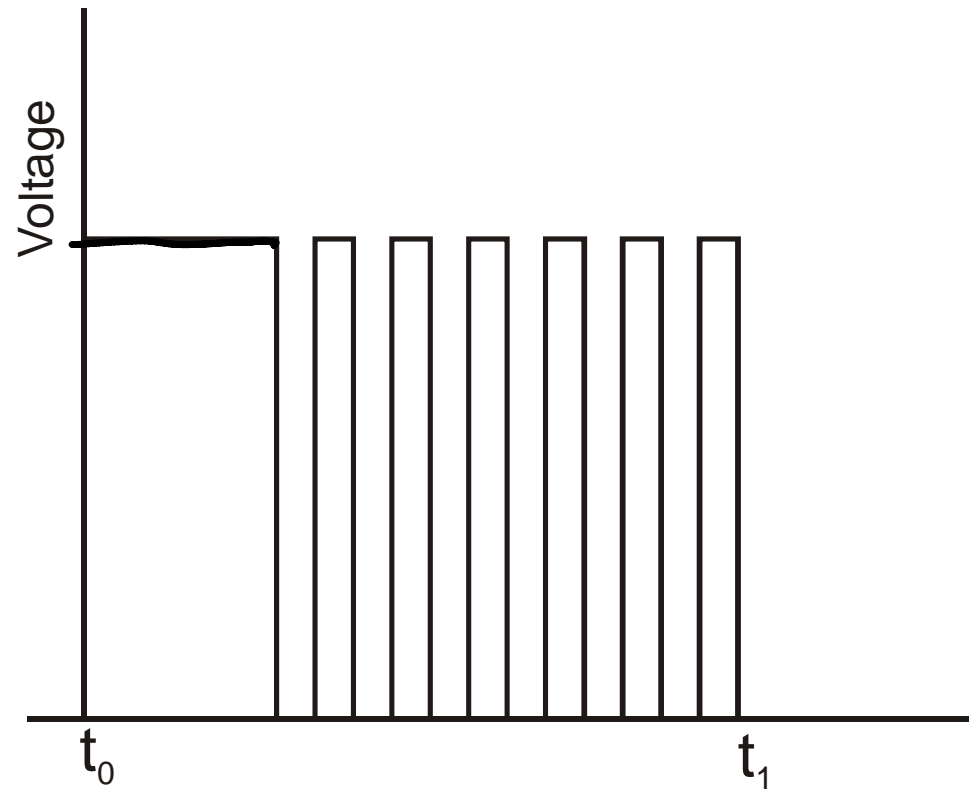


Diode Snubber for H-bridge

Single Power Supply

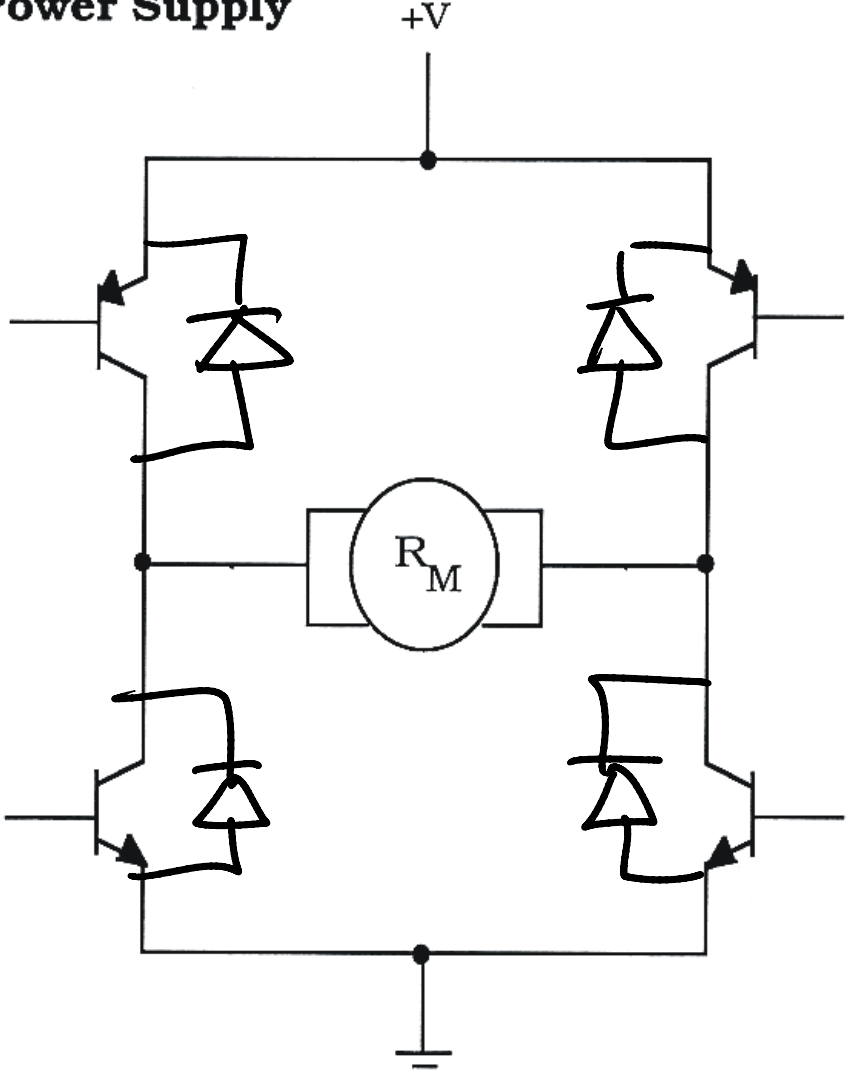


Zener Snubber for H-bridge


Single Power Supply

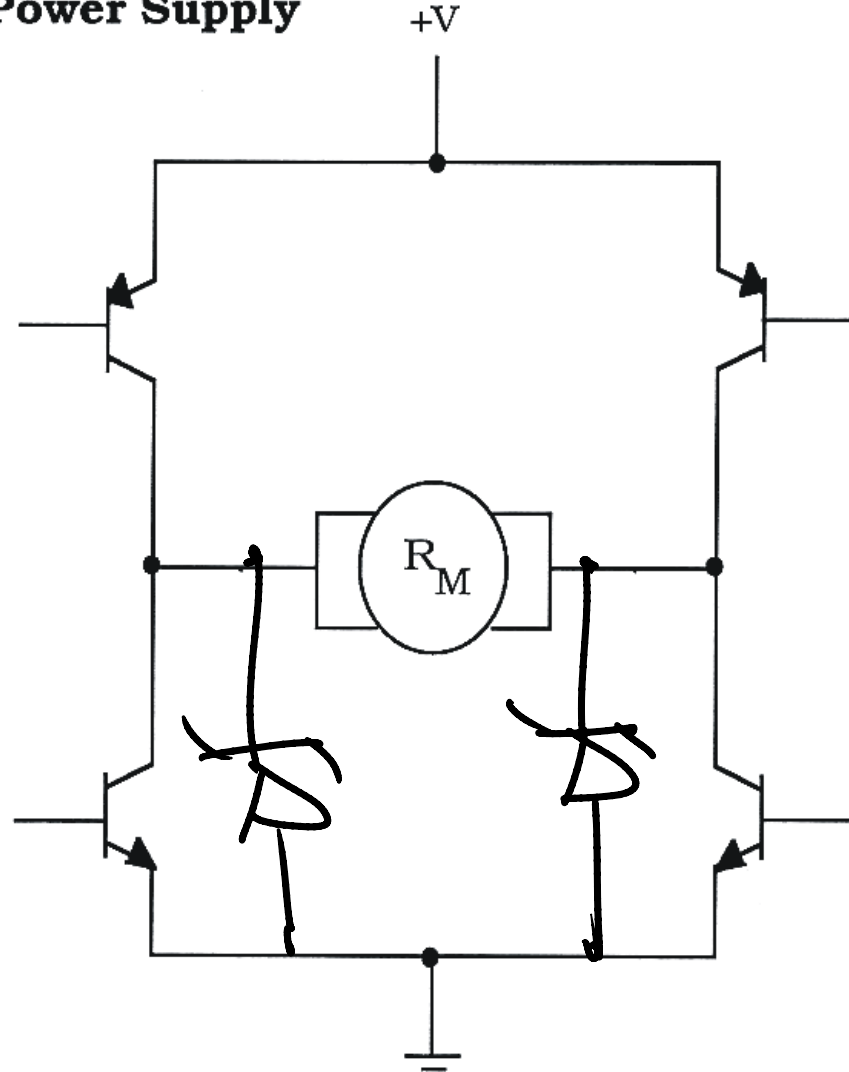


Other Snubbing Alternatives (1.3)

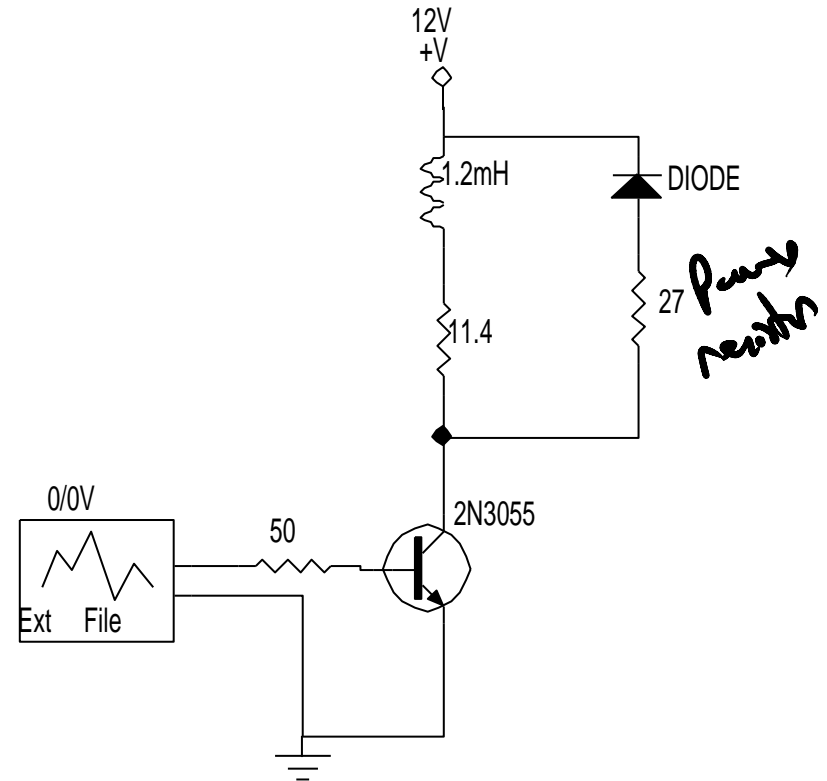


Other Snubbing Alternatives (2.3)

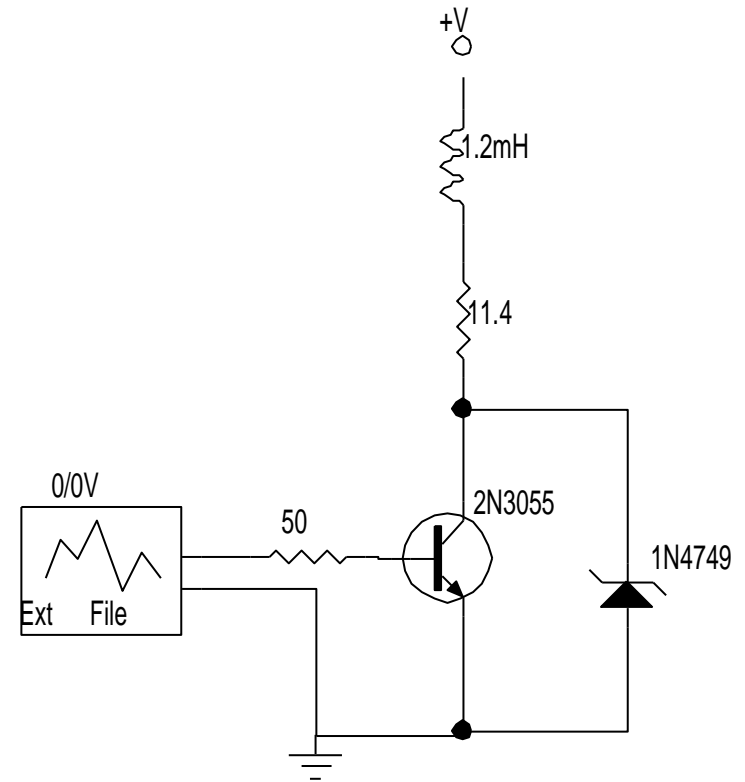

Other Snubbing Alternatives (3.3)

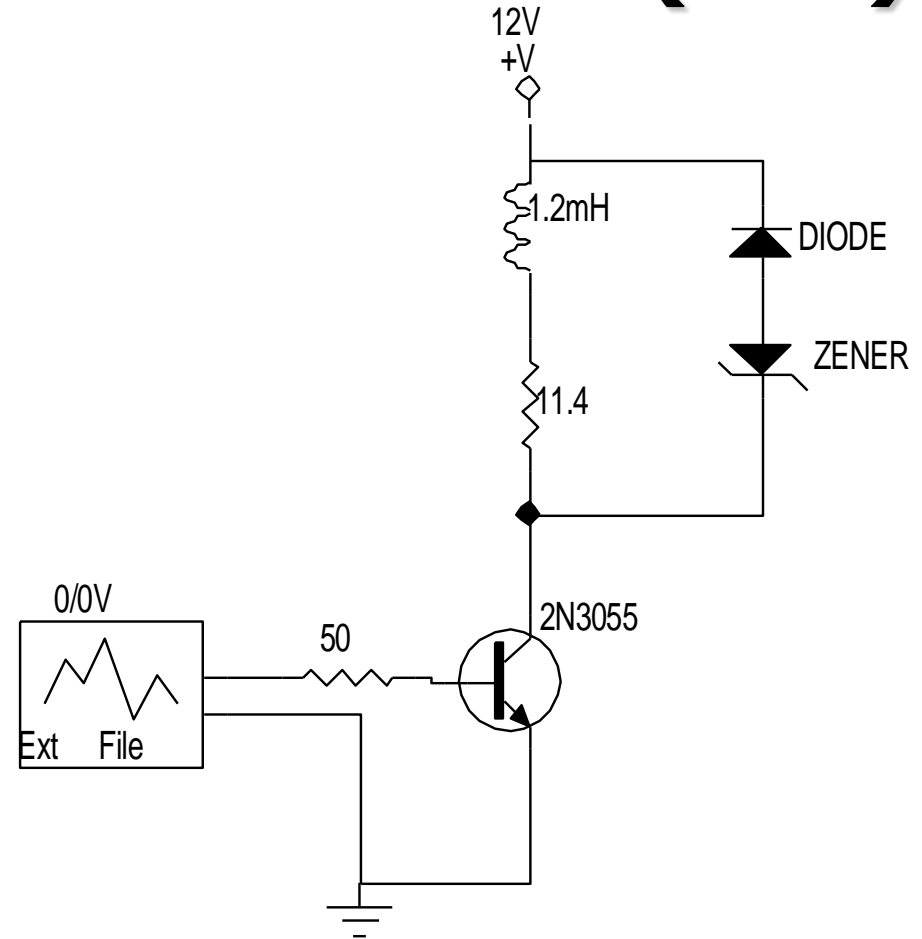

Snubbing Techniques Compared (1.2)

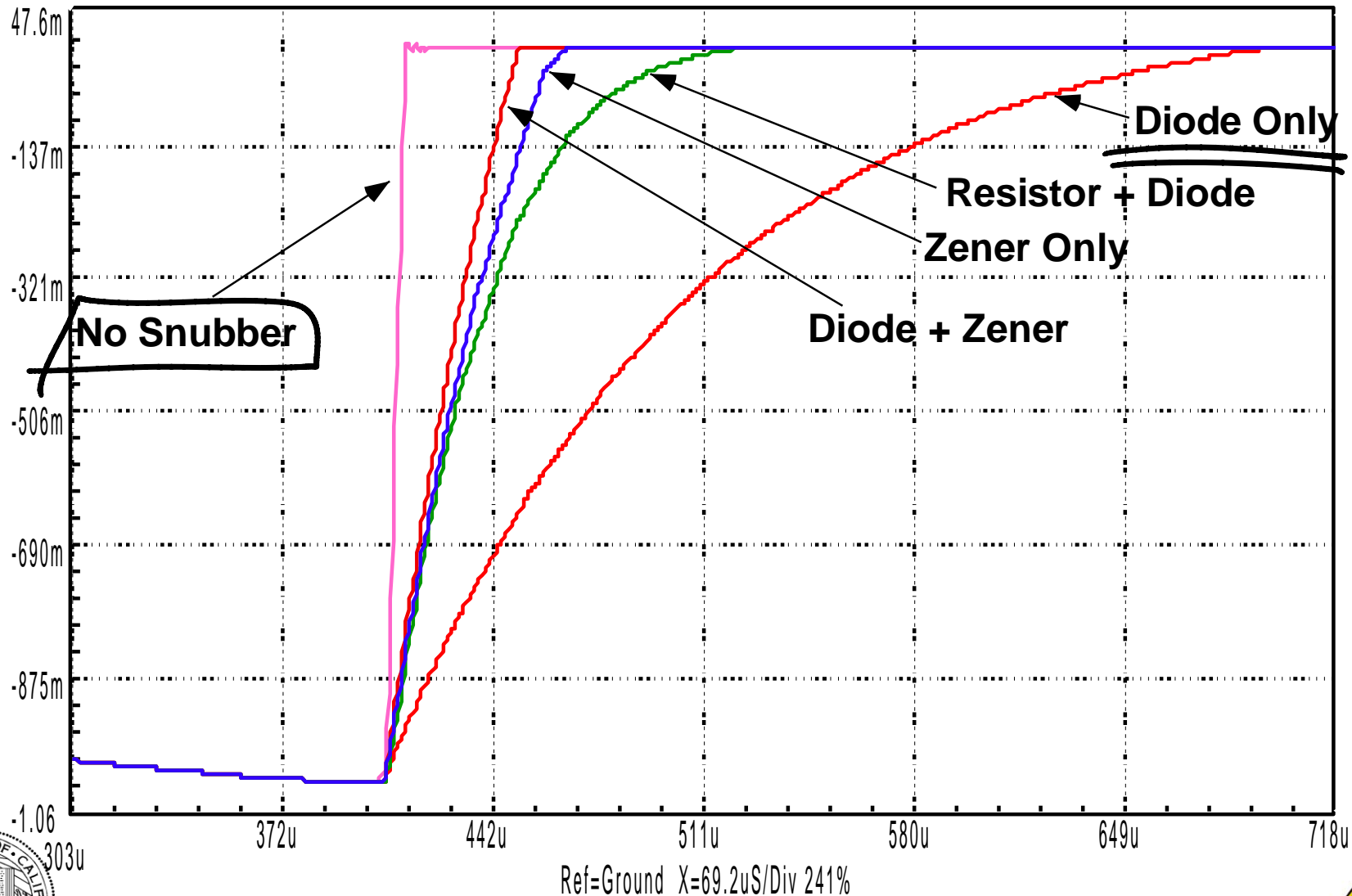

Snubbing Techniques Compared (2.2)



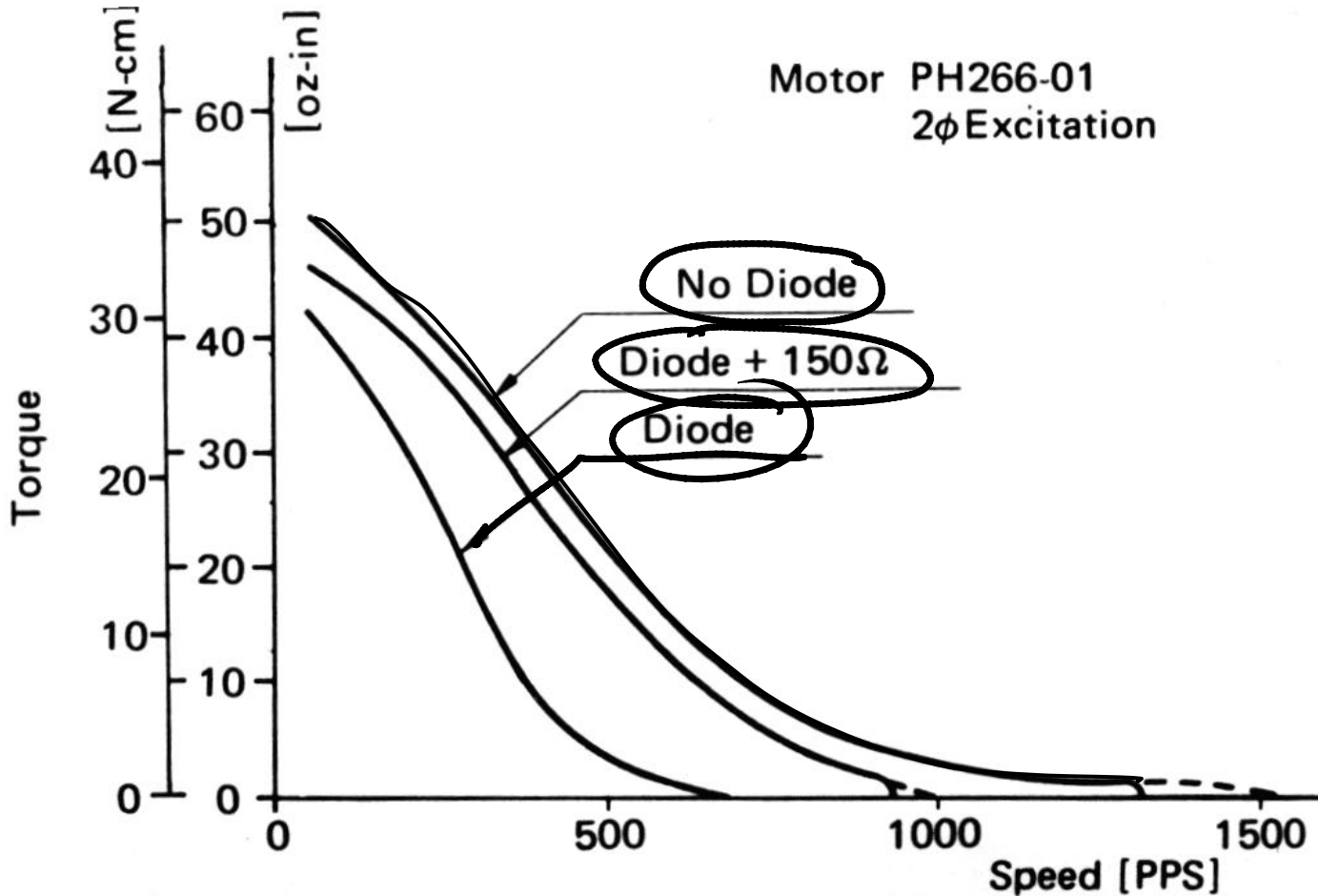


Figure 6-5 Torque-speed curves of Oriental Motor PH266-01 stepping motor with no diode, diode +150 ohm resistor and diode suppression circuits

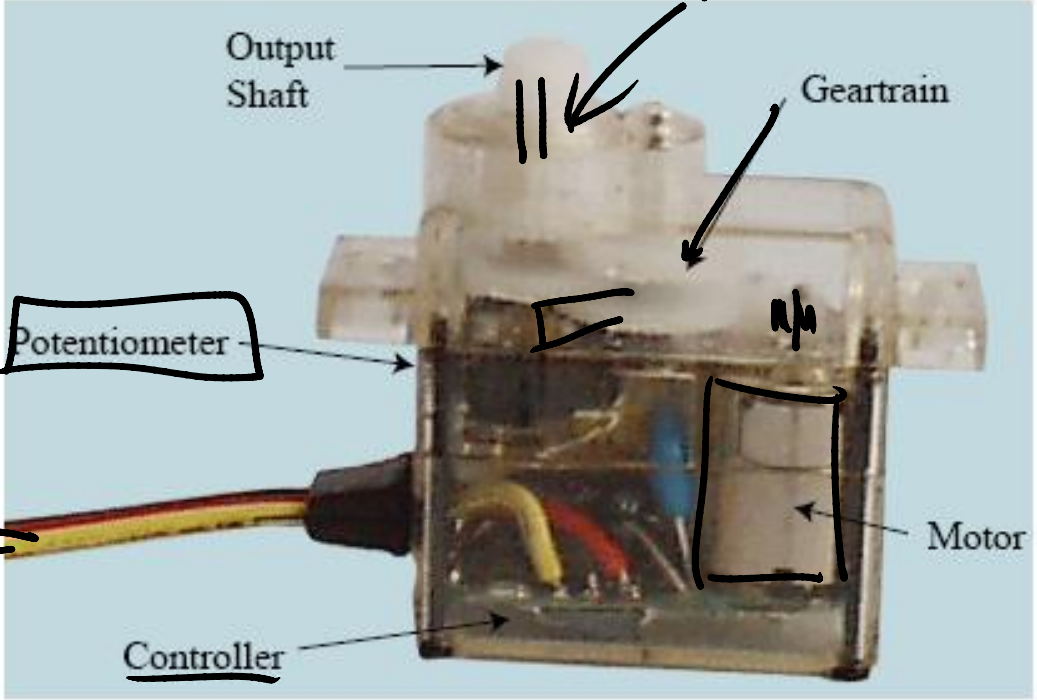


R/C Servos

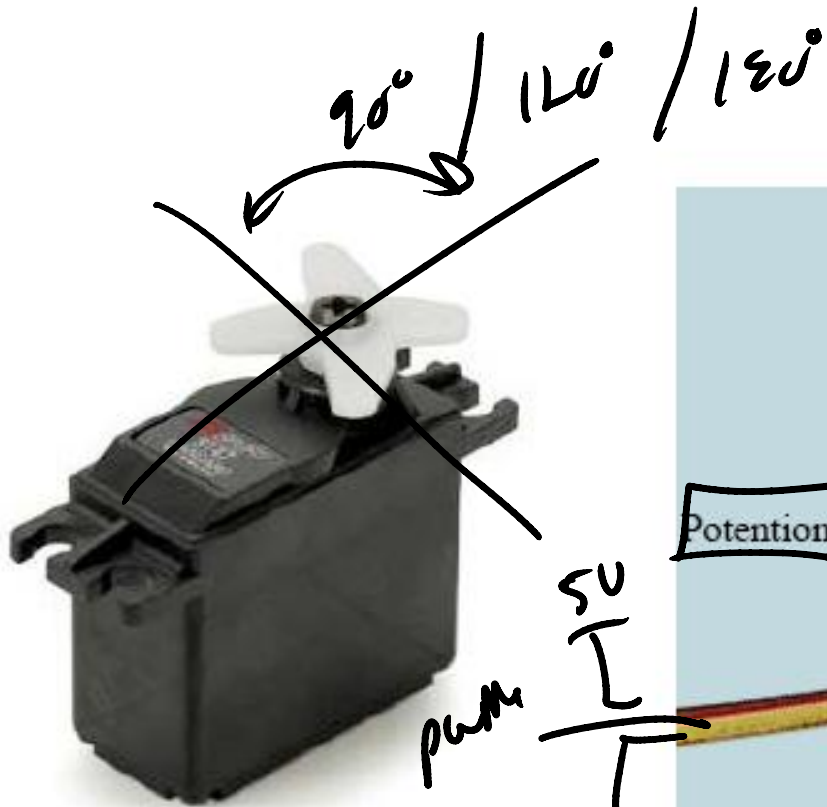

www.forallx.com #13



R/C Servos

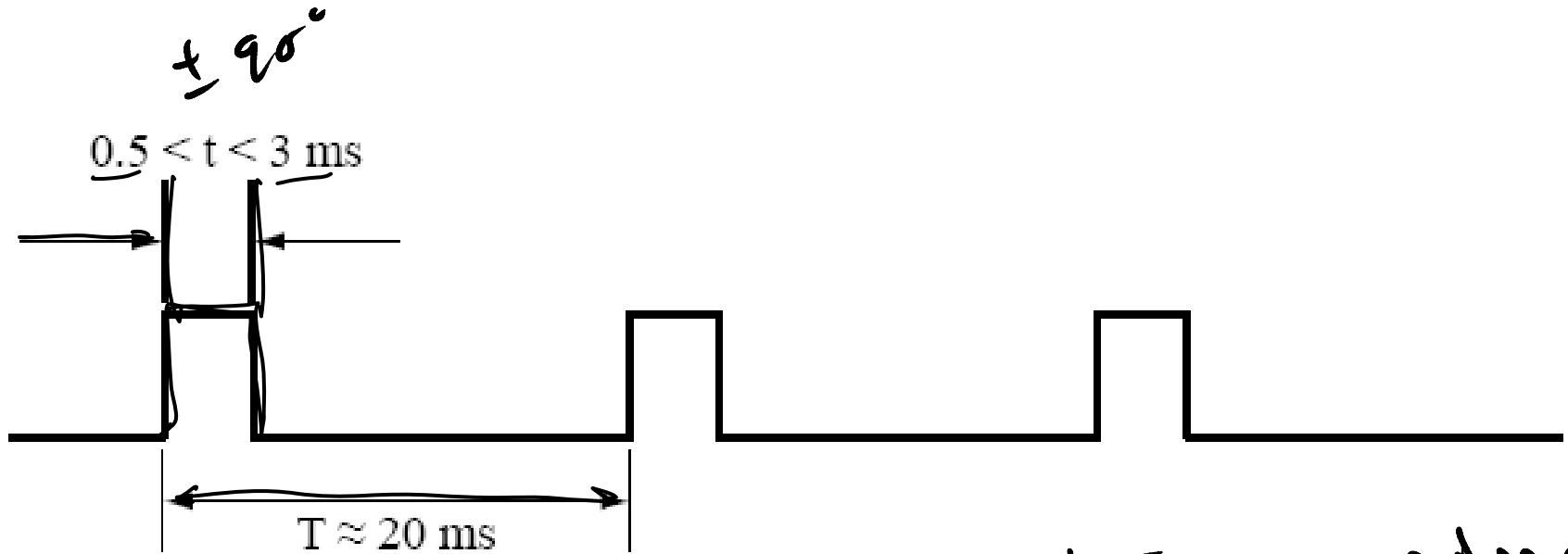

50 Hz

1.5 ms - center 0°
1 ms - -60°
2 ms - $+60^\circ$



Questions?

