 


INPUTS: TWO n BIT BINARY NUMBERS

$[a_{n-1} \dots a_0]_2$, $[b_{n-1} \dots b_0]_2$

OUTPUT: 1 IF EACH $a_i = b_i$ ($0 \leq i \leq n-1$),
0 OTHERWISE



How many Rows AND columns would the TRUTH TABLE FOR THIS CIRCUIT HAVE ?

ANSWER: 2^{2n} Rows
 $2n+1$ Columns


HOW MANY TRANSISTORS ARE NEEDED TO BUILD THIS CIRCUIT? ANSWER: $10n - 2$

OUR NEXT TASK IS TO CONSTRUCT A CIRCUIT WHICH ADDS TWO n BIT BINARY NUMBERS. THIS CIRCUIT IS CALLED AN n -BIT FULL ADDER.

EX.

$$\begin{array}{r}
 101101100 \\
 10010110 \\
 \hline
 10110011 \\
 101001001
 \end{array}
 \quad n=8$$

WE START BY BUILDING A 1-BIT ADDER WHICH TAKES THREE INPUTS (TWO BITS AND A CARRY) AND RETURNS TWO OUTPUTS (SUM AND NEW CARRY)

 

THESE 1-BIT ADDERS CAN THEN BE COMBINED TO FORM A PHYSICAL IMPLEMENTATION OF THE ABOVE ALGORITHM (WHICH IS ESSENTIALLY THE ADDITION ALGORITHM GIVEN ON THE FIRST DAY OF CLASS.)

THE TRUTH TABLE FOR 1-ADD IS :

INPUTS			OUTPUTS	
a	b	c	C _{OUT}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

THE GENERAL PROCEDURE FOR CONSTRUCTING A CIRCUIT IS AS FOLLOWS :


- 1.) FOR EACH OUTPUT COLUMN
- 2.) FOR EACH ROW CONTAINING A 1 IN THAT COLUMN
- 3.) FORM "PRODUCT" CORRESPONDING TO INPUTS
- 4.) FORM THE "SUM" OF THESE "PRODUCTS"
- 5.) DESIGN A CIRCUIT CORRESPONDING TO THE RESULTING SET OF LOGICAL EXPRESSIONS.

FROM THE ABOVE TABLE WE GET :

$$C_{OUT} \equiv (\bar{a} \cdot b \cdot c) + (a \cdot \bar{b} \cdot c) + (a \cdot b \cdot \bar{c}) + (a \cdot b \cdot c)$$

$$S \equiv (\bar{a} \cdot \bar{b} \cdot c) + (\bar{a} \cdot b \cdot \bar{c}) + (a \cdot \bar{b} \cdot \bar{c}) + (a \cdot b \cdot c)$$

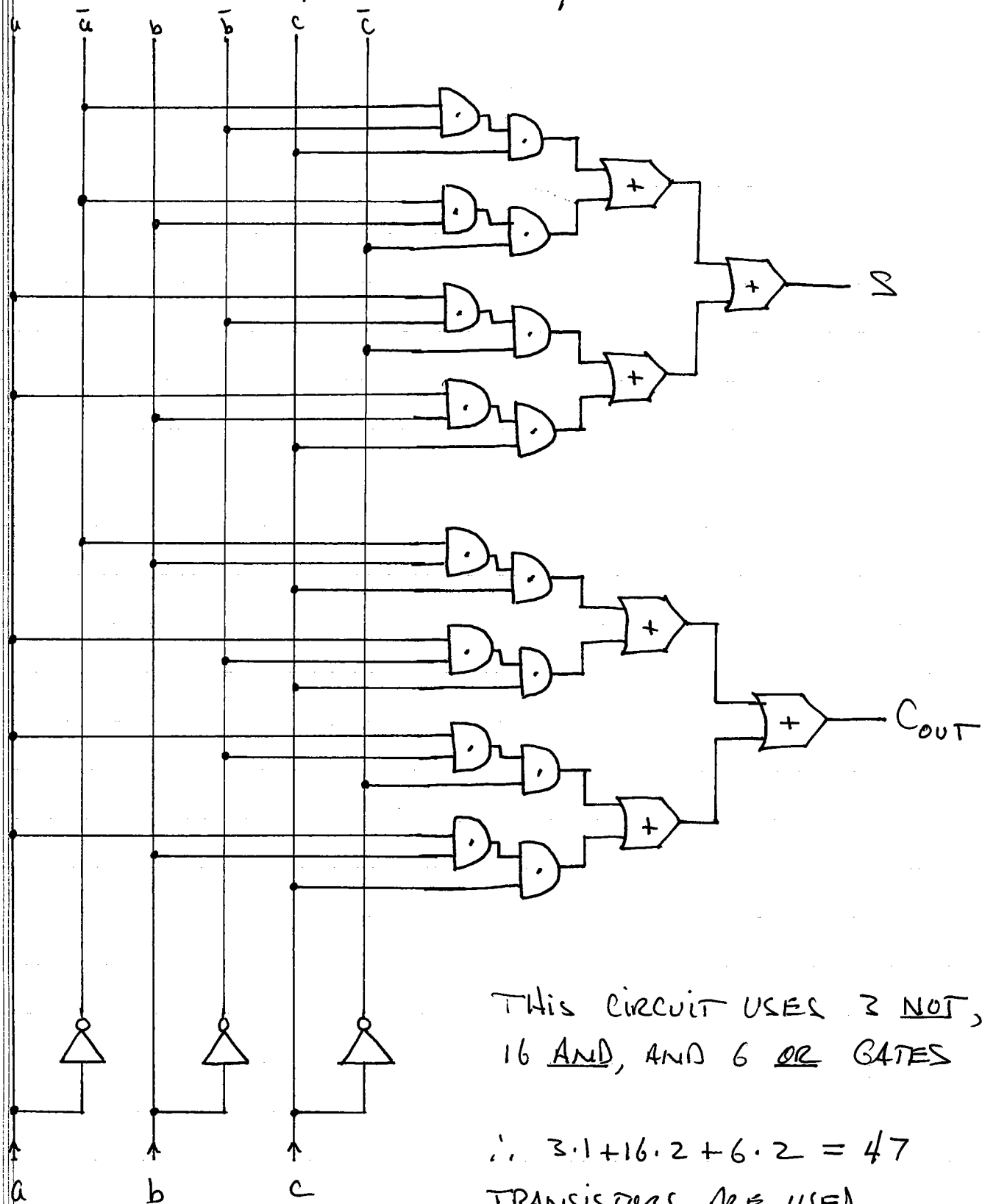WE NEED A SYSTEMATIC WAY TO DRAW CIRCUITS :




THIS CIRCUIT USES 3 NOT, 16 AND, AND 6 OR GATES

$$\therefore 3 \cdot 1 + 16 \cdot 2 + 6 \cdot 2 = 47$$

TRANSISTORS ARE USED.

TO CONSTRUCT THE FULL N-BIT ADDER WE COMBINE N COPIES OF THE ABOVE CIRCUIT.
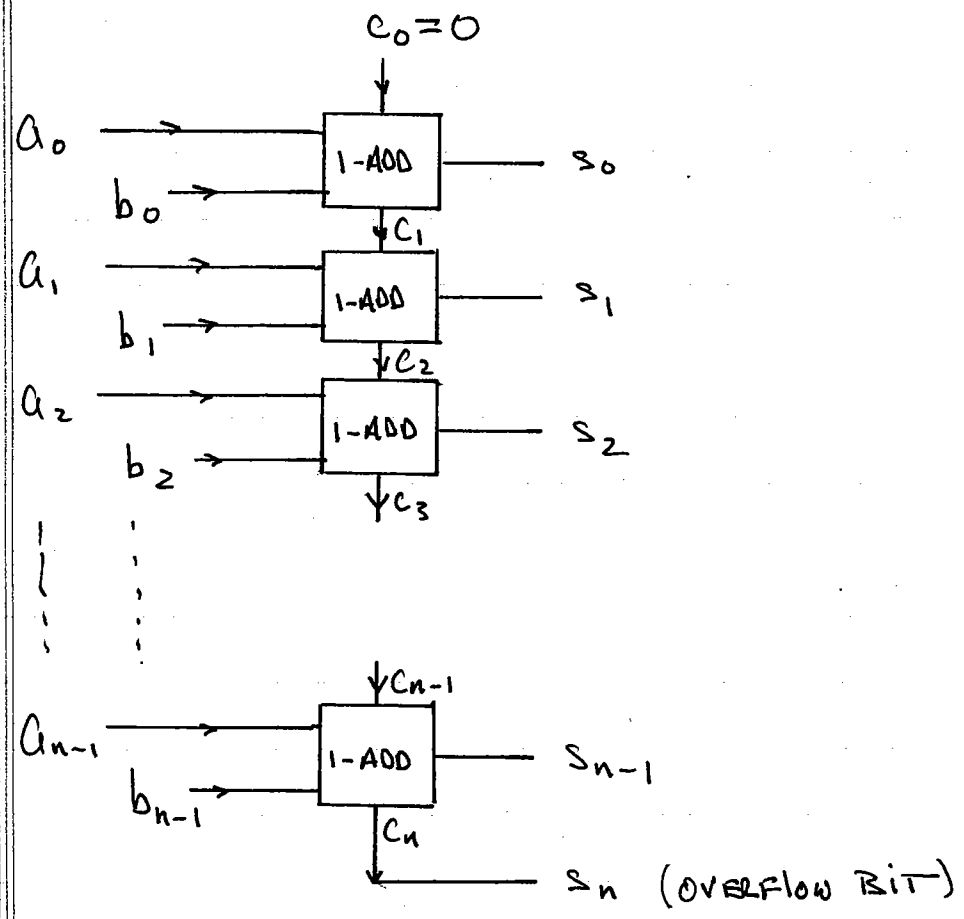
$$\underbrace{[a_{n-1} \dots a_0]_2 + [b_{n-1} \dots b_0]_2}_{\text{INPUTS}} = \underbrace{[s_n s_{n-1} \dots s_0]_2}_{\text{OUTPUT}}$$



THE N-BIT FULL ADDER USES $47N$ TRANSISTORS. FOR EXAMPLE, A 32-BIT ADDER USES $47 \cdot 32 = 1504$ TRANSISTORS


WHAT ABOUT SUBTRACTION ?

EX

$$\begin{array}{r} 010 \\ \times \times 01 = 13 \\ \underline{0111} = 7 \\ 0110 = 6 \end{array}$$

EXERCISE

DESIGN A 1-BIT SUBTRACTION CIRCUIT

 


IF $a - b - \text{LOAN} < 0$ THEN $\text{BORROW} = 1$, OTHERWISE $\text{BORROW} = 0$. THEN $d = 2 \cdot \text{BORROW} + a - b - \text{LOAN}$


a	b	LOAN	d	BORROW
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

USING 1-SUB WE CAN BUILD AN N-BIT SUBTRACTOR

EX $n=4$

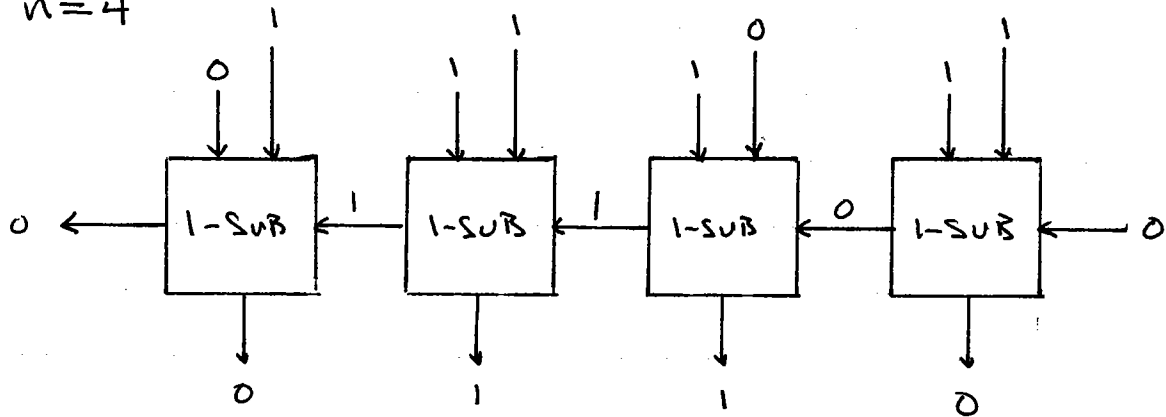

THE GENERAL N-BIT SUBTRACTOR LOOKS LIKE

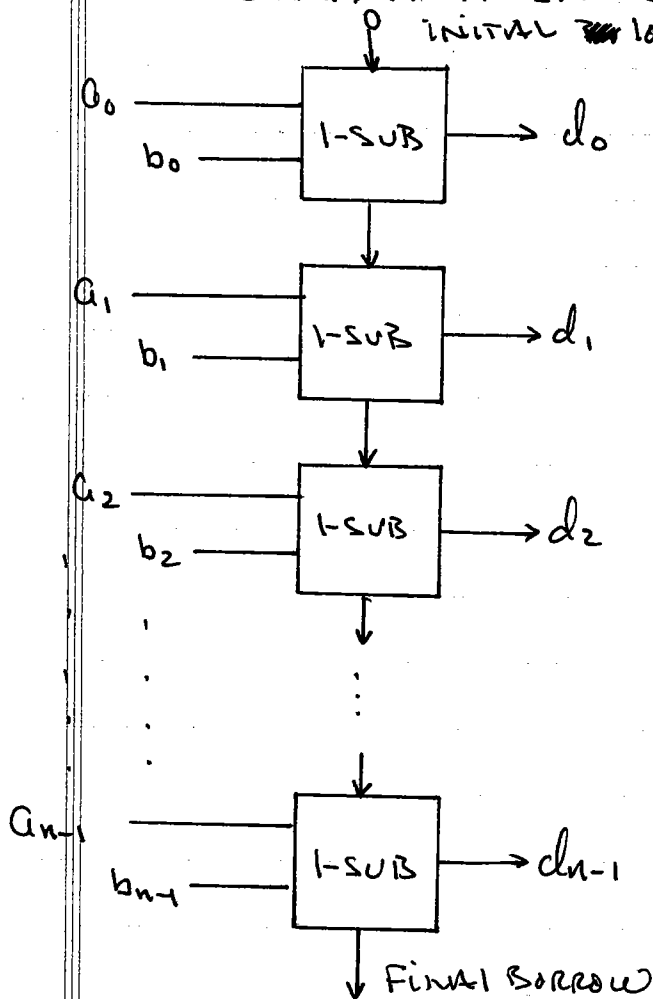

$$[d_0 \dots d_{n-1}] = [a_0 \dots a_{n-1}] - [b_0 \dots b_{n-1}]$$

COMPARISON BIT = $\begin{cases} 1 & \text{if } [a_0 \dots a_{n-1}] < [b_0 \dots b_{n-1}] \\ 0 & \text{OTHERWISE} \end{cases}$