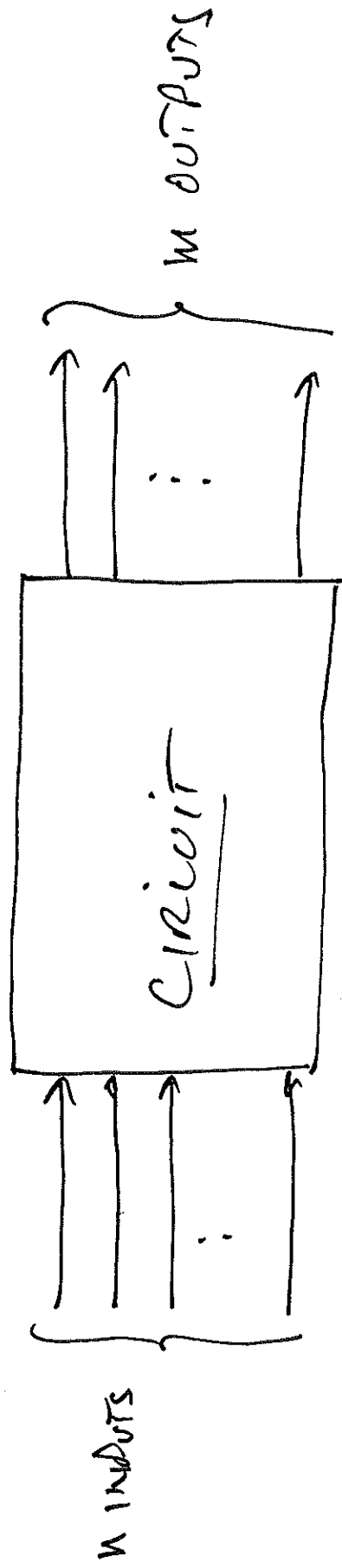


LOGICAL EQUIVALENCE

NOTICE :  $P \oplus Q \equiv P \cdot \bar{Q} + \bar{P} \cdot Q$


P	Q	$\bar{P}$	$\bar{Q}$	$P \cdot \bar{Q}$	$\bar{P} \cdot Q$	$P \cdot \bar{Q} + \bar{P} \cdot Q$	$P \oplus Q$
0	0	1	1	0	0	0	0
0	1	1	0	0	1	1	1
1	0	0	1	1	0	1	1
1	1	0	0	0	0	0	0

DEFN: A COMBINATIONAL CIRCUIT IS A COLLECTION OF LOGIC GATES THAT TRANSFORMS A SET OF BINARY INPUTS TO A SET OF BINARY OUTPUTS. REQUIRE: OUTPUTS DEPEND ONLY ON CURRENT OF INPUTS.



Ex.

6 Transistors

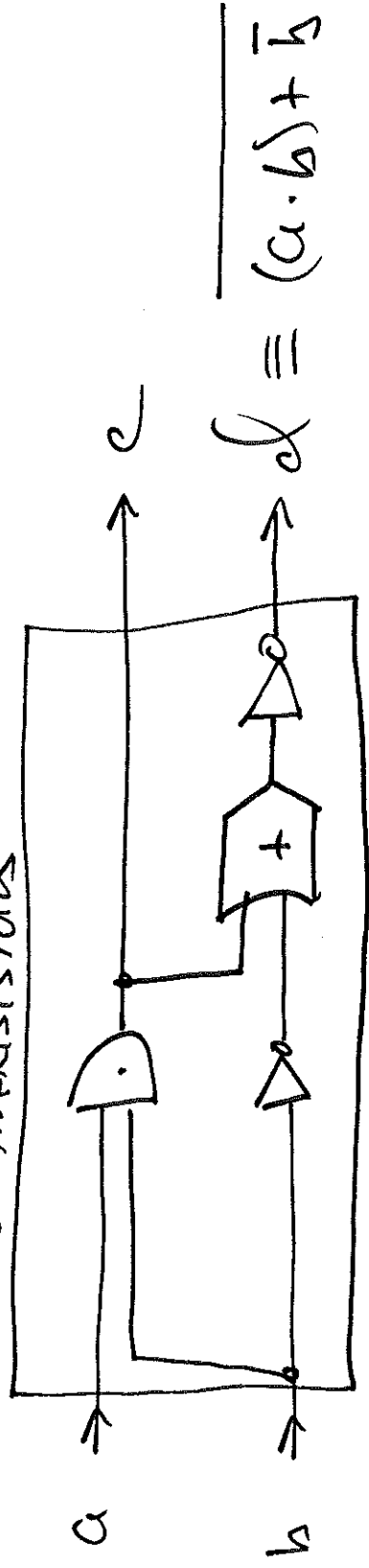

$$d \equiv \overline{(a \cdot b) + \bar{b}}$$


$a$	$b$	$c$	$d$
0	0	0	0
0	1	0	1
1	0	0	0
1	1	1	0

Note:

$$c \equiv a \cdot b$$

$$d \equiv \bar{a} \cdot \bar{b}$$

THIS SUGGESTS AN ALTERNATIVE DESIGN:

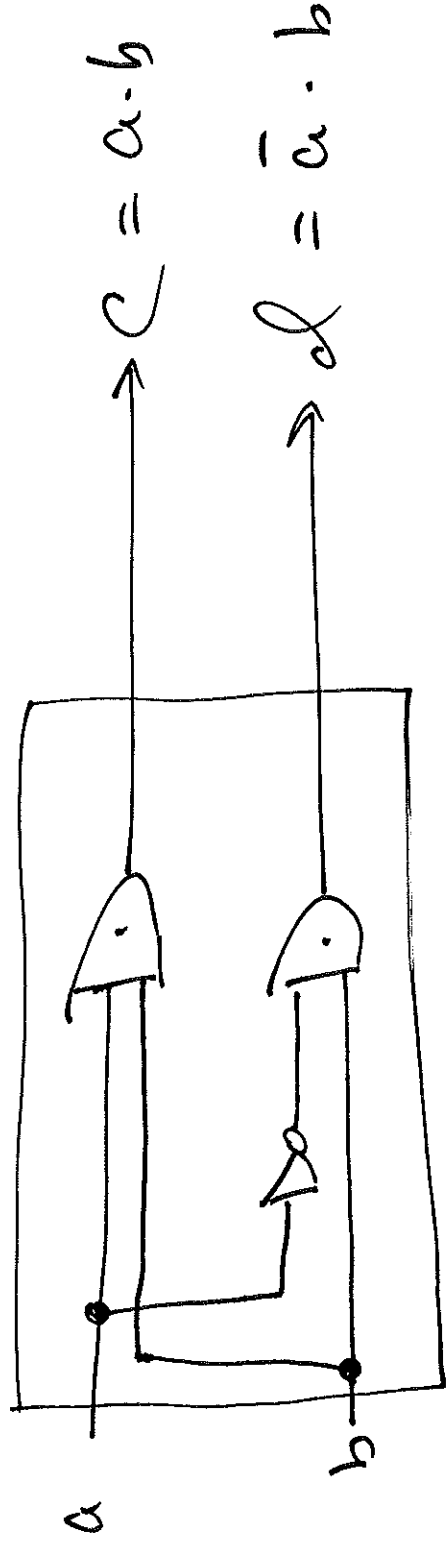

$$c = a \cdot b$$


$$d = \bar{a} \cdot b$$

5 TRANSISTORS


LOGICAL EQUIVALENCE:  $\overline{(a \cdot b) + \bar{b}} \equiv \bar{a} \cdot b$

a	b	$\bar{a}$	$\bar{b}$	$a \cdot b$	$\bar{a} \cdot b$	$(a \cdot b) + \bar{b}$	$\overline{(a \cdot b) + \bar{b}}$
0	0	1	1	0	0	1	0
0	1	1	0	0	1	0	1
1	0	0	1	0	0	1	0
1	1	0	0	1	0	1	0

CORRESPONDENCE:

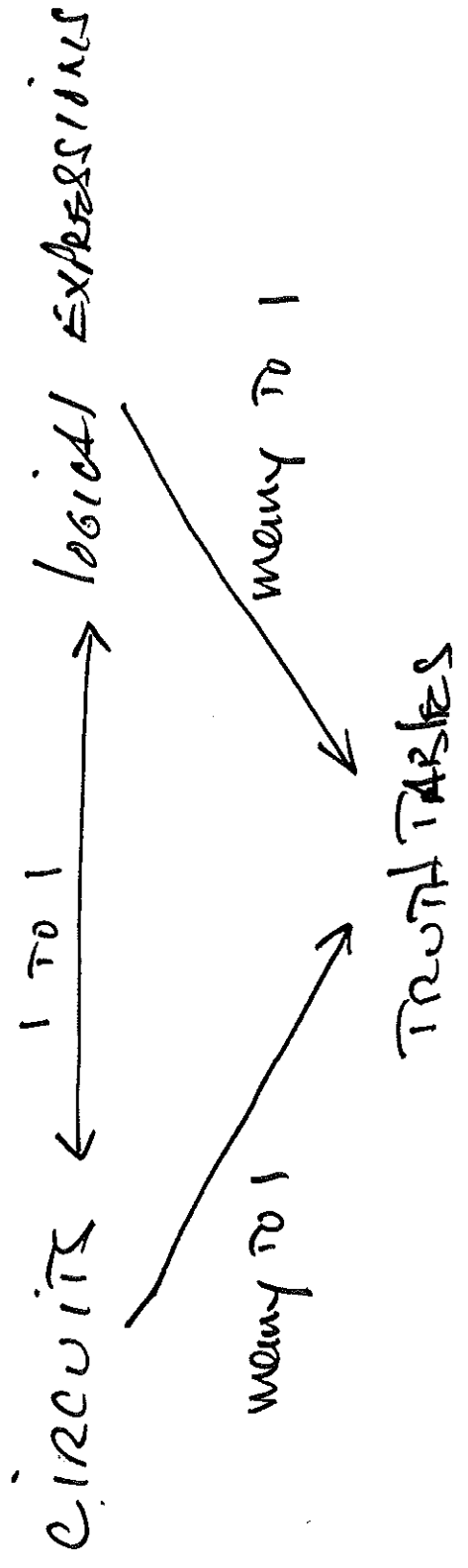

EX. 1-BIT COMPARE FOR EQUALITY CIRCUIT,

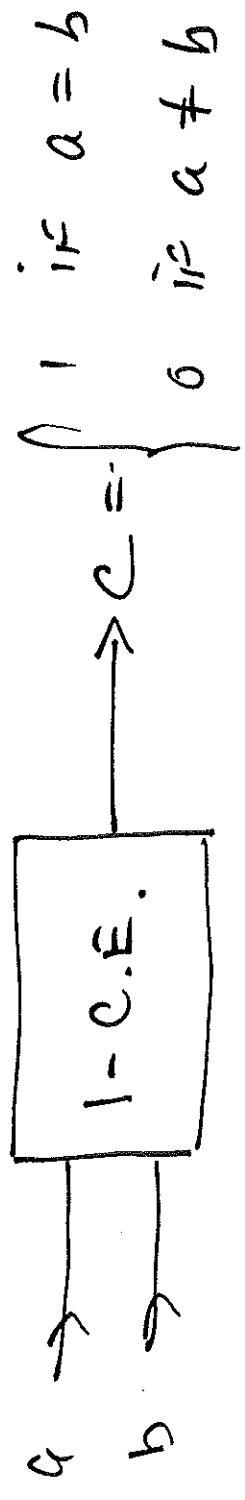

TRUTH TABLE:

a	b	c	$a \cdot b$	$\bar{a}$	$\bar{b}$	$\bar{a} \cdot \bar{b}$	$\bar{a} \cdot \bar{b} + a \cdot b$
0	0	1	0	1	1	1	1
0	1	0	0	1	0	0	0
1	0	0	0	0	1	0	0
1	1	1	1	0	0	0	1

NOTE:  $c \equiv \bar{a} \cdot \bar{b} + a \cdot b$


CONVENTION:

• HAS HIGHER PRECEDENCE THAN + & ∅

$a \cdot b + c$

means  $(a \cdot b) + c$

NOT  $a \cdot (b + c)$

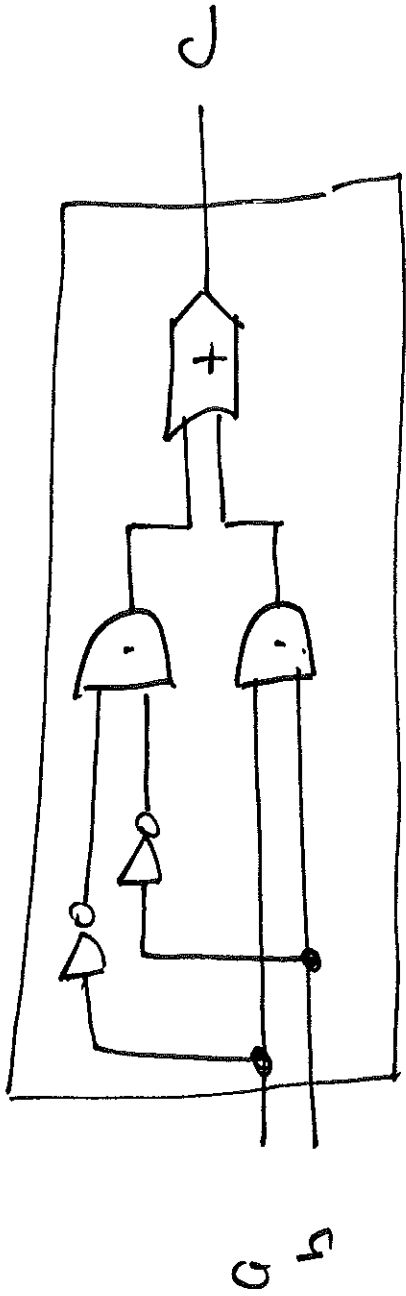

# Transistor = 8


EX. N-BIT COMPARE FOR EQUALITY CIRCUIT.

INPUT:

$a = a_{n-1} \dots a_1 a_0$  } Two N-BIT BINARY  
 $b = b_{n-1} \dots b_1 b_0$  } #5

OUTPUT: SINGLE BIT  $c = \begin{cases} 1 & \text{if } a=b \\ 0 & \text{if } a \neq b \end{cases}$

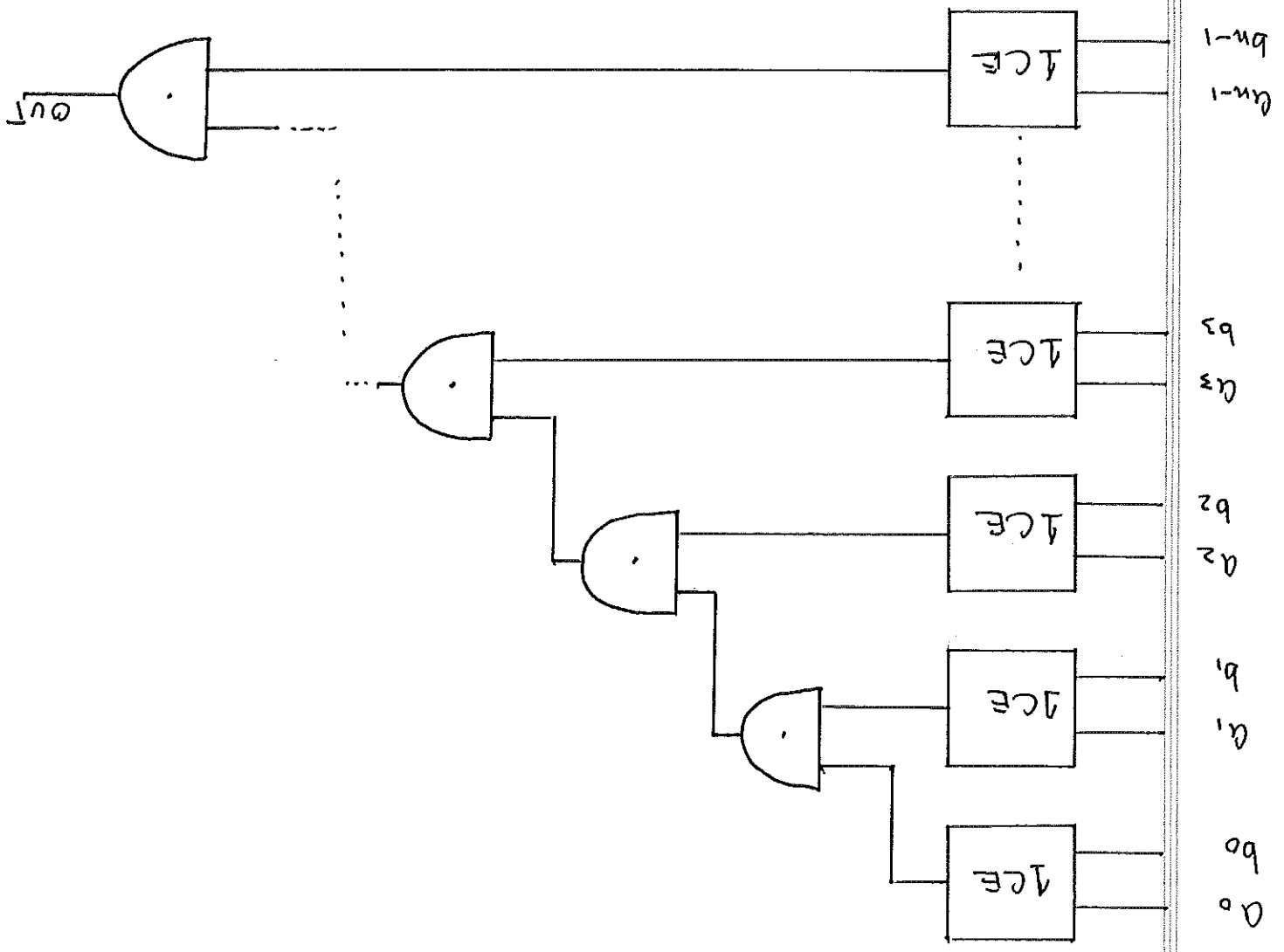INPUTS: Two n BIT BINARY NUMBERS  
 $[a_{n-1} \dots a_0]_2, [b_{n-1} \dots b_0]_2$   
 OUTPUT: 1 IF EACH  $a_i = b_i$  ( $0 \leq i \leq n-1$ ),  
 0 OTHERWISE



How many Rows AND columns would the truth TABLE FOR this circuit HAVE ?

ANSWER:  $2^{2n}$  Rows  
 $2n+1$  columns



Ex. Goal: n-bit Full Adder

$$\begin{array}{r} n=8 : \\ 101101100 \\ 10010110 \\ \hline 10110011 \\ 101001001 \end{array}$$

