

CMS 10

11-3-08

11

TRUTH TABLE FOR 1-AND

a	b	c	c _{out}	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$\begin{array}{r} \text{EX} \\ 1 \quad 1 \\ 0 \quad 0 \\ \hline 0 \end{array}$$

$$\begin{array}{r} \text{EX} \\ 1 \quad 1 \\ 1 \quad 1 \\ \hline 1 \end{array}$$

Circuit Design Algorithm!


12

- 1.) for each output column
- 2.) for each row containing A 1 in that column
- 3.) form "product" corresponding to those inputs
- 4.) form "sum" of these "products"

$$C_{out} = [(\bar{a} \cdot b \cdot c) + (a \cdot \bar{b} \cdot c)] + [a \cdot b \cdot \bar{c}] + (a \cdot b \cdot c)$$

$$S = [(\bar{a} \cdot \bar{b} \cdot c) + (\bar{a} \cdot b \cdot \bar{c})] + [a \cdot \bar{b} \cdot \bar{c}] + (a \cdot b \cdot c)$$

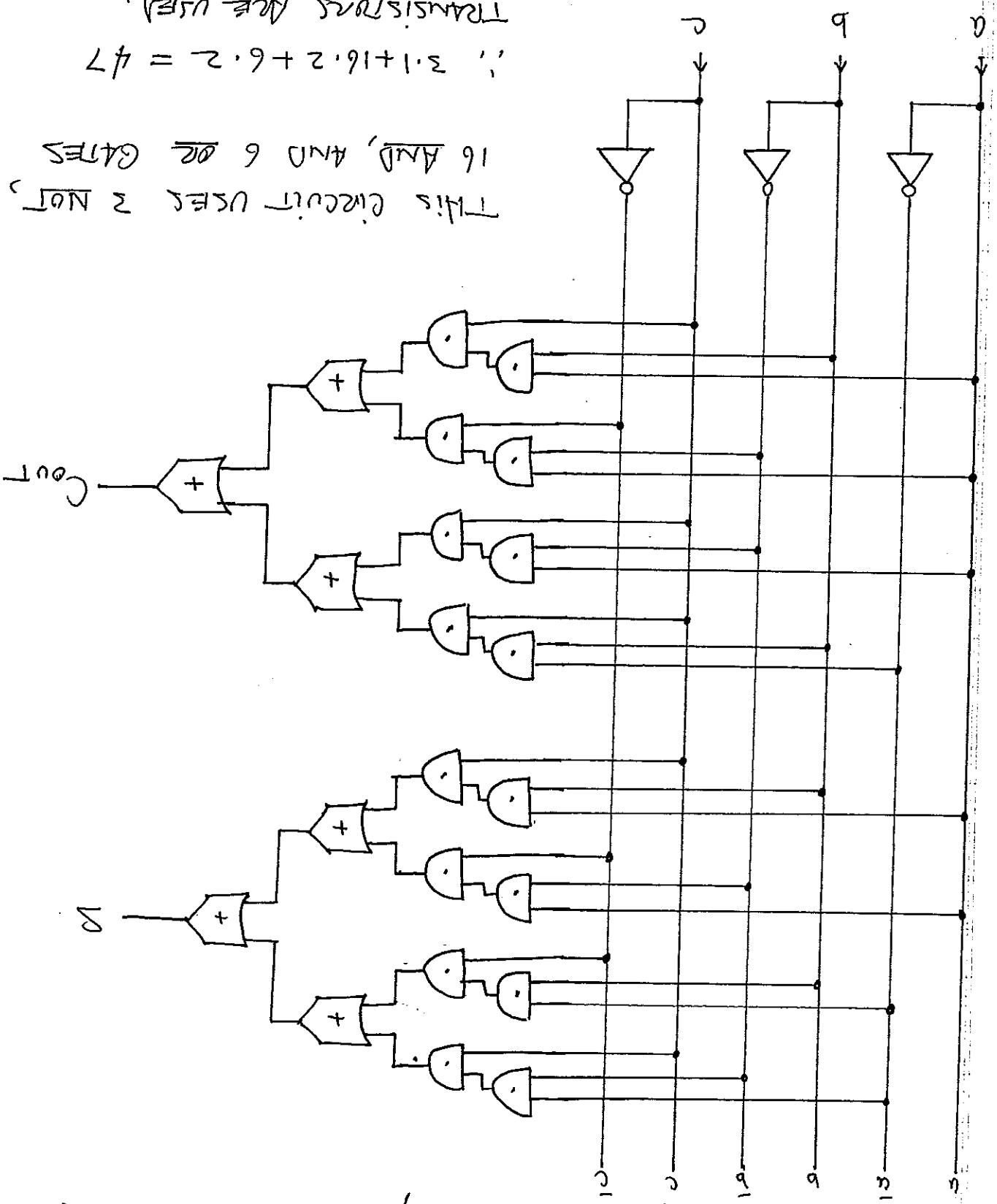WE NEED A SYSTEMATIC WAY TO DRAW CIRCUITS:






THIS CIRCUIT USES 3 NOT, 16 AND, AND 6 OR GATES



∴ 3·1+16·2+6·2 = 47

TRANSISTORS ARE USED.

NO 3-INPUT
AND GATES

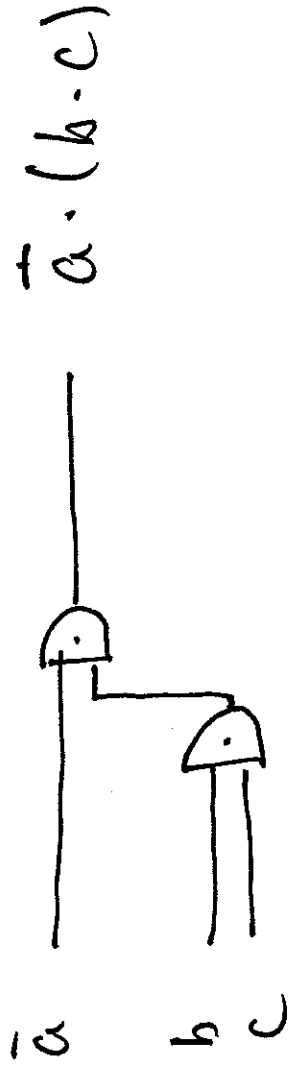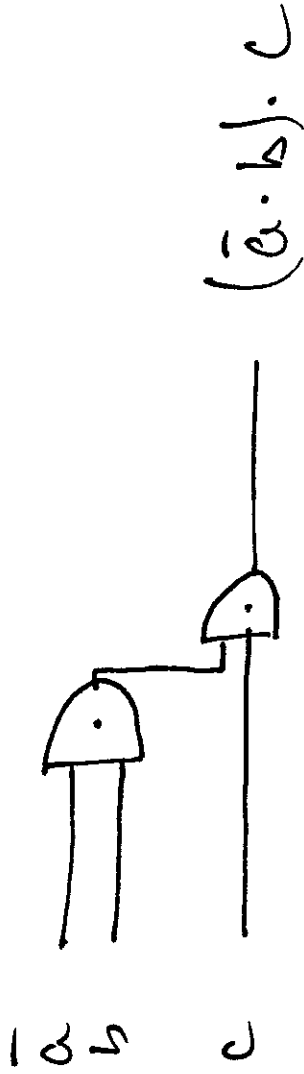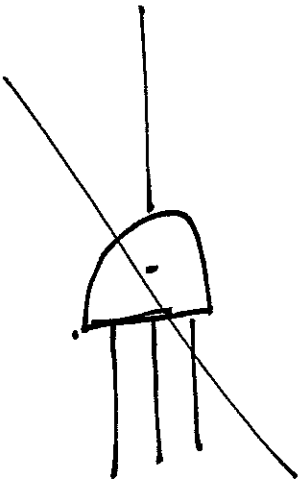

19

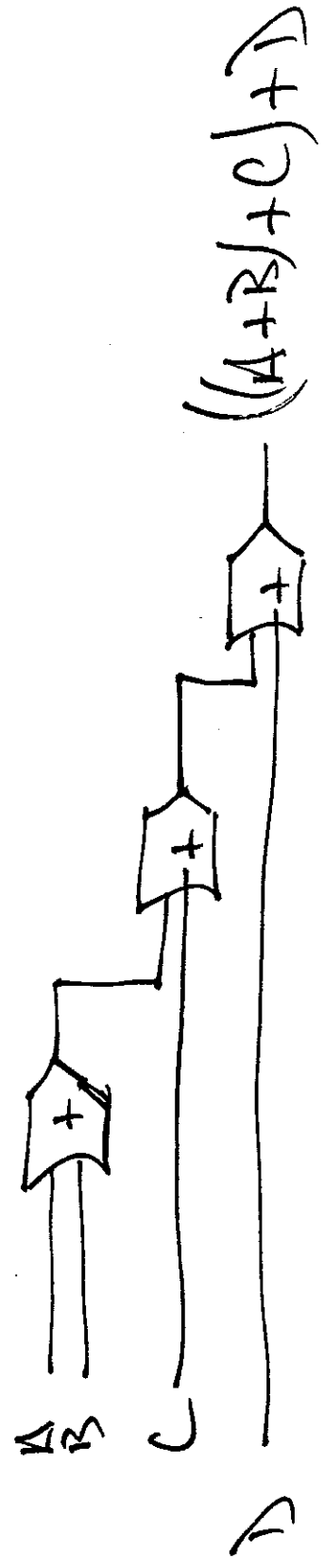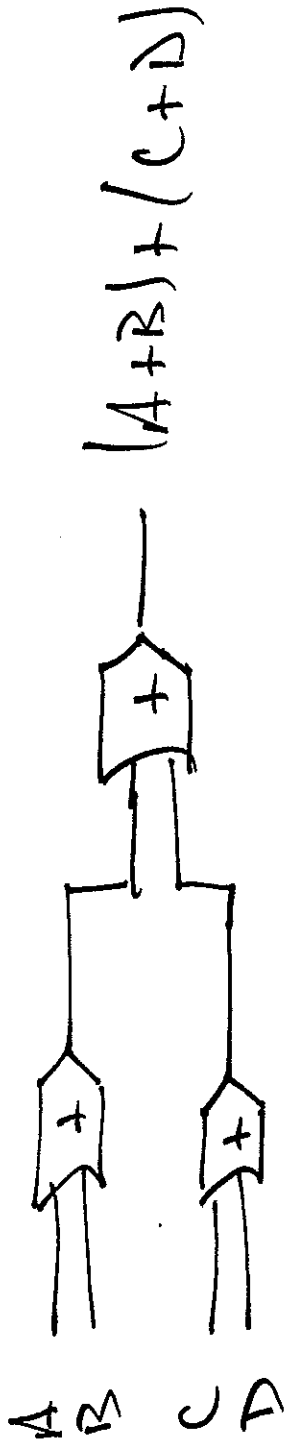

$$A+(B+(C+D))$$

ASSOCIATIVE LAWS

15

$$A \cdot (B \cdot C) \equiv (A \cdot B) \cdot C \quad \checkmark$$

$$A + (B + C) \equiv (A + B) + C$$


A	B	C	B · C	A · (B · C)	A · B	(A · B) · C
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	1	0	0	0
1	0	0	0	0	0	0
1	0	1	0	0	0	0
1	1	0	0	0	1	0
1	1	1	1	1	1	1



TO CONSTRUCT THE FULL N-BIT ADDRESS WE COMBINE N COPIES OF THE ABOVE CIRCUIT.

$$[a_{n-1} \dots a_0]_2 + [b_{n-1} \dots b_0]_2 = [s_n s_{n-1} \dots s_0]_2$$

INPUTS OUTPUT

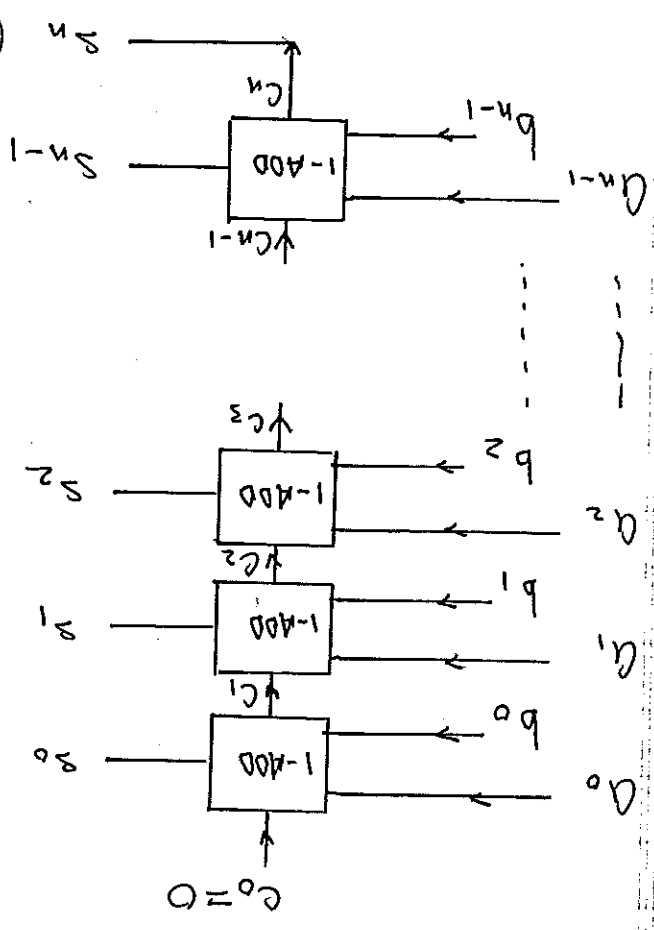

THE N-BIT FULL ADDRESS USES 4N TRANSISTORS.
 FOR EXAMPLE, A 32-BIT ADDRESS USES 47.32
 = 1504 TRANSISTORS


WHAT ABOUT SUBTRACTION?

EX

$$\begin{array}{r} 010 \\ \times 01 \\ \hline 0110 \\ 0111 \\ \hline 0110 = 6 \end{array}$$

EXERCISE

DESIGN A 1-BIT SUBTRACTION CIRCUIT

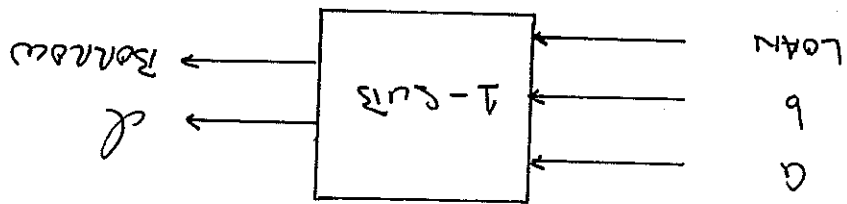


IF $a - b - \text{LOAN} < 0$ THEN $\text{BORROW} = 1$, OTHERWISE $\text{BORROW} = 0$. THEN $d = 2 \cdot \text{BORROW} + a - b - \text{LOAN}$


a	1	1	1	0	0	0	0	0	0
b	1	1	0	1	1	0	0	0	0
LOAN	1	0	1	0	1	0	1	1	0
d	1	0	0	1	0	1	1	1	0
BORROW	1	0	0	0	0	1	1	1	0

USING 1-BIT WE CAN BUILD AN N-BIT SUBTRACTOR

EX N=4

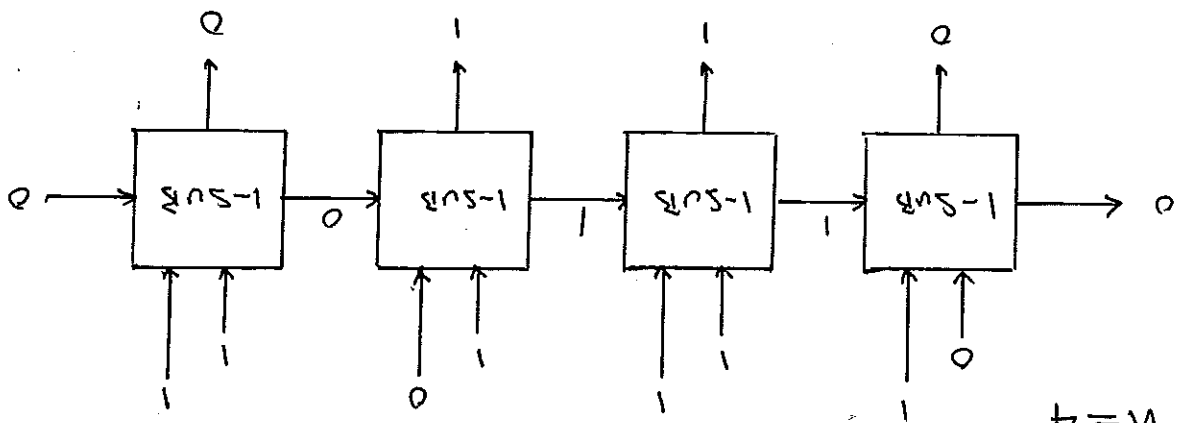

THE GENERAL N-BIT SUBTRACTOR LOOKS LIKE

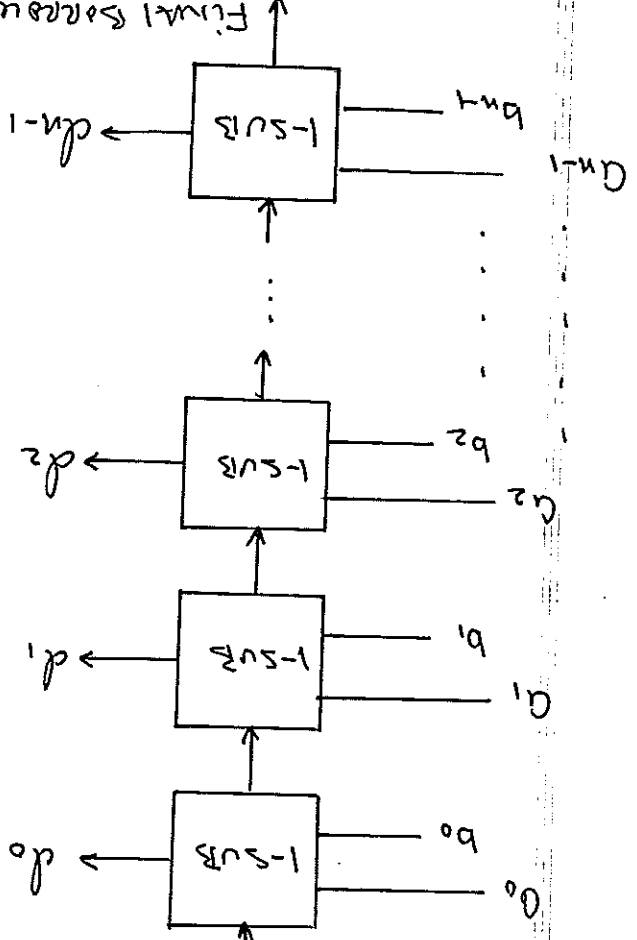

$$[d_0 \dots d_{n-1}] = [a_0 \dots a_{n-1}] - [b_0 \dots b_{n-1}]$$

Final borrow $\text{RIT} = \begin{cases} 1 & \text{if } [a_0 \dots a_{n-1}] < [b_0 \dots b_{n-1}] \\ 0 & \text{OTHERWISE} \end{cases}$