


CNAPS 10

11-10-09


11

Logic GATES


and

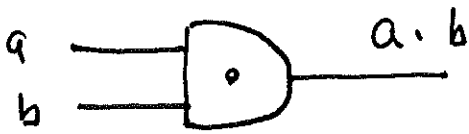


a	b	a.b
0	0	0
0	1	0
1	0	0
1	1	1

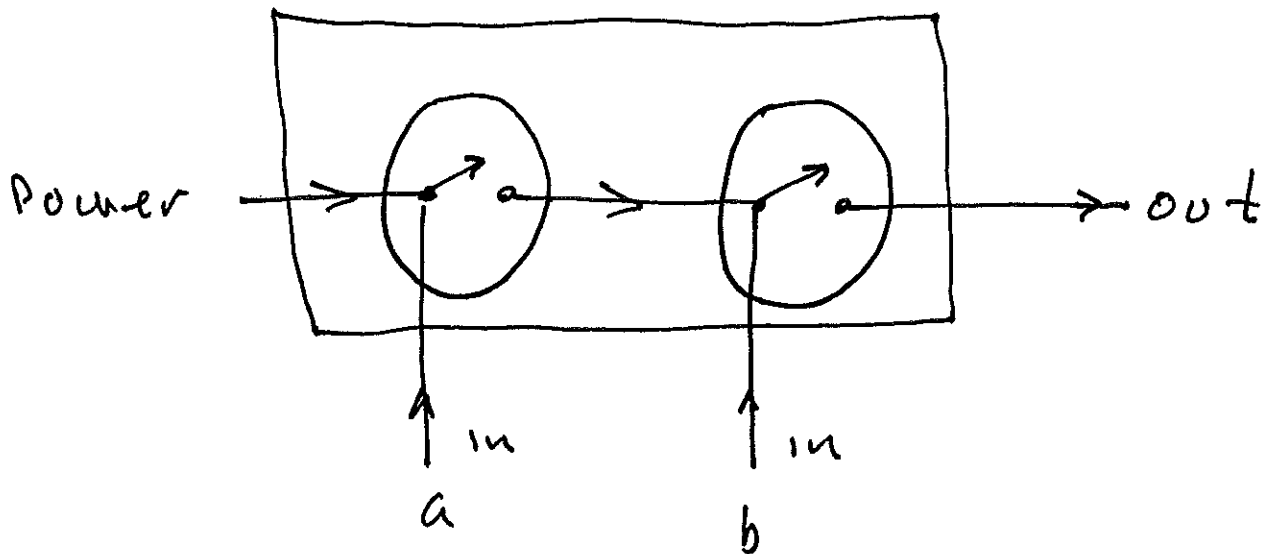


or

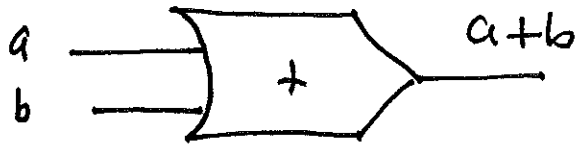


a	b	a + b
0	0	0
0	1	1
1	0	1
1	1	1

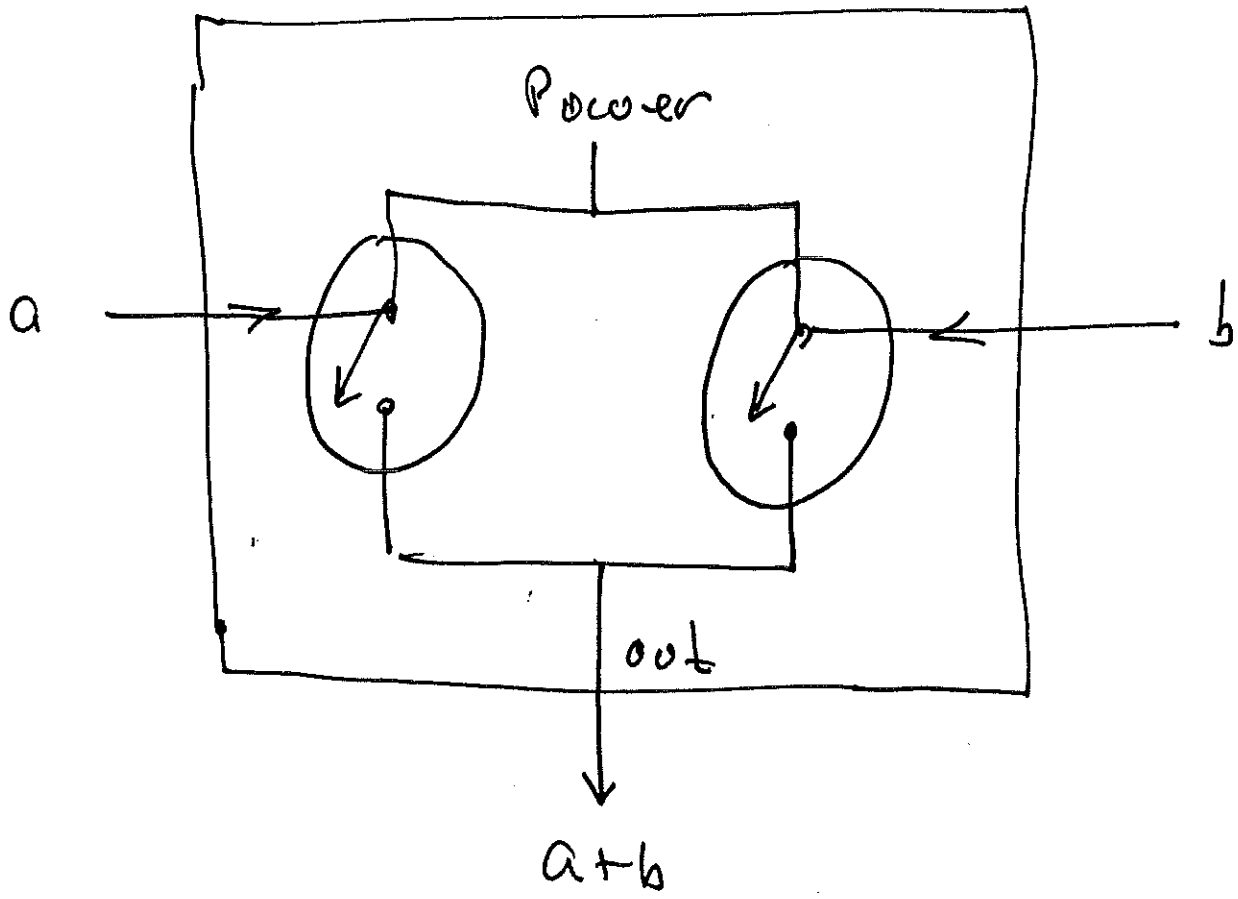

Not

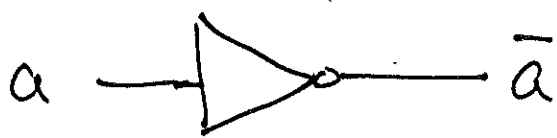


a	\bar{a}
0	1
1	0

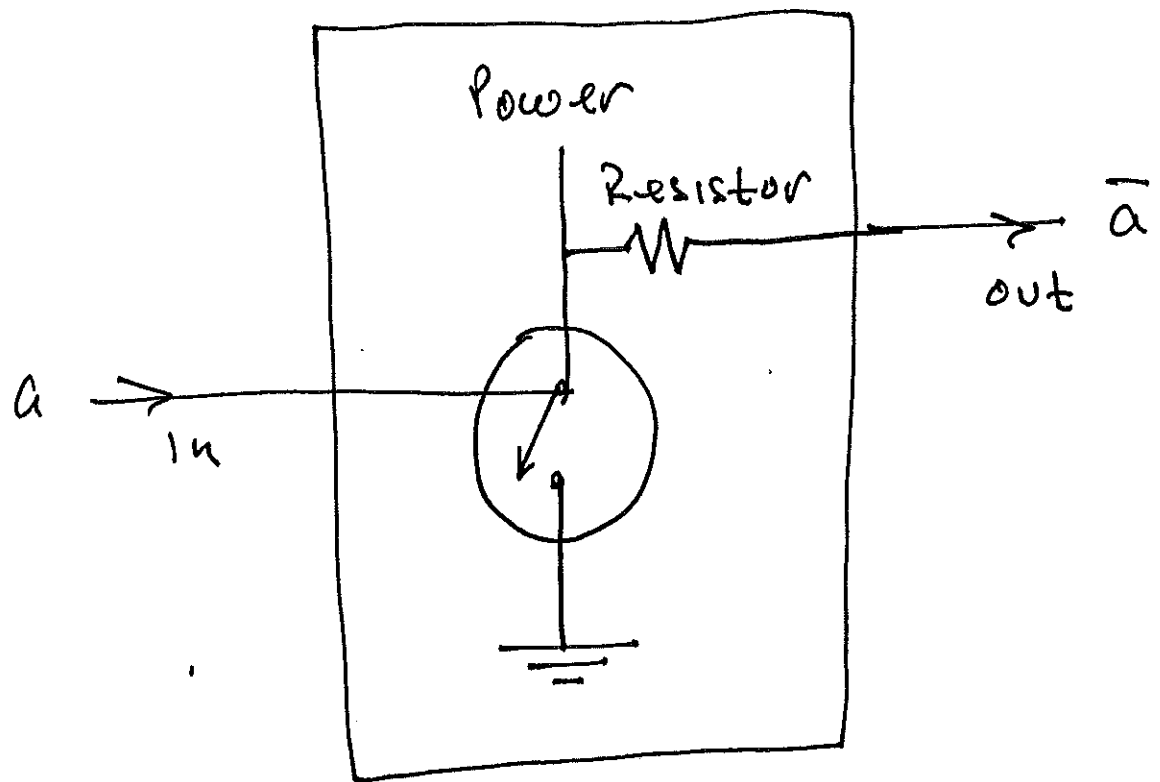

Recall : xor (symbol \oplus)

a	b	$a \oplus b$
0	0	0
0	1	1
1	0	1
1	1	0

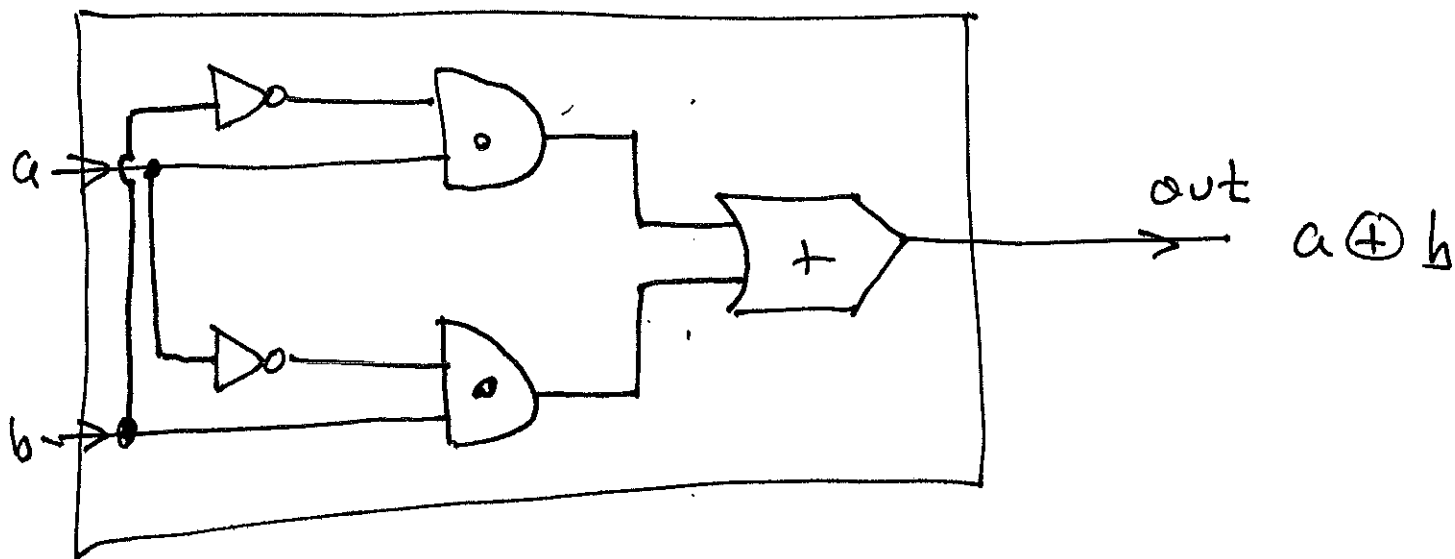

$$a \oplus b \equiv (a \cdot \bar{b}) + (\bar{a} \cdot b)$$

Truth Table for $(a \cdot \bar{b}) + (\bar{a} \cdot b)$


a	b	\bar{a}	\bar{b}	$a \cdot \bar{b}$	$\bar{a} \cdot b$	$(a \cdot \bar{b}) + (\bar{a} \cdot b)$
0	0	1	1	0	0	0
0	1	1	0	0	1	1
1	0	0	1	1	0	1
1	1	0	0	0	0	0

This truth table proves that

$$a \oplus b \equiv (a \cdot \bar{b}) + (\bar{a} \cdot b)$$

Defn A Combinational Circuit

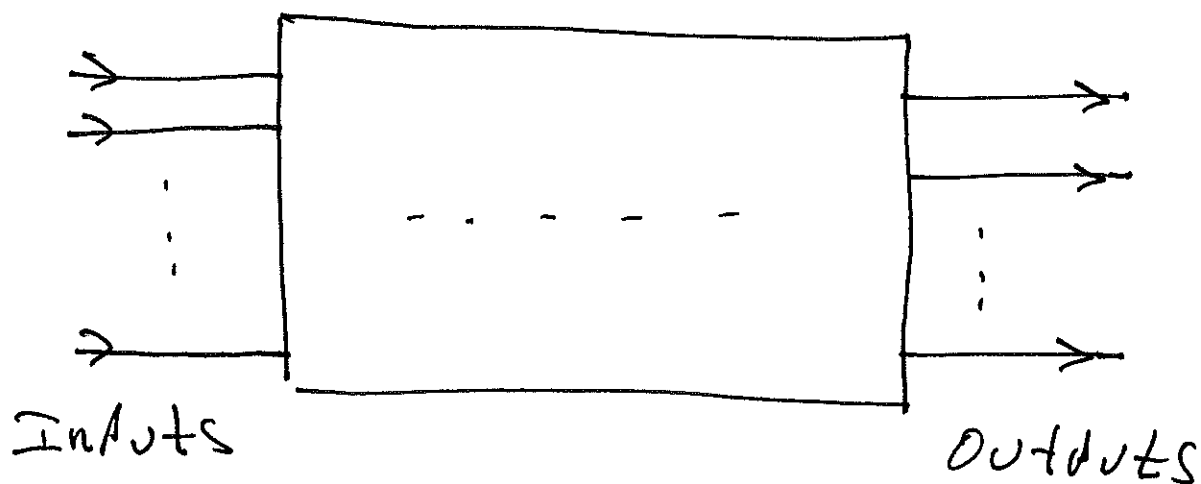
is a collection of logic gates
that transforms some binary
inputs to some binary outputs



Require: output depend on
current values of inputs.

Ex

7

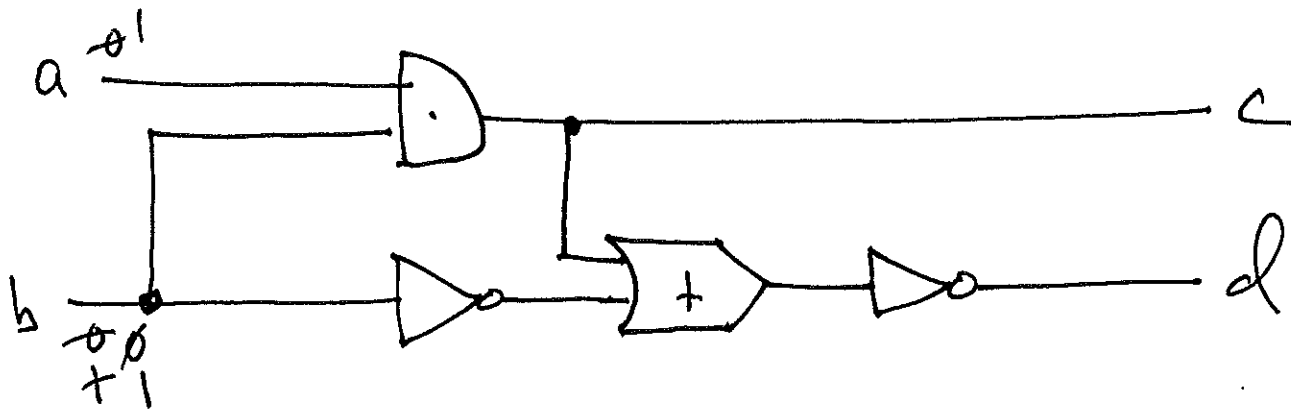

TRUTH TABLE :

a	b	c	d
0	0	0	0
0	1	0	1
1	0	0	0
1	1	1	0

note : $c \equiv a \cdot b$

$$d = \overline{(a \cdot b) + \bar{b}}$$