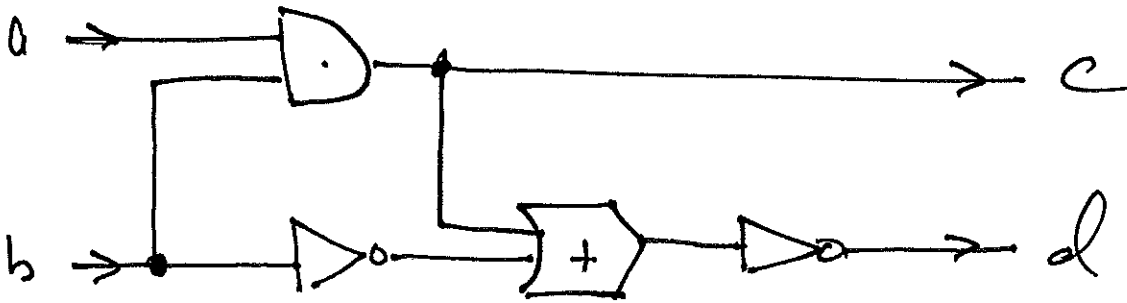


CMPD 10

11-12-09

L

Recall:



6 TRANSISTORS


Truth Table:

$a$	$b$	$c$	$d$
0	0	0	0
0	1	0	1
1	0	0	0
1	1	1	0

note:  $c \equiv a \cdot b$

$d \equiv \bar{a} \cdot b$

# An Equivalent circuit

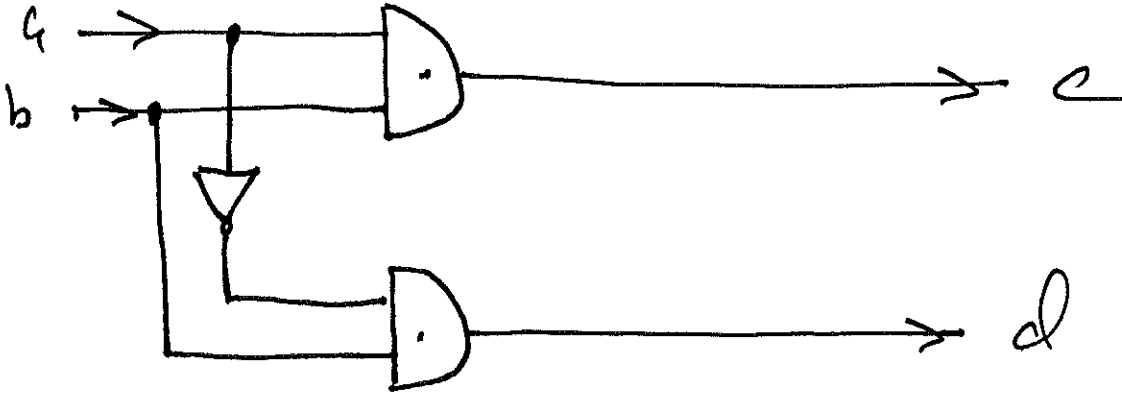

5 Transistors

NOTE: from 1<sup>st</sup> circuit:


$$d \equiv \overline{b + (a \cdot b)}$$

Truth Table showing  $\overline{b + (a \cdot b)} \equiv \bar{a} \cdot \bar{b}$  ✓

a	b	$\bar{a}$	$\bar{b}$	$(a \cdot b)$	$b + (a \cdot b)$	$\overline{b + (a \cdot b)}$	$\bar{a} \cdot \bar{b}$
0	0	1	1	0	1	0	0
0	1	1	0	0	0	1	1
1	0	0	1	0	1	0	0
1	1	0	0	1	1	0	0



## CORRESPONDANCES:

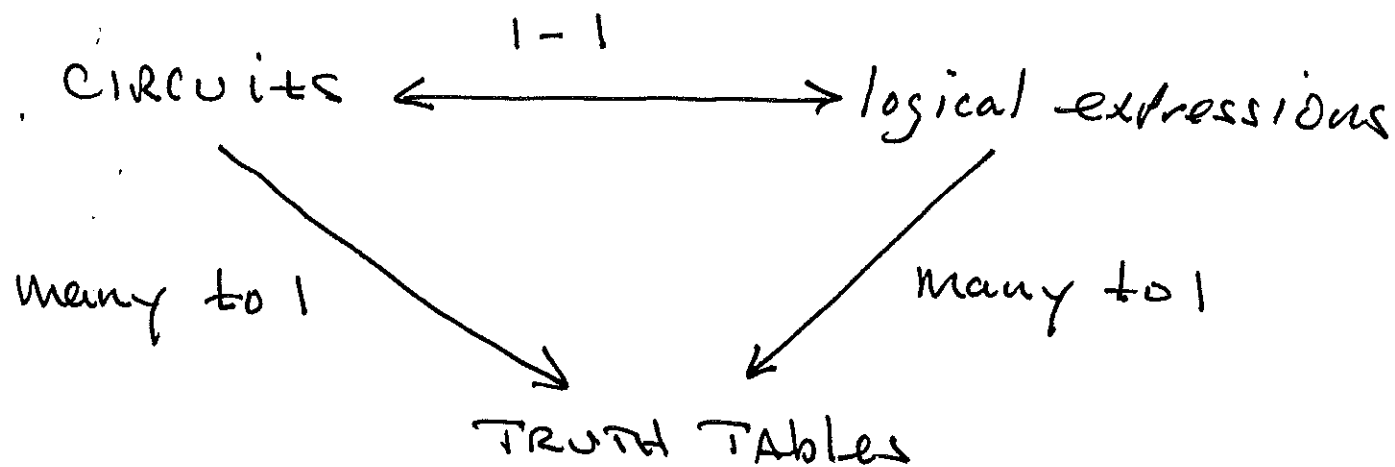

Ex. Design a 1-bit Compare for equality circuit. i.e. given inputs  $a, b$  output 1 if  $a=b$ , 0 if  $a \neq b$ .

a	b	c
0	0	1
0	1	0
1	0	0
1	1	1


observe!  $c \equiv (\bar{a} \cdot \bar{b}) + (a \cdot b)$

(4)

entzick

a	b	$\bar{a}$	$\bar{b}$	$\bar{a} \cdot \bar{b}$	$a \cdot b$	$\bar{a} \cdot \bar{b} + a \cdot b$
0	0	1	1	1	0	1
0	1	1	0	0	0	0
1	0	0	1	0	0	0
1	1	0	0	0	1	1


einheit

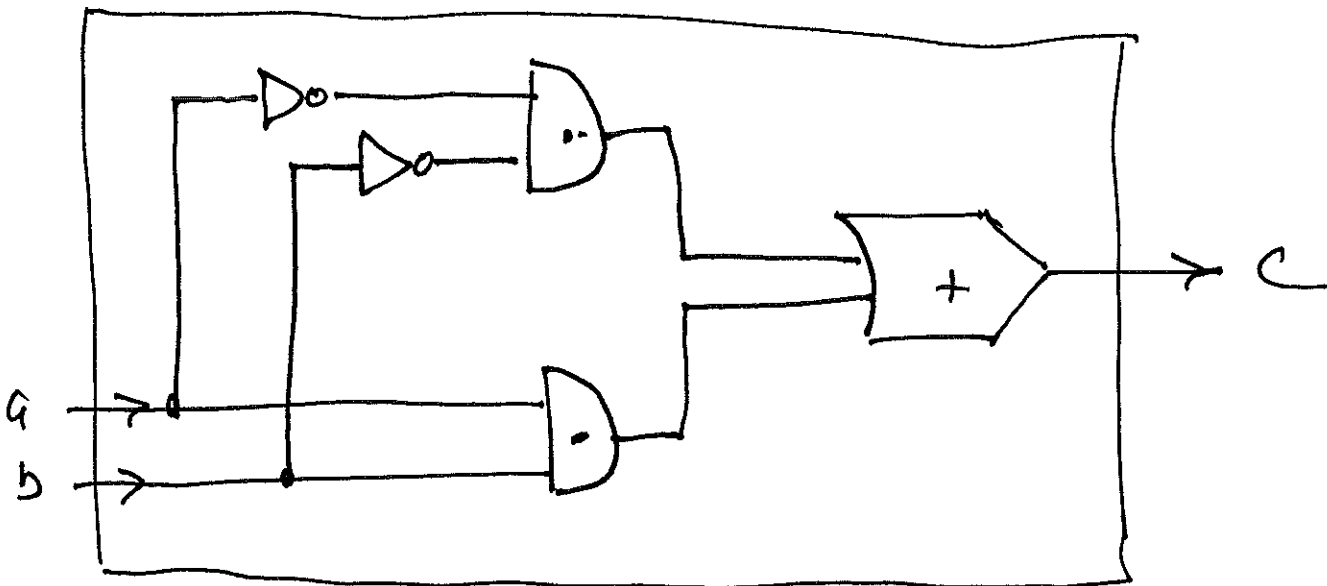

1-CE

Ex.  $n$ -bit compare for equality circuit. Input: 2 bit strings of length  $n$ :  $a_0 \dots a_{n-1}$ ,  $b_0 \dots b_{n-1}$   
Output: 1 if 2 bit strings are identical, 0 otherwise.


Use 1-CB Circuit

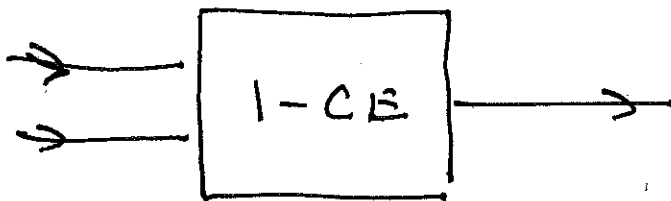

INPUTS: TWO  $n$  BIT BINARY NUMBERS

$$[a_{n-1} \dots a_0]_2, [b_{n-1} \dots b_0]_2$$

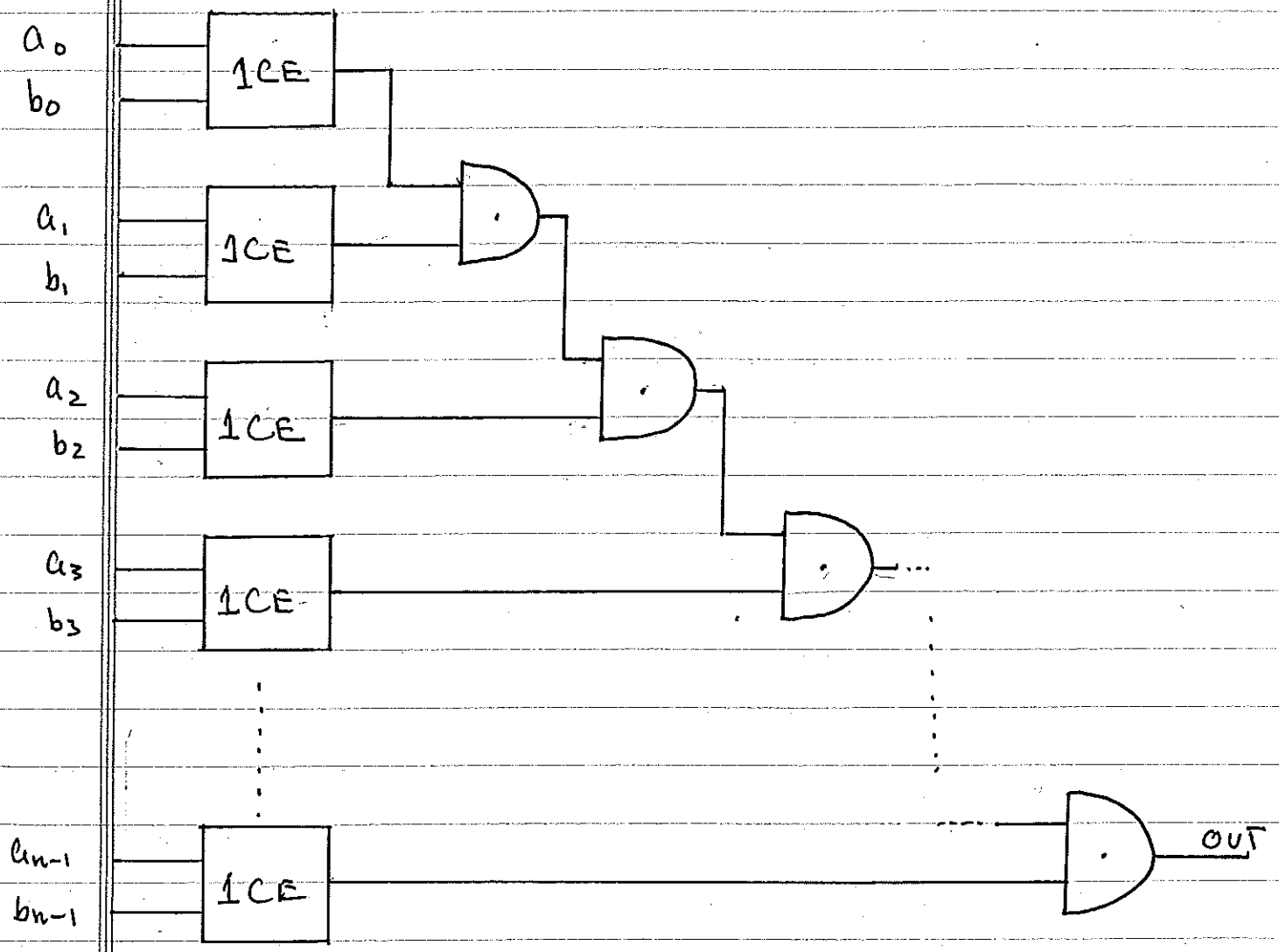OUTPUT: 1 IF EACH  $a_i = b_i$  ( $0 \leq i \leq n-1$ ),  
0 OTHERWISE



How many rows and columns would the truth table for this circuit have?

ANSWER:  $2^{2n}$  Rows  
 $2n+1$  Columns


Ex. Goal: Design n-bit full adder 7

ex. addition in binary  $n=8$

$$\begin{array}{r} 101101100 \\ 10010110 \\ \hline 101100111 \\ \hline 101001001 \end{array}$$

{ Inputs:  $a, b, c_{in}$   
Outputs:  $s, c_{out}$

First build a 1-bit adder

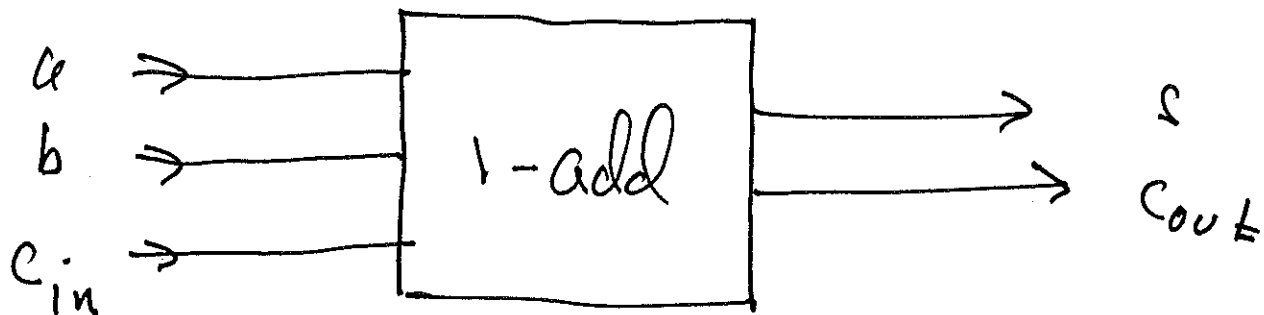

Truth Table:

inputs			outputs	
a	b	c	C <sub>out</sub>	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Circuit Design algorithm

- 1.) for each output col.
- 2.) for each row containing a 1 in that col.
- 3.) form 'product' of corresponding inputs
- 4.) form 'sum' of these products
- 5.) Draw circuit corresponding to this set of logical expressions.



from truth table we get

9

$$C_{out} \equiv (\bar{a} \cdot b \cdot c) + (a \cdot \bar{b} \cdot c) + (a \cdot b \cdot \bar{c}) + (a \cdot b \cdot c)$$


$$S \equiv (\bar{a} \cdot \bar{b} \cdot c) + (\bar{a} \cdot b \cdot \bar{c}) + (a \cdot \bar{b} \cdot \bar{c}) + (a \cdot b \cdot c)$$


Now Draw circuit !

note


$$S \equiv \left[ (\bar{a} \cdot \bar{b}) \cdot c \right] + \left[ (\bar{a} \cdot b) \cdot \bar{c} \right] + \left[ (a \cdot \bar{b}) \cdot \bar{c} \right] + \left[ (a \cdot b) \cdot c \right]$$

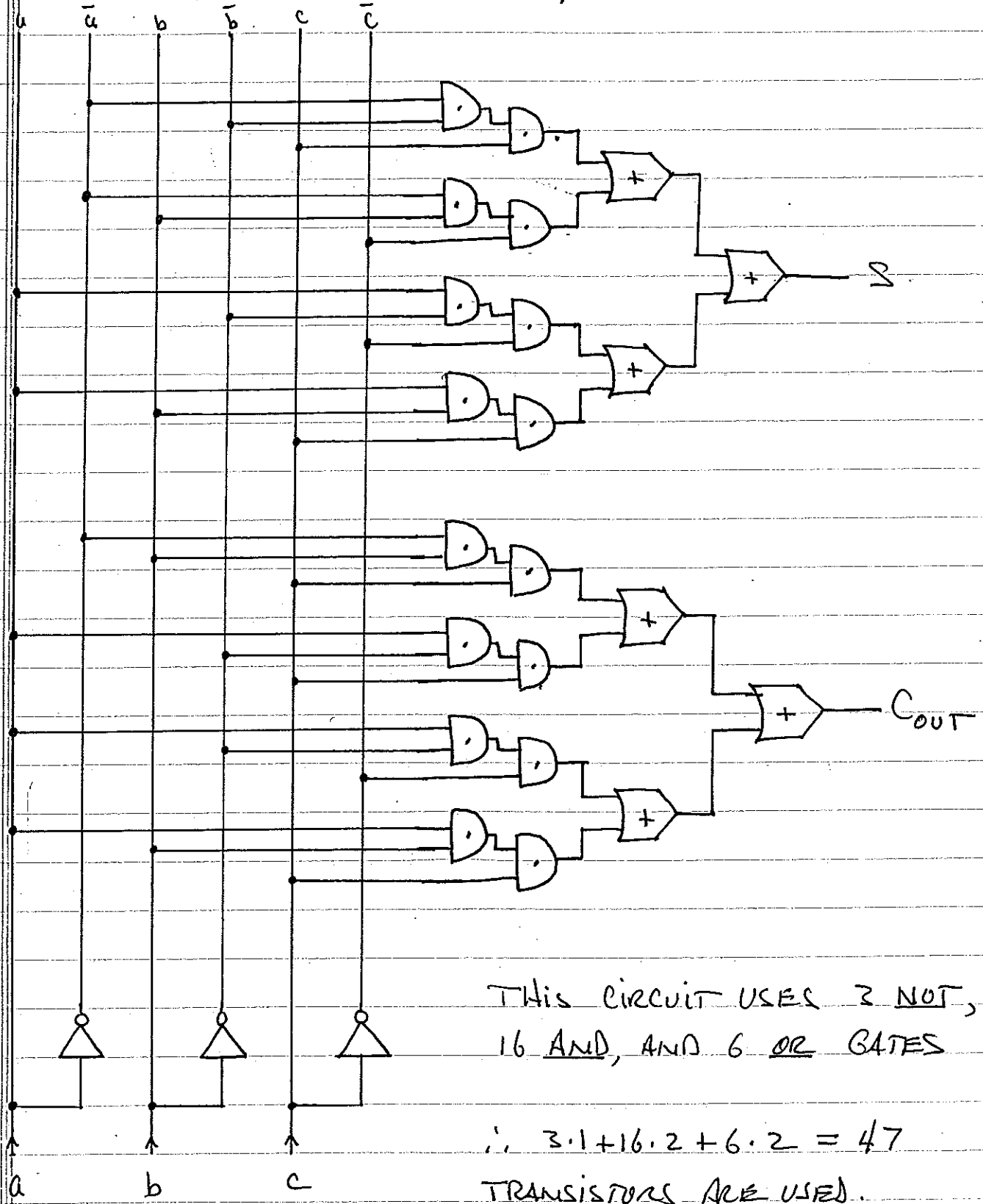WE NEED A SYSTEMATIC WAY TO DRAW CIRCUITS:




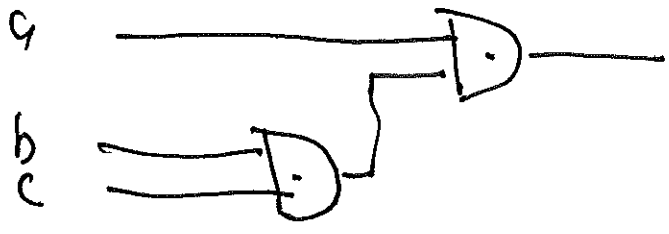

$$a \cdot (b \cdot c)$$

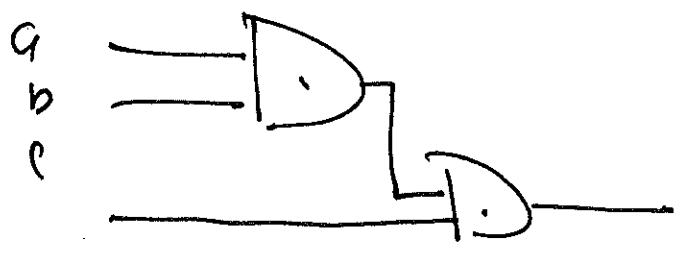

$$(a \cdot b) \cdot c$$

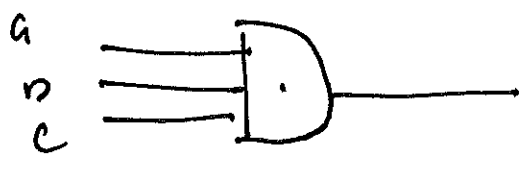

$$a \cdot b \cdot c$$

# Lab 4: Examples

n	100	200	400	800	1600
f(n)	113979	527482	2391840	10685800	47198500
<u>Guess <math>\Theta(n^3)</math></u>					
$n^3$	1000000	8000000	64000000	512000000	4096000000
f(n)/n <sup>3</sup>	0.113979	0.0659352	0.0373724	0.0208708	0.0115231

Conclusion:  $\Theta(n^3)$  Too high.

## Guess $\Theta(n^2)$

$n^2$	10000	40000	160000	640000	2560000
f(n)/n <sup>2</sup>	11.3979	13.187	14.949	16.6966	18.4369

Conclusion:  $\Theta(n^2)$  Too low.

## Guess $\Theta(n^2 \log n)$

$n^2 \log(n)$	46051.7	211933	958634	4278150	18887100
f(n)/n <sup>2</sup> log(n)	2.47503	2.48891	2.49505	2.49777	2.49899

Conclusion:  $f(n) = \Theta(n^2 \log n)$

Const = 2.498