

CNAPS 10

11-4-10



Symbols

Logic operators:

math

Circuits

conjunction (and)

\wedge

\cdot

disjunction (or)

\vee

$+$

Negation (not)

\neg

$\overline{\text{exp}}$

exclusive or (xor)

$\bar{\vee}$

\oplus

Logical constants

false

F

0

true

T

1

Truth Tables

Negation :

a	\bar{a}
0	1
1	0

Conjunction, disjunction, exclusive or

a	b	$a \cdot b$	$a + b$	$a \oplus b$
0	0	0	0	0
0	1	0	1	1
1	0	0	1	1
1	1	1	1	0

Logical Identities :

• commutative : $a \cdot b = b \cdot a$

$$a + b = b + a$$

$$a \oplus b = b \oplus a$$

• associative : $a \cdot (b \cdot c) = (a \cdot b) \cdot c$

$$a + (b + c) = (a + b) + c$$

$$a \oplus (b \oplus c) = (a \oplus b) \oplus c$$

• Distributive : $a \cdot (b + c) = (a \cdot b) + (a \cdot c)$

$$a + (b \cdot c) = (a + b) \cdot (a + c)$$

• Demorgan : $\overline{a \cdot b} = \bar{a} + \bar{b}$


$$\overline{a + b} = \bar{a} \cdot \bar{b}$$

• other : $a \cdot 1 = a$ $a \cdot 0 = 0$
 $a + 1 = 1$ $a + 0 = a$

Truth table for 1st DeMorgan:

$\overline{a \cdot b} = \bar{a} + \bar{b}$ ✓

a	b	a · b	$\overline{a \cdot b}$	\bar{a}	\bar{b}	$\bar{a} + \bar{b}$
0	0	0	1	1	1	1
0	1	0	1	1	0	1
1	0	0	1	0	1	1
1	1	1	0	0	0	0

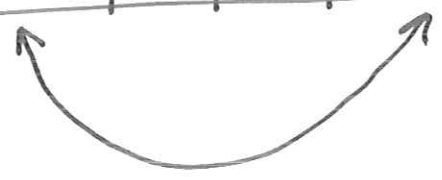

1st Distributive: $a \cdot (b + c) = (a \cdot b) + (a \cdot c)$ ✓


a	b	c	b + c	$a \cdot (b + c)$	a · b	a · c	$(a \cdot b) + (a \cdot c)$
0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	1	1	1	0	1	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1



Logic Gates:



a	b	$a \cdot b$
0	0	0
0	1	0
1	0	0
1	1	1

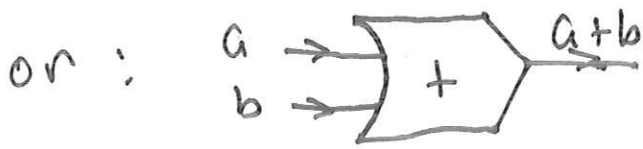


a	b	$a + b$
0	0	0
0	1	1
1	0	1
1	1	1




a	\bar{a}
0	1
1	0

and

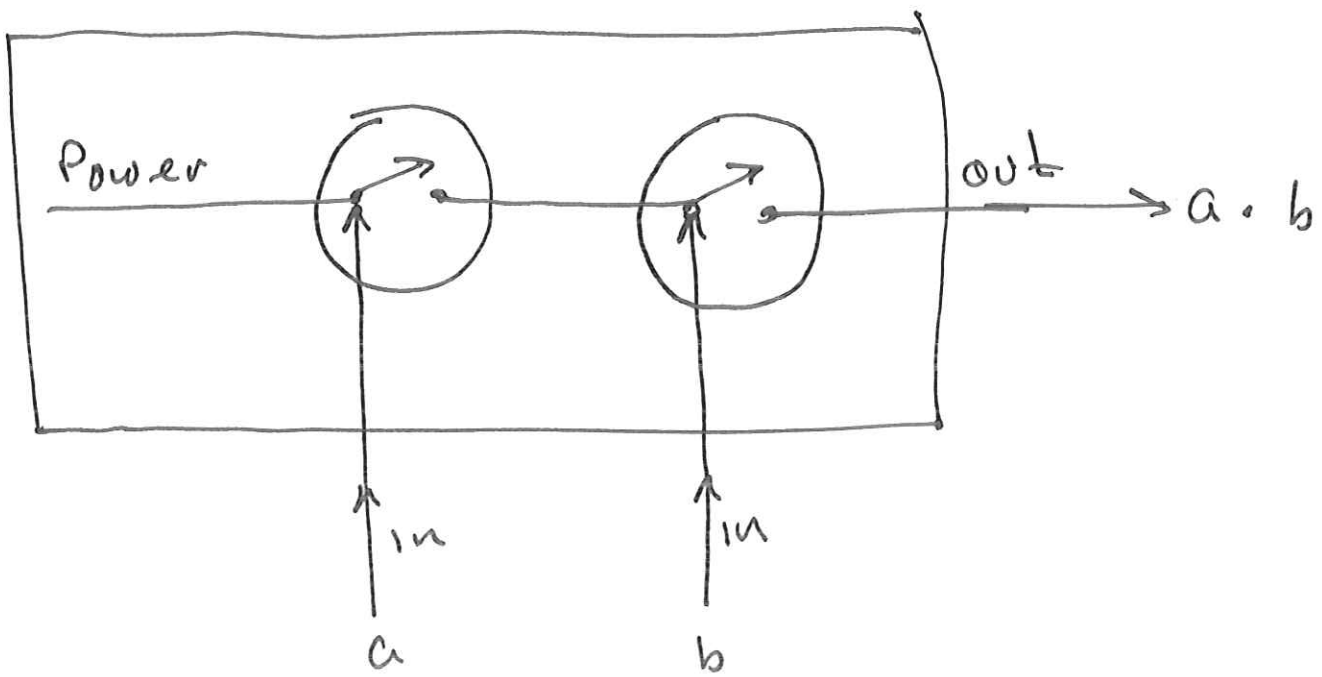


Or

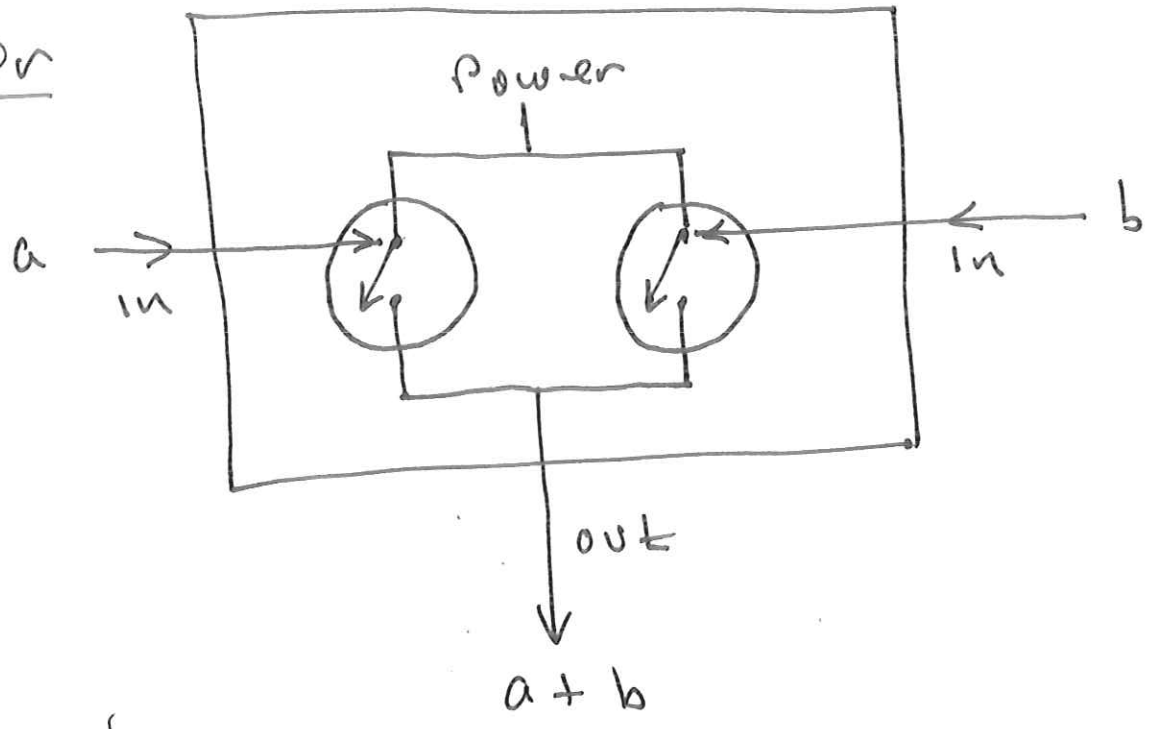

✓

NOT

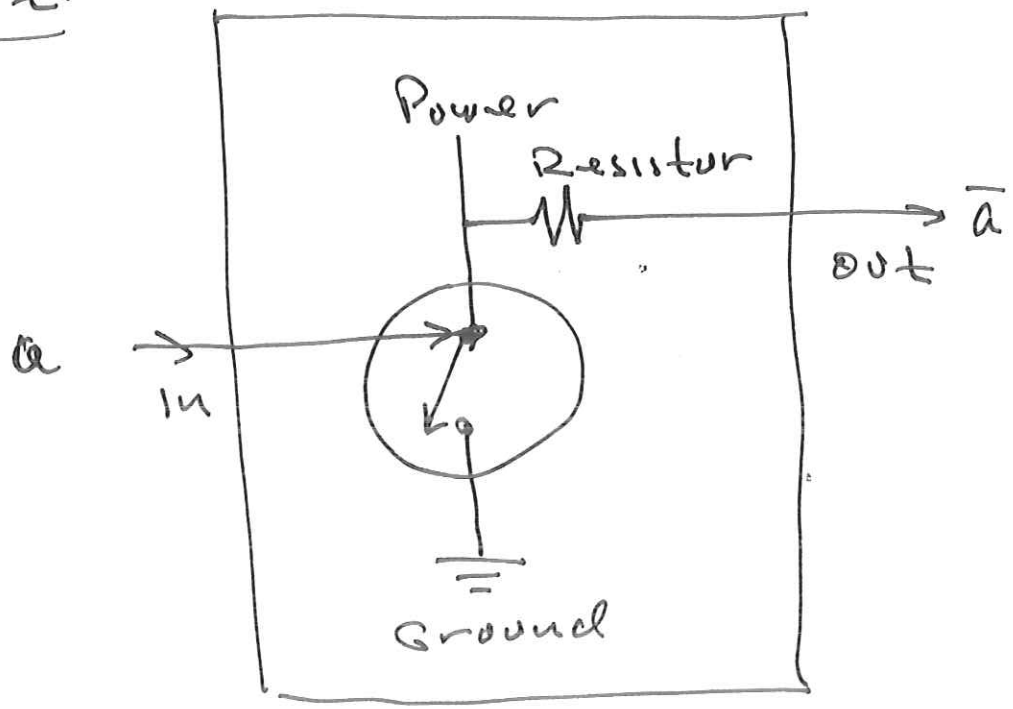


another identity: $a \oplus b = (a \cdot \bar{b}) + (\bar{a} \cdot b)$


a	b	$a \oplus b$	\bar{a}	\bar{b}	$a \cdot \bar{b}$	$\bar{a} \cdot b$	$(a \cdot \bar{b}) + (\bar{a} \cdot b)$
0	0	0	1	1	0	0	0
0	1	1	1	0	0	1	1
1	0	1	0	1	1	0	1
1	1	0	0	0	0	0	0



exor gate:

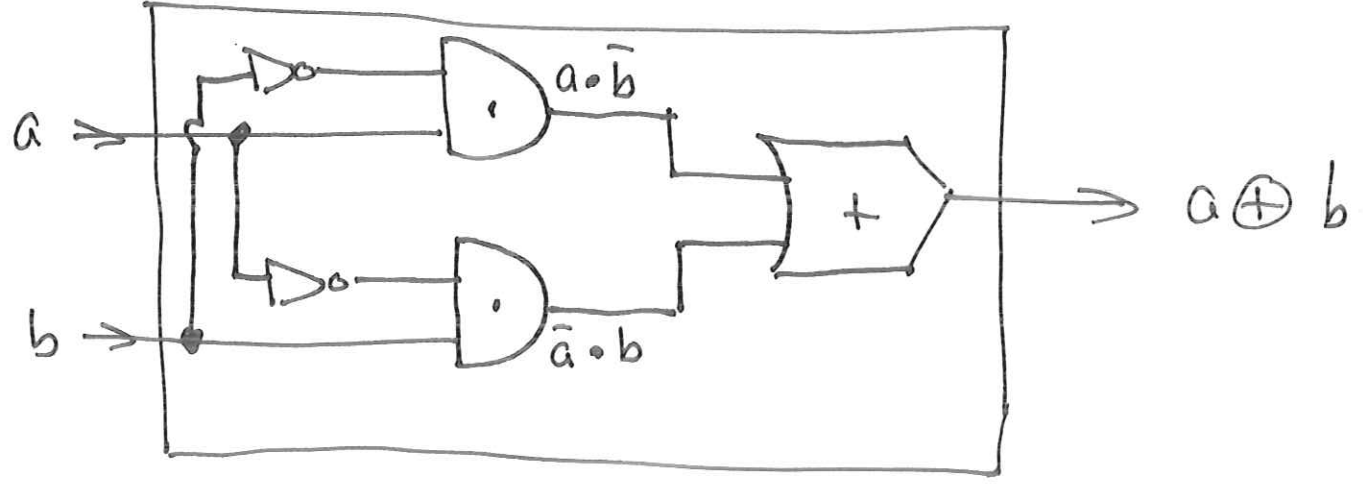

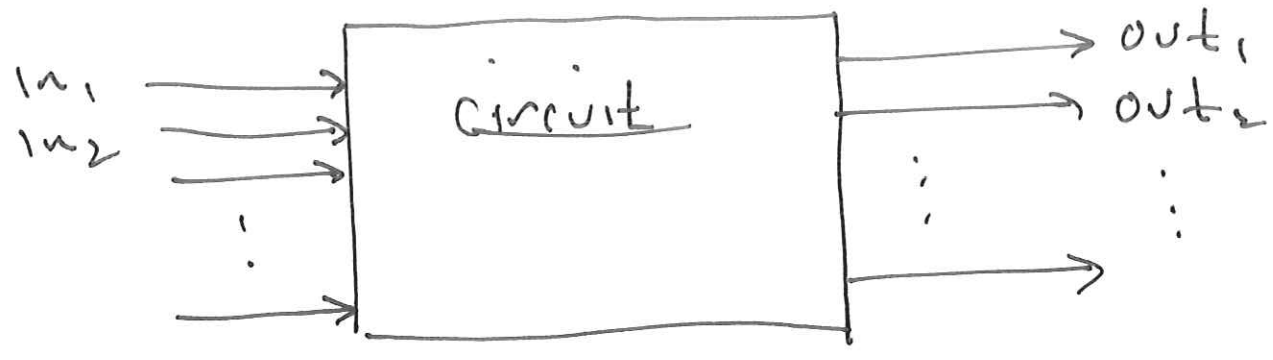
a Combinational circuit is a collection of logic gates that transform some binary inputs into binary outputs



≡ x.

$$\# \text{Transistors} = 2 + 1 + 2 + 1 = 6$$

9

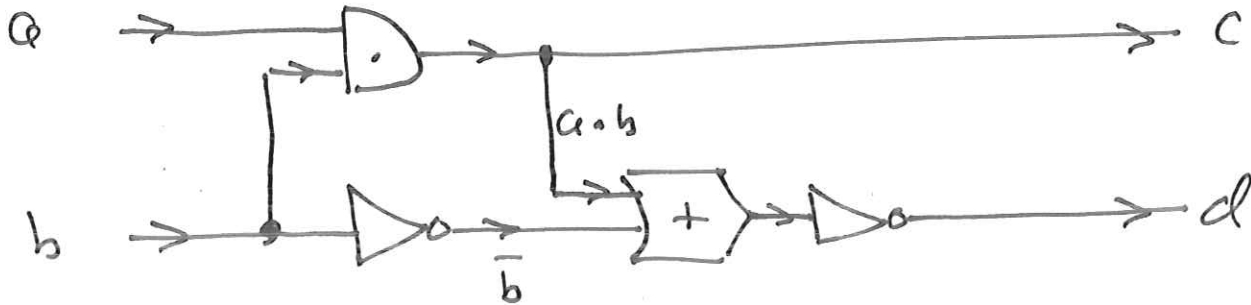

a	b	c	d
0	0	0	0
0	1	0	1
1	0	0	0
1	1	1	0

note:


$$c = a \cdot b$$

$$d = (a \cdot b) + \overline{b} = \overline{a} \cdot b$$

✓ Exercise: Show these are equivalent by truth table


a	b	\bar{a}	\bar{b}	$\bar{a} \cdot b$	$a \cdot b$	$(a \cdot b) + \bar{b}$	$(a \cdot b) + \bar{b}$
0	0	1	1	0	0	1	0
0	1	1	0	1	0	0	1
1	0	0	1	0	0	1	0
1	1	0	0	0	1	1	0

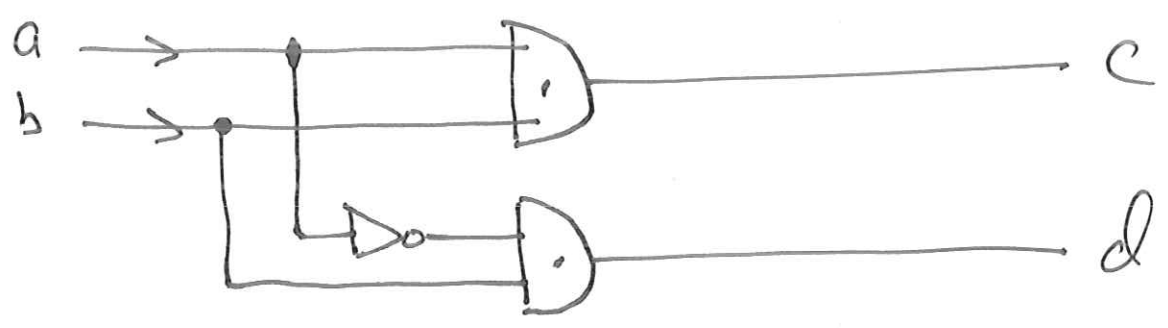now that: $c = a \cdot b$
 $d = \bar{a} \cdot b$



#transistors = 2 + 2 + 1 = 5

Correspondence:


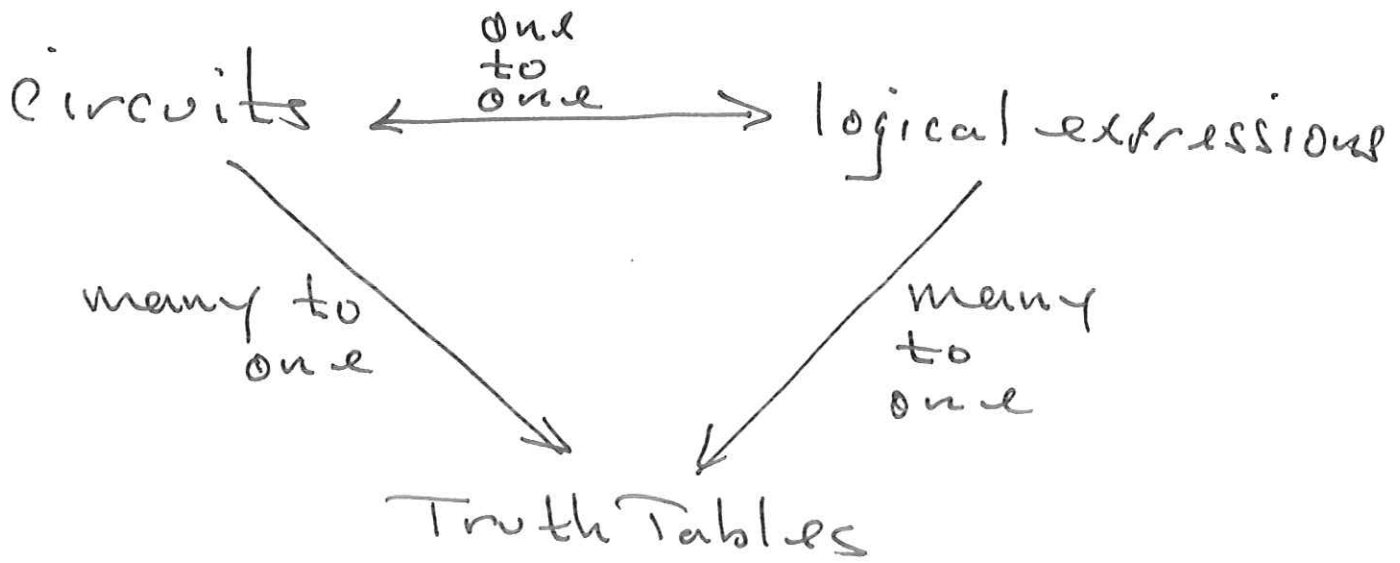


Ex. design a 1-bit compare for equality circuit

a	b	c
0	0	1
0	1	0
1	0	0
1	1	1

note: $c = (\bar{a} \cdot \bar{b}) + (a \cdot b)$

Exercise: check this

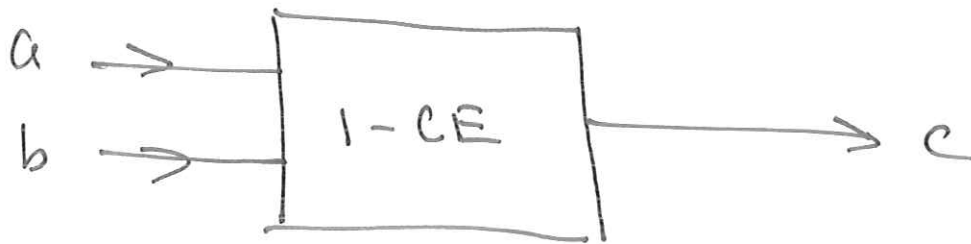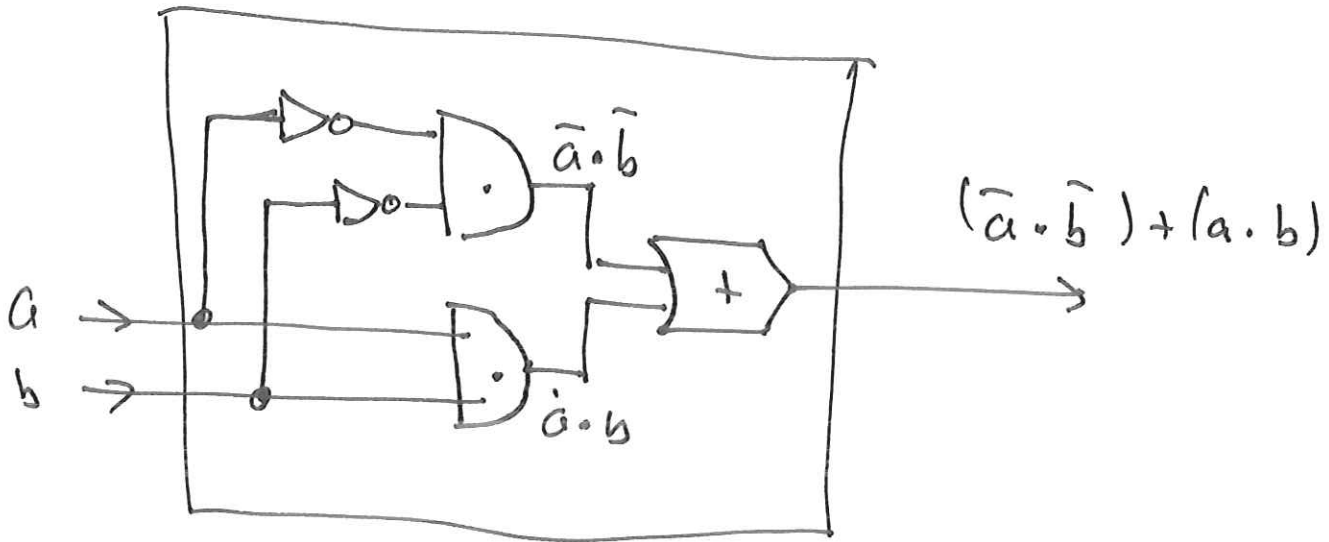

Ex. n-bit comp for equality

Inputs:

$a_{n-1} a_{n-2} \dots a_1 a_0$


$b_{n-1} b_{n-2} \dots b_1 b_0$

Output: 1 if equal 0 otherwise

INPUTS: TWO n BIT BINARY NUMBERS

$[a_{n-1} \dots a_0]_2$, $[b_{n-1} \dots b_0]_2$

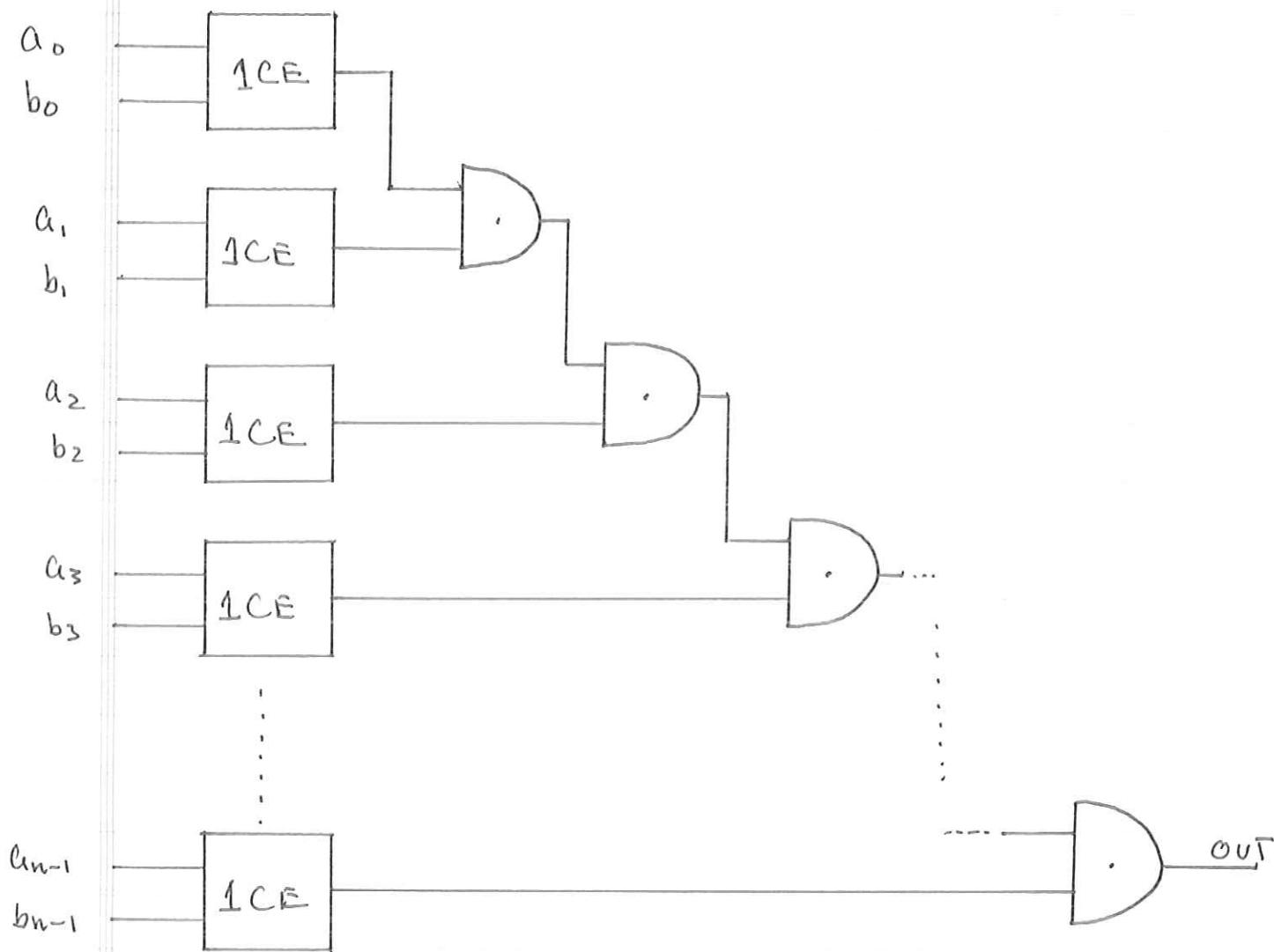OUTPUT: 1 IF EACH $a_i = b_i$ ($0 \leq i \leq n-1$),
0 OTHERWISE



How many rows and columns would the truth table for this circuit have?

ANSWER: 2^{2n} Rows
 $2n+1$ Columns