


CNAPS 10 11-9-10

EX. n-bit full adder

for example $n=8$

```
  1 0 1 1 0 1 1 0 0
    1 0 0 1 0 1 1 0
    1 0 1 1 0 0 1 1
  -----
  1 0 1 0 0 1 0 0 1
```

First Build 1-bit Adder

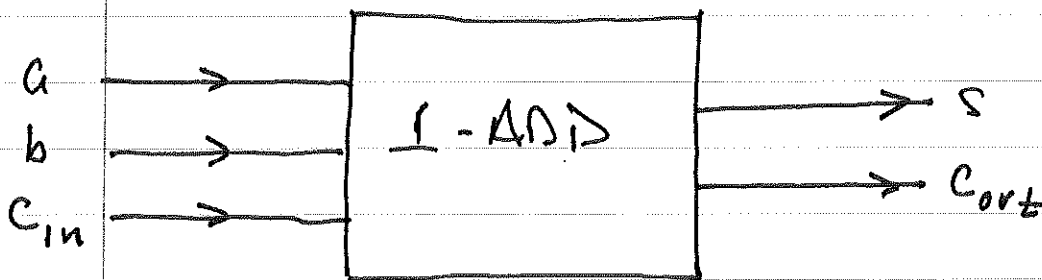

inputs			outputs	
a	b	c	C _{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Circuit Design Algorithm:

for each output column


for each row containing a 1 in that col
 form "product" corres. to inputs
 form "sum" of these "products"

Design circuit corres. to logical exp.

$$C_{out} = \bar{a} \cdot b \cdot c + a \cdot \bar{b} \cdot c + a \cdot b \cdot \bar{c} + a \cdot b \cdot c$$






$$S = \bar{a} \cdot \bar{b} \cdot c + \bar{a} \cdot b \cdot \bar{c} + a \cdot \bar{b} \cdot \bar{c} + a \cdot b \cdot c$$

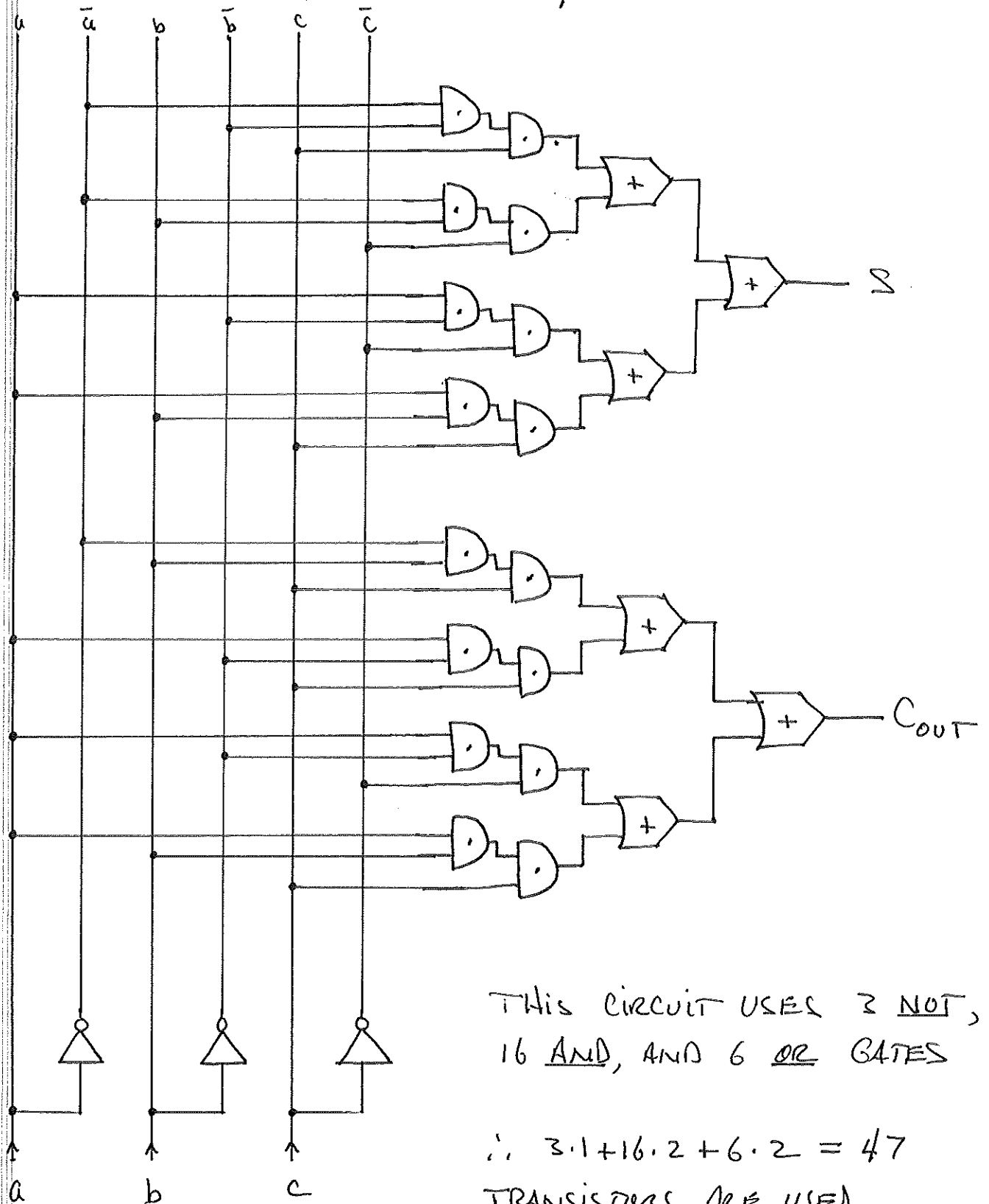WE NEED A SYSTEMATIC WAY TO DRAW CIRCUITS:




Circuits \leftrightarrow Parenthesized logical expressions

3

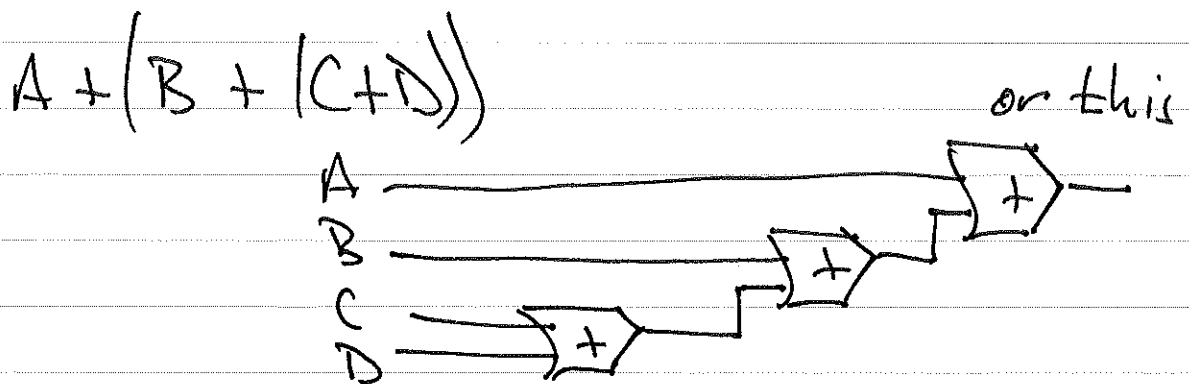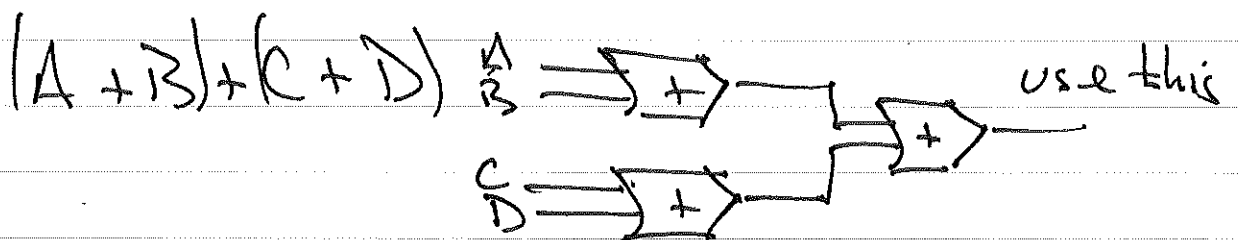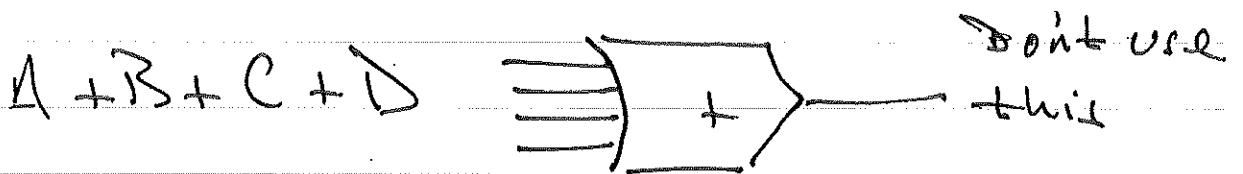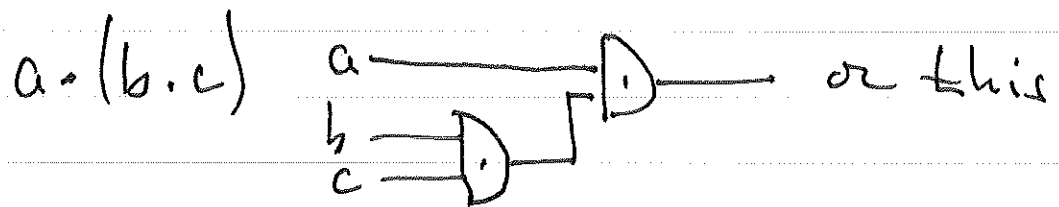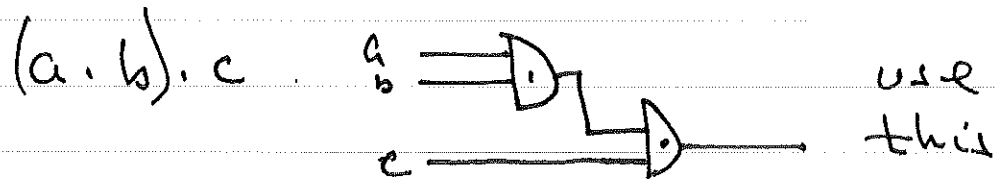

TO CONSTRUCT THE FULL N-BIT ADDER WE COMBINE N COPIES OF THE ABOVE CIRCUIT.
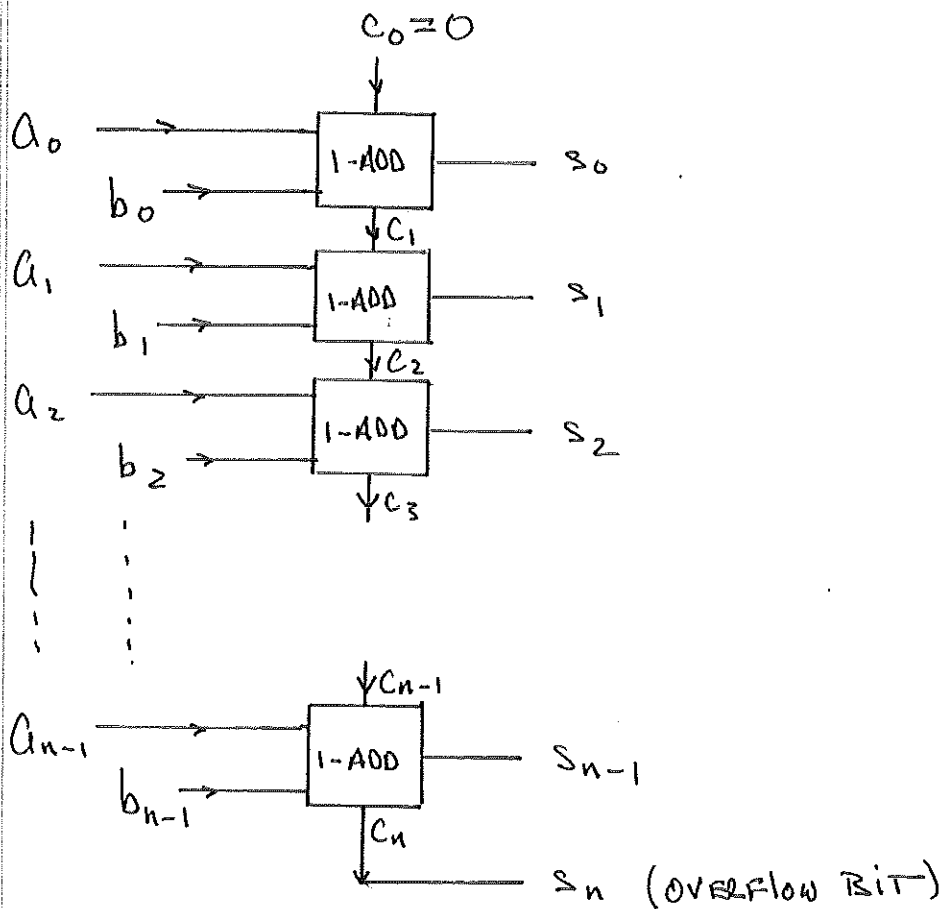
$$\underbrace{[a_{n-1} \dots a_0]_2 + [b_{n-1} \dots b_0]_2}_{\text{INPUTS}} = \underbrace{[s_n s_{n-1} \dots s_0]_2}_{\text{OUTPUT}}$$




THE N-BIT FULL ADDER USES $47N$ TRANSISTORS.
 FOR EXAMPLE, A 32-BIT ADDER USES $47 \cdot 32$
 $= 1504$ TRANSISTORS

[d]

Subtraction:

Ex
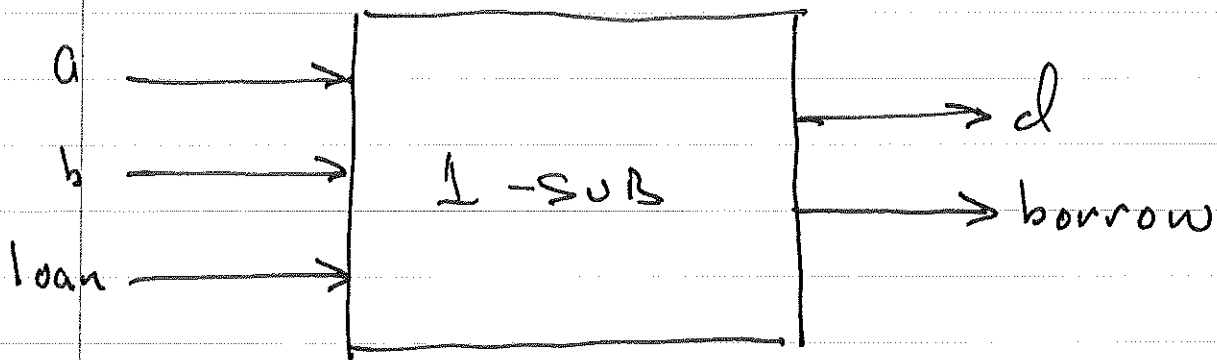
$$\begin{array}{r} 0 \ 0 \\ \times \times \ 0 \ 1 \\ \hline 0 \ 1 \ 1 \ 1 \\ \hline 0 \ 1 \ 1 \ 0 \end{array}$$



if $a - b - \text{loan} < 0$
 borrow = 1
else
 borrow = 0
 $d = 2 \cdot \text{borrow} + a - b - \text{loan}$

5

inputs			output	
a	b	loan	d	borrow
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$d = \bar{a}\bar{b}l + \bar{a}b\bar{l} + a\bar{b}\bar{l} + abl$$


borrow = exercise !!

Exercise: Draw The Circuit for 1-SUB.


once 1-SUB is built we can build an n-bit subtractor for any n.

USING 1-SUB WE CAN BUILD AN N-BIT SUBTRACTOR

EX n=4

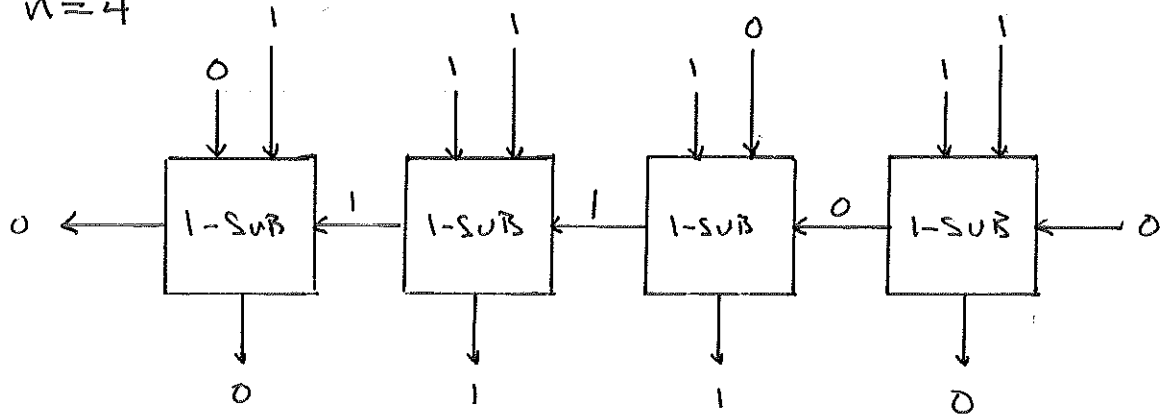

THE GENERAL N-BIT SUBTRACTOR LOOKS LIKE

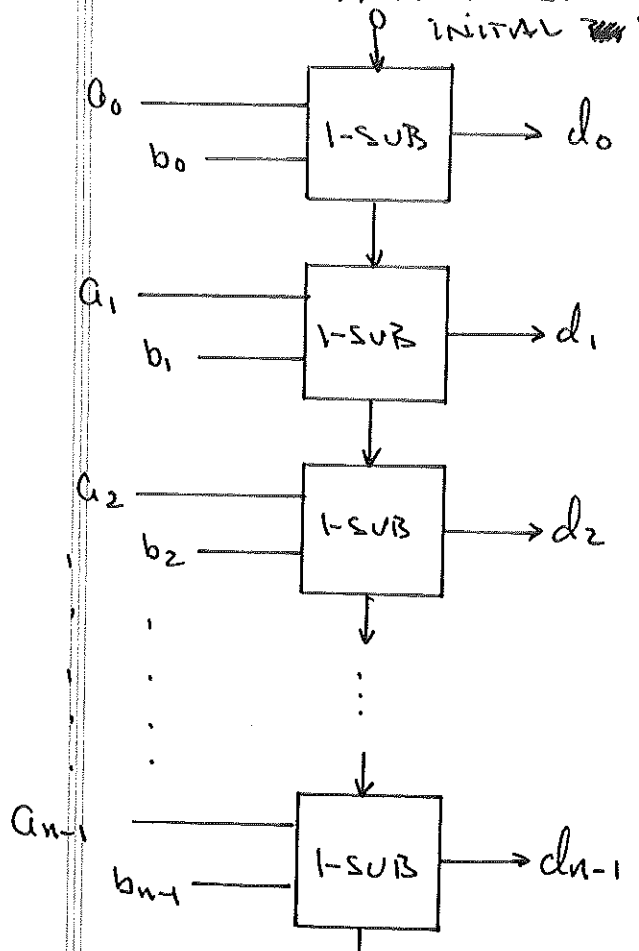

$$[d_0 \dots d_{n-1}] = [a_0 \dots a_{n-1}] - [b_0 \dots b_{n-1}]$$

COMPARISON BIT = $\begin{cases} 1 & \text{if } [a_0 \dots a_{n-1}] < [b_0 \dots b_{n-1}] \\ 0 & \text{OTHERWISE} \end{cases}$