
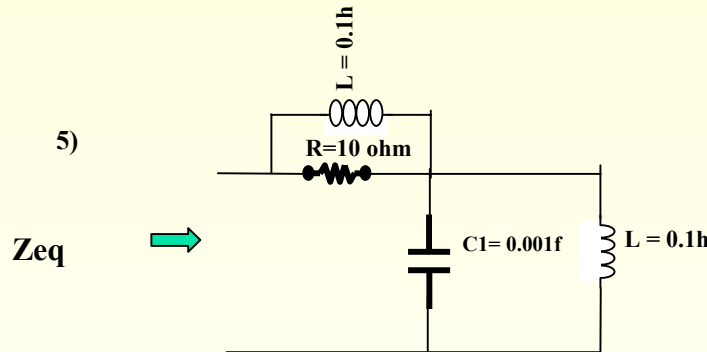
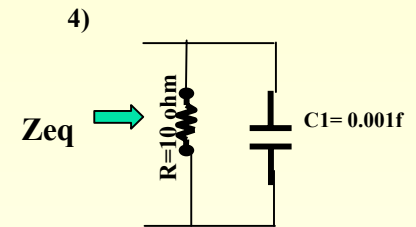
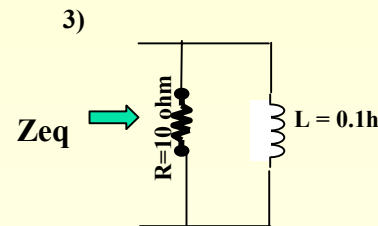
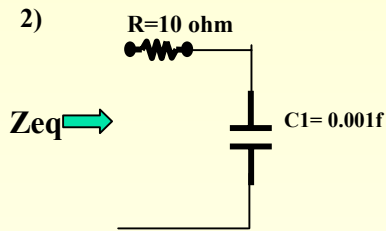


# Quiz 5

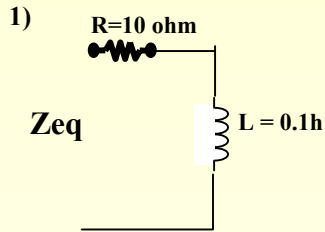1) Calculate the equivalent impedance and express it in complex and polar forms for an input frequency of  $\omega=100$  :



2) Find current, average and reactive power for 1) and 4) for a voltage source of  $v(t) = 10 \cos 100t$

# Quiz 5 Answers

- 1)
- 1)  $Z_{eq} = 10 + j10, 10\sqrt{2} \angle 45$
  - 2)  $Z_{eq} = 10 - j / 100 * .001 = 10 - j10, 10\sqrt{2} \angle - 45$
  - 3)  $Z_{eq} = j100 / (10 + j10) = j100 (10 - j10) / 200 = 5 + j5\sqrt{50} \angle 45$
  - 4)  $Z_{eq} = j10 / (j - 1) = 5 - j5, \sqrt{50} \angle - 45$
  - 5)  $Z_{eq} = (5 + j5) + (5 - j5) = 10, 10 \angle 0$

2)

**Average Power =  $V_m * I_m (\cos\theta) / 2$**

**Reactive Power =  $v_m * I_m (\sin\theta) / 2$**

- 1)  $3.53 * (\cos 45) = 2.5\omega$  active power  
 $3.53 * (\sin 45) = 2.5w$  reactive power

$7.07 (\cos -45) = 5 w$  active power  
 $7.07 (\sin -45) = 5w$  capacitive reactive power